

# CpE 690: Introduction to VLSI Design

## Lecture 9 SPICE Simulation





Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology

Hoboken, NJ 07030

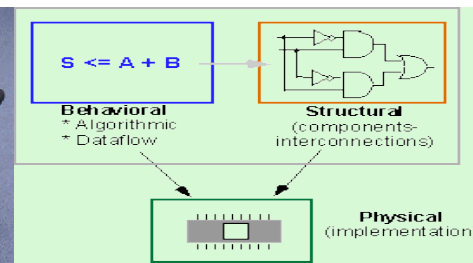   Adapted from Lecture Notes, David Mahoney Harris CMOS VLSI Design



# Simulation of VLSI Circuits

- Complex circuits cannot be analyzed using analytic expressions for transistor behavior
  - simple models useful for estimation to compare competing approaches
  - modern transistors are highly non-linear devices that deviate significantly from first-order models (e.g. Shockley)
  - need simulation to confidently verify correct operation and performance
    - over range of process, temperature & voltage variations
- Simulation at different levels of abstraction:
  - Process simulation e.g. SUPREME
  - Device simulation e.g. PROPHET
  - Circuit simulation e.g. SPICE
  - Logic Simulation e.g. ModelSim, Isim (VHDL, Verilog)
  - Architectural Simulation (processor specific)
  - Algorithmic Simulation (MATLAB)

# Introduction to SPICE

- **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis
  - Developed in 1970's at Berkeley
  - Many commercial versions are available
    - HSPICE is a robust industry standard
    - PSpICE is PC based – also widely used
    - LTSpICE free version from Linear Technology
    - WinSpice is another Windows based version
    - T-Spice is part of the Tanner Package
- Originally written in FORTRAN for punch-card machines
  - Circuits elements are called *cards*
  - Complete description is called a SPICE *deck*

# Structure of a SPICE Deck

*A SPICE deck may contain:*


- Circuit components
  - netlist of resistors, capacitors, transistors, subcircuits etc.
  - netlist can be
    - handwritten
    - extracted from layout
    - derived from schematic
- Sources
  - voltage sources, current sources etc. to drive circuit
- Device models
  - transistor models, resistor models, diode models etc.
- SPICE commands
  - initial conditions, type of analysis, plot specification etc.

# Manually Writing a SPICE Deck


- Writing a SPICE deck is like writing a good program
  - Plan: sketch schematic on paper or in editor
    - Modify existing decks whenever possible
  - Code: strive for clarity
    - Start with name, email, date, purpose
    - Generously comment
  - Test:
    - Predict what results should be
    - Compare with actual
    - Understand any differences before you proceed!
 
# Example: RC Filter

```
* RC_Filter.cir
* backland@stevens.edu 4/2/12
* Find the response of RC circuit to rising input
*
*-----
* Parameters and options
*-----
.options gmin=1e-9
*-----
* Simulation netlist
*-----
R1      in out 2k
C1      out gnd 100f
*-----
* Sources
*-----
Vin     in gnd  pw1 0ps 0 100ps 0 150ps 1.0 1ns 1.0
*-----
* Commands
*-----
.tran 10ps 1ns
.print v(in) v(out)
.end
```



# RC\_Filter T-Spice Result

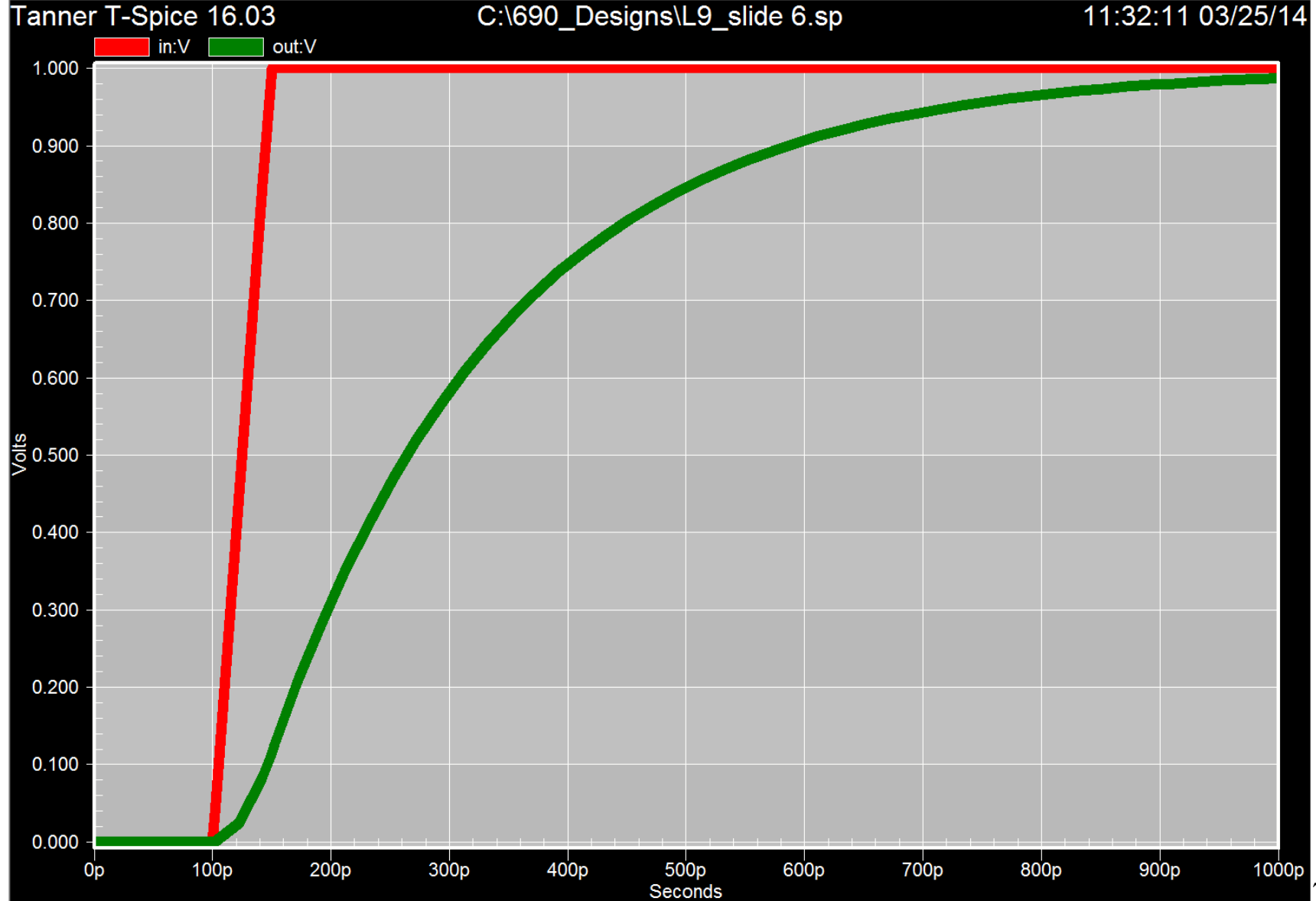

# Sources

## ❑ *DC Source*

vdd vdd gnd 2.5


## ❑ *Piecewise Linear Source*

vin in gnd pw1 0ps 0 100ps 0 150ps 1.0 1ns 1.0

## ❑ *Pulsed Source*

vck clk gnd PULSE 0 1.0 0ps 100ps 100ps 300ps 800ps

**PULSE v1 v2 td tr tf pw per**

 



# Circuit Elements

Letter	Element
R	Resistor
C	Capacitor
L	Inductor
K	Mutual Inductor
V	Independent voltage source
I	Independent current source
M	MOSFET
D	Diode
Q	Bipolar transistor
W	Lossy transmission line
X	Subcircuit
E	Voltage-controlled voltage source
G	Voltage-controlled current source
H	Current-controlled voltage source
F	Current-controlled current source

# Units

Letter	Unit	Magnitude
a	atto	$10^{-18}$
f	femto	$10^{-15}$
p	pico	$10^{-12}$
n	nano	$10^{-9}$
u	micro	$10^{-6}$
m	milli	$10^{-3}$
k	kilo	$10^3$
x	mega	$10^6$
g	giga	$10^9$


**Ex: 100 femptofarad capacitor = 100fF, 100f, 100e-15**

# Analyses


<b>.ac</b>	Small signal AC (linear)
<b>.dc</b>	DC transfer function
<b>.disto</b>	Distortion
<b>.noise</b>	Noise (linear)
<b>.op</b>	Operating Point
<b>.pz</b>	Pole-zero (linear)
<b>.sens</b>	DC or AC Sensitivity
<b>.temp</b>	Temperature sweep
<b>.tf</b>	Transfer function (linear)
<b>.tran</b>	Transient
 
# DC Analysis

```
* MOS_IV.cir
* backland@stevens.edu 4/2/12
* Plot IV characteristics of NMOS device
*-----
* Parameters and options
*-----
.options gmin=1e-9
.include mosis_tsmc_180nm_18.model
.temp 70
*-----
* Simulation netlist
*-----
M1    drain gate gnd gnd NMOS W=0.4u L=0.2u
*-----
* Sources
*-----
Vgs   gate gnd 0
Vds   drain gnd 0
*-----
* Commands
*-----
.dc Vds 0 3.5 0.1  Vgs 0 3.5 0.5
.print id(M1)
.end
```



# T-Spice: I-V Characteristics

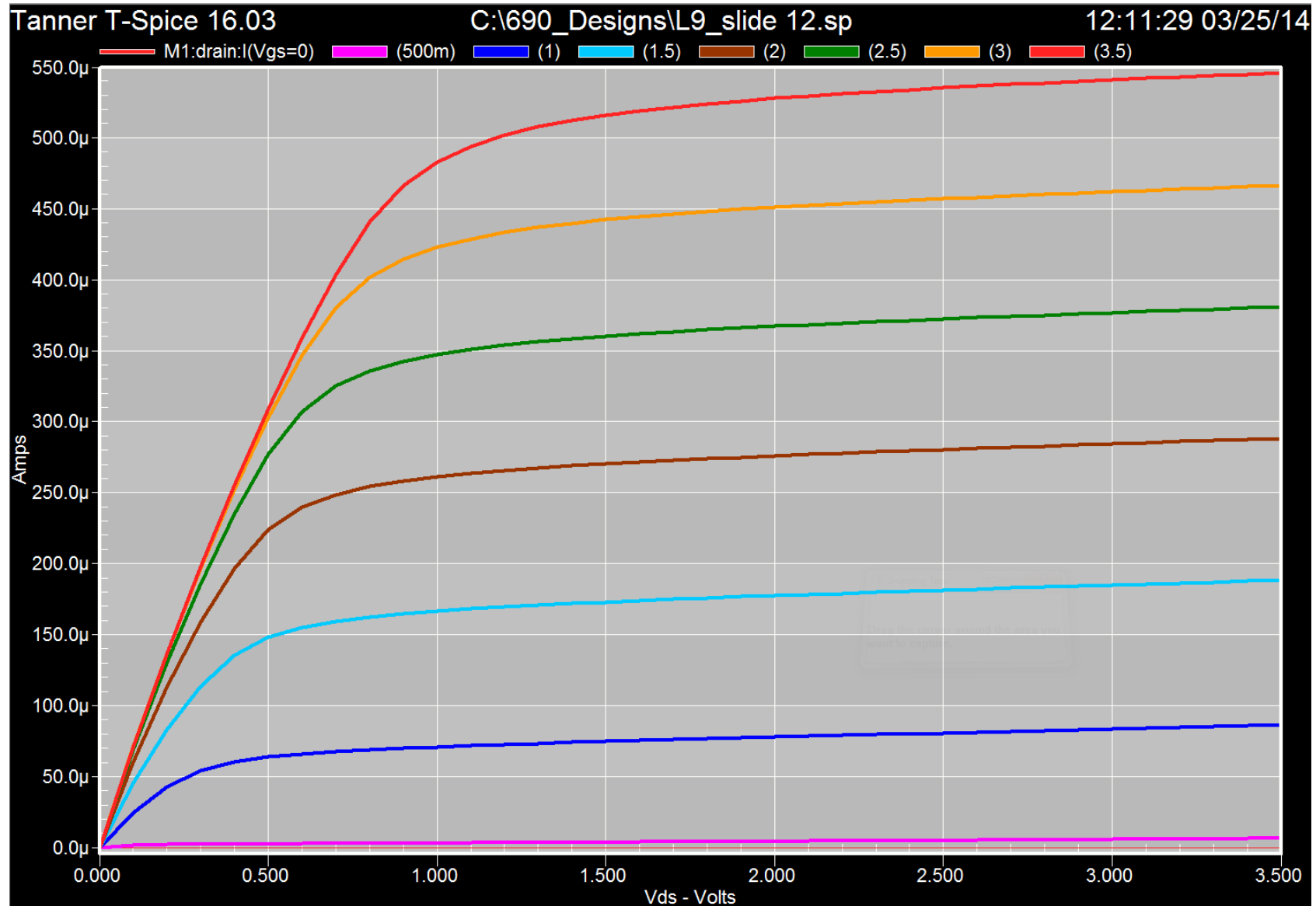

# MOSFET Elements

M element for MOSFET:

Mname drain gate source body type


+ W=<width> L=<length>

+ AS=<area source> AD = <area drain>


+ PS=<perimeter source> PD=<perimeter drain>
 
# Transient Analysis

```
* Inverter.cir
*-----
* Parameters and options
*-----
.options gmin=1e-9
.include mosis_tsmc_180nm_18.model
.param SUPPLY=3.3
*-----
* Simulation netlist
*-----
M1    y a gnd gnd NMOS W=0.4u L=0.2u AD=1.6E-13 PD=1.6u AS=1.6E-13 PS=1.6u
M2    y a vdd vdd PMOS W=0.8u L=0.2u AD=3.2E-13 PD=2.4u AS=3.2E-13 PS=2.4u
*-----
* Sources
*-----
Vvdd  vdd gnd SUPPLY
Vvin  a gnd PULSE 0 SUPPLY 50p 1p 1p 200p 400p
*-----
* Commands
*-----
.tran 5p 400p
.print v(a) v(y)
.end
```



# Inverter Transient Results

 




# Subcircuits

- Build hierarchy by declaring common elements as subcircuits

```
.subckt inv a y N=1 P=2
M1 y a gnd gnd NMOS W='N*0.4u' L=0.2u AS='N*0.4u*0.2u'
+ PS='2*N*0.4u+0.4u' AD='N*0.4u*0.2u' PD='2*N*0.4u+0.4u'
M2 y a vdd vdd PMOS W='P*0.4u' L=0.2u AS='P*0.4u*0.2u'
+ PS='2*P*0.4u+0.4u' AD='P*0.4u*0.2u' PD='2*P*0.4u+0.4u'
.ends
```

- Ex: Fanout-of-4 Inverter Delay

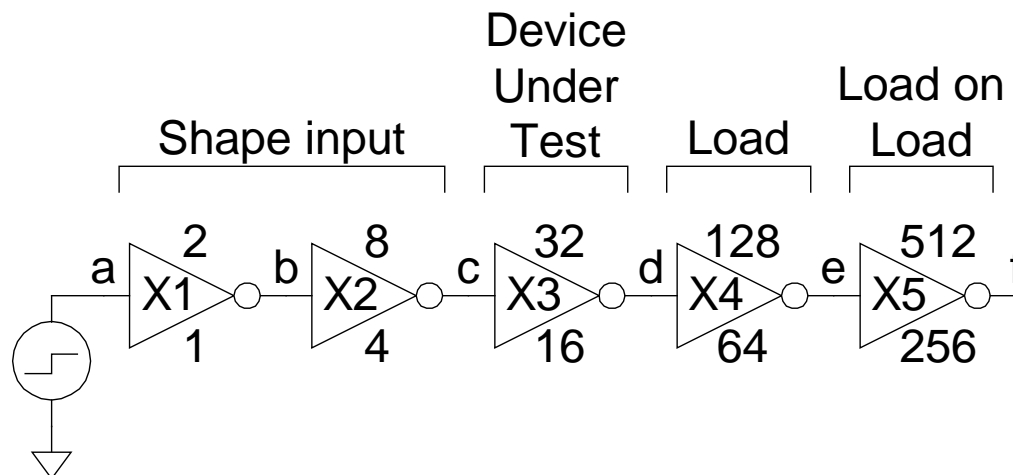

# FO4 Inverter Delay (T-Spice)

```
* Inv_FO4_delay.cir
*-----
* Parameters and options
*-----

.options gmin=1e-9
.include mosis_tsmc_180nm_18.model
.param SUPPLY=3.3
.global vdd gnd
*-----

* Simulation netlist
*-----

.subckt inv a y N=1 P=2
M1 y a gnd gnd NMOS W='N*0.4u' L=0.2u AS='N*0.4u*0.2u'
+ PS='2*N*0.4u+0.4u' AD='N*0.4u*0.2u' PD='2*N*0.4u+0.4u'
M2 y a vdd vdd PMOS W='P*0.4u' L=0.2u AS='P*0.4u*0.2u'
+ PS='2*P*0.4u+0.4u' AD='P*0.4u*0.2u' PD='2*P*0.4u+0.4u'
.ends


X1 a b inv N=1 P=2
X2 b c inv N=4 P=8
X3 c d inv N=16 P=32
X4 d e inv N=64 P=128
X5 e f inv N=256 P=512

*shape input
*shape input
*device under test
*load
*load on load
```


# FO4 Inverter Delay (cont.)

```
*-----  
* Sources  
*-----  
Vvdd  vdd gnd SUPPLY  
Vvin  a gnd PULSE 0 SUPPLY 0p 100p 100p 600p 1200p  
*-----  
* Commands  
*-----  
.tran 1p 1200p  
  
.print v(a) v(b) v(c) v(d) v(e)  
  
.measure tran tpdr trig v(c) val='SUPPLY/2' fall=1  
+ targ v(d) val='SUPPLY/2' rise=1  
.measure tran tpdf trig v(c) val='SUPPLY/2' rise=1  
+ targ v(d) val='SUPPLY/2' fall=1  
.measure tran trise trig v(d) val='0.2*SUPPLY' rise=1  
+ targ v(d) val='0.8*SUPPLY' rise=1  
.measure tran tfall trig v(d) val='0.8*SUPPLY' fall=1  
+ targ v(d) val='0.2*SUPPLY' fall=1  
.end
```

# FO4 Results

 
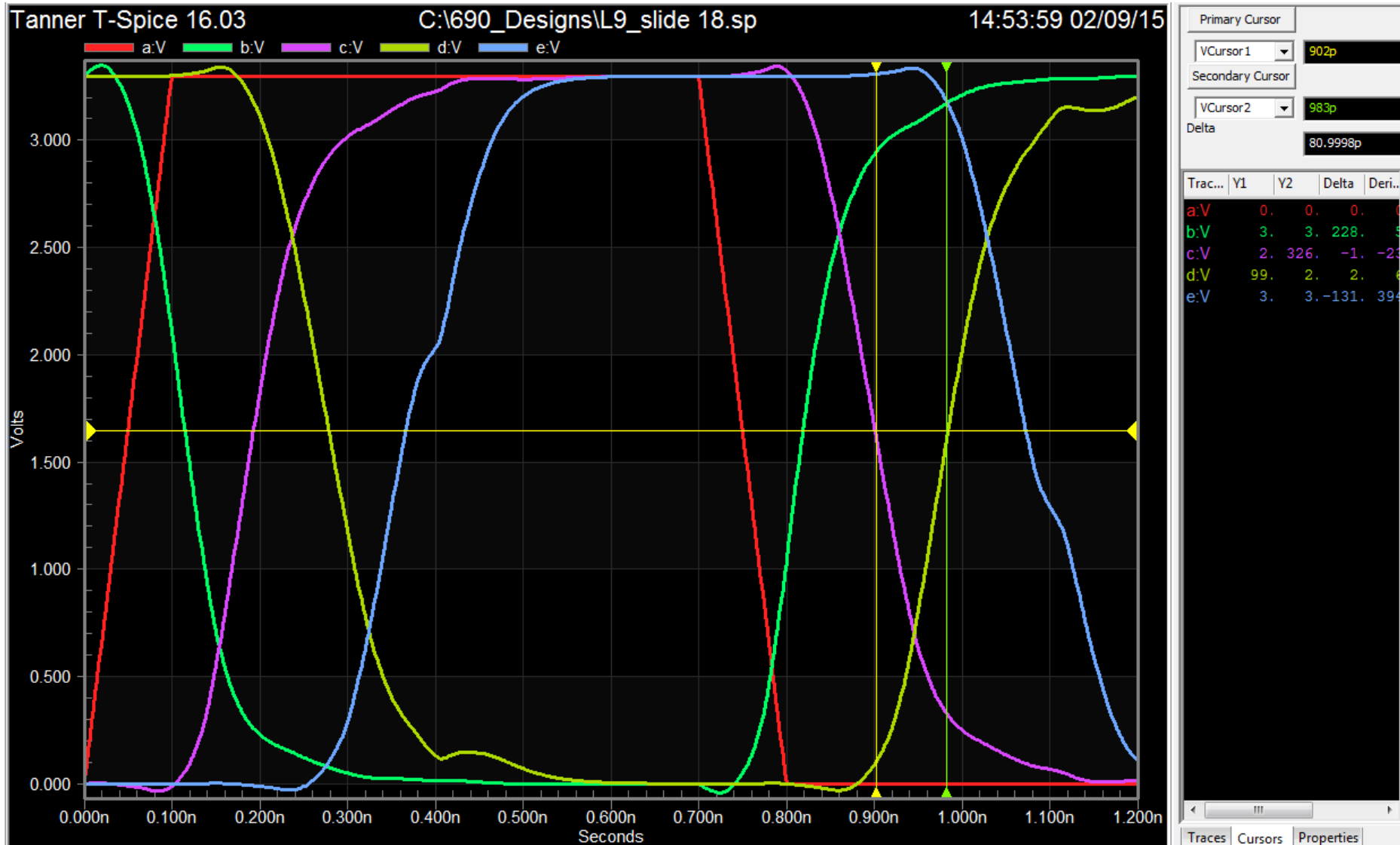
# Using cursors to measure propagation delay



# Using SPICE commands to measure delay

- generated using .measure commands in SPICE deck:

