

CPE 690: Introduction to VLSI Design

Lecture 4





VHDL – part III

Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology


Hoboken, NJ 07030

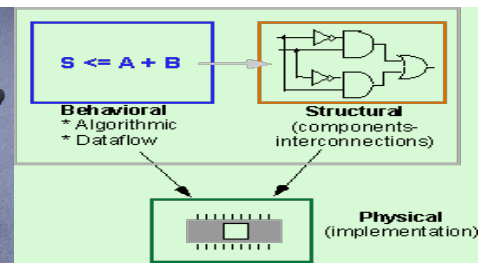   


VHDL Synthesis

What is Synthesis?

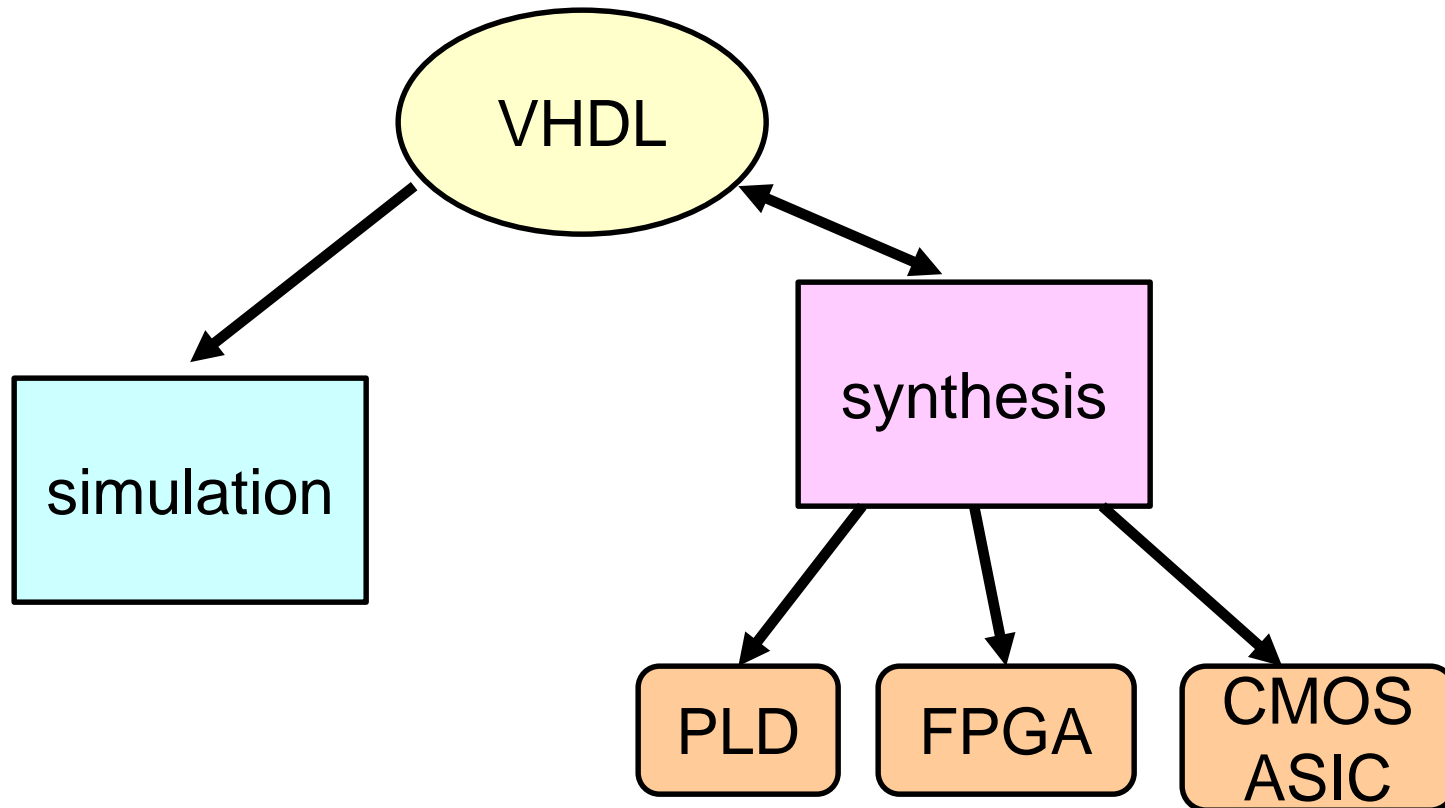- Process of creating a RTL or gate level net-list from a VHDL model
- Net-list can be used to create a physical (hardware) implementation



Synthesis Process

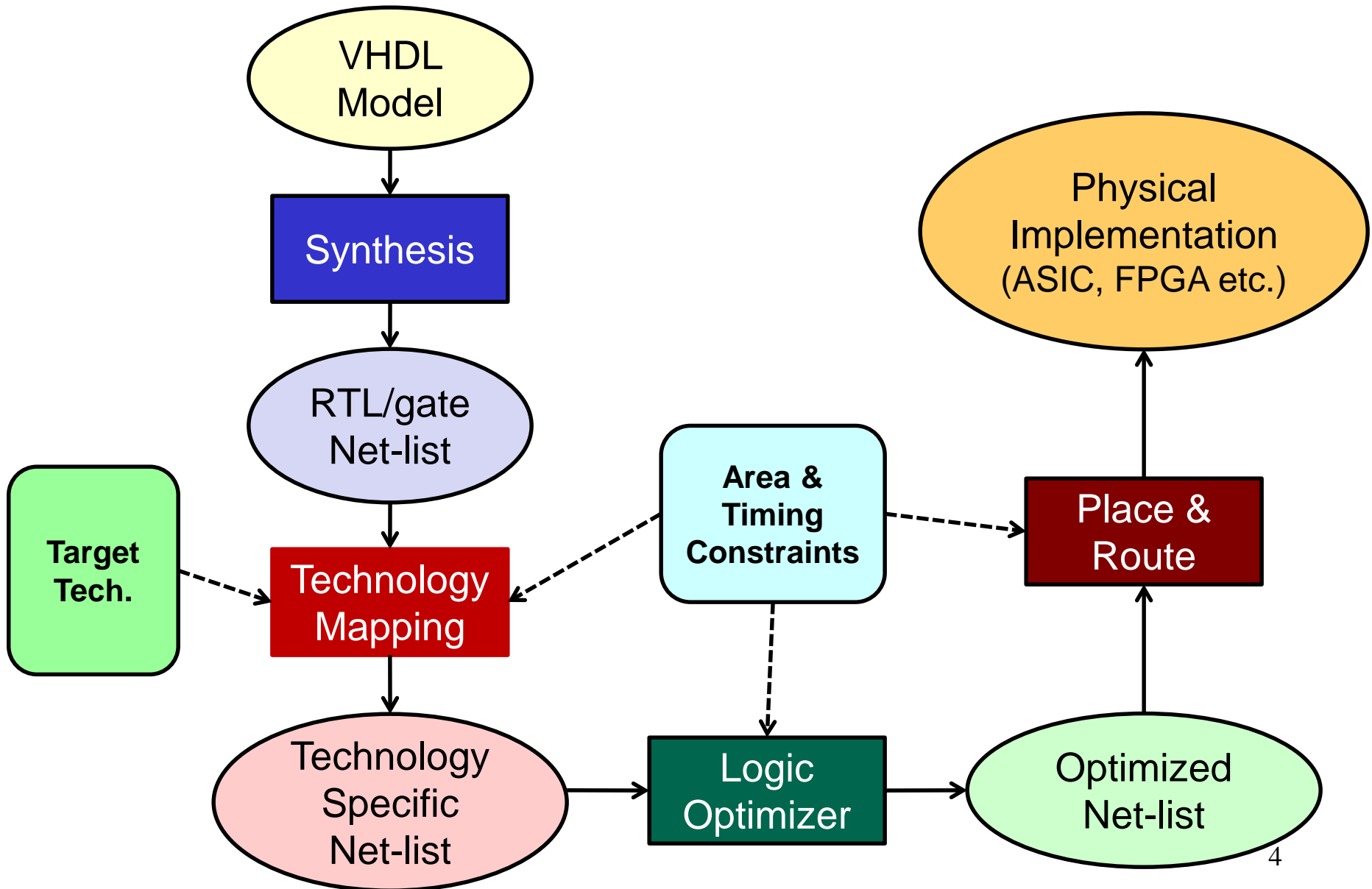

Limitations of Synthesis

- VHDL can model a hardware system at different levels of abstraction from gate level up algorithmic level
- Synthesis tools cannot, in general, map arbitrary high level behavioral models into hardware.
- Many VHDL constructs have no hardware equivalent:
 - wait for 10 ns;**
 - signal a1: real;**
 - y<= x'last_value;**
 - assert a=b report “mismatch” severity error;**
- Even if VHDL code is synthesizable, it may lead to very inefficient (in terms of area, speed) implementation
- In moving from VHDL high level behavioral description to synthesizable VHDL hardware description, designer needs to know:
 - What subset of VHDL is **synthesizable**
 - What hardware is **inferred** by various VHDL constructs

Inference

- Synthesis is the process of hardware [inference](#) followed by [optimization](#)
- The synthesis compiler [infers](#) hardware structures from your VHDL code
- Those hardware structures are subsequently [optimized](#) to meet your area and/or speed constraints.
- Part of being a good synthesis designer is being able to put yourself in the place of the compiler and understand what hardware constructs are likely to be inferred from your code.


Inferring Signals

- In VHDL, signals are used to represent timed information flow between subsystems.
- When synthesizing from VHDL, the basic hardware implementations of signals are:
 - Wires
 - Latches (level sensitive)
 - Flip-flops (edge triggered)
- Signals generated by combinational circuits (where output depends only on the current value of the inputs) can be implemented as wires
- Signals generated by sequential circuits (where output depends on current and previous value of inputs) are implemented as latches or flip-flops

Flip-flop vs. Latch


Flip-flop

*stores data when
clock rises*

 

Latch

 *passes data when G is high
stores data when G is low*



Inference from Declarations

- When a signal is declared, there needs to be sufficient information to determine the correct number of bits

```
signal result: std_logic_vector (12 downto 0);  
signal count: integer;  
signal index: integer range 0 to 18:= 0;
```

```
type state_type is (state0, state1, state2, state3);  
signal next state: state_type;
```

- How many bits are required to represent *count* ?
 - Compilers are conservative: they will only perform transformations that are guaranteed not to produce incorrect answers
- Initializations are often ignored
 - Need to include run-time initialization in hardware (e.g. reset)
- How many bits are required to represent *next_state* ?

Inference from Simple CSA's

target_signal <= *expression*;

e.g. A <= (B **nand** C) **or** Y **after** 12 ns;

- A simple CSA assigns a value to a target signal that is a function of the present value of the signals in the RHS expression.
 - Whenever an event occurs on any signal in *expression*, *target_signal* is re-evaluated.
 - no memory of previous values
- The synthesis compiler will infer a combinational circuit
- Delay information (e.g. **after** 12 ns) will be ignored.
- You can control inferred structure by appropriately grouping logic operations into assignment statements

Logical Grouping

- Use of intermediate signals can be used to infer different logical (RTL) implementations:

```
entity abc is  
port(w, x, y, z: in std_logic;  
      A, B, C: out std_logic);  
end entity abc;
```

```
architecture dataflow of abc is  
signal s1, s2: std_logic;  
begin
```

```
A <= w and x and y and z;
```

```
s1 <= w and x;
```

```
s2 <= y and z;
```




```
B <= s1 and s2;
```

```
s3 <= w and x;
```

```
s4 <= s3 and y;
```


```
C <= s4 and z;
```

```
end architecture;
```

   


Logical Grouping Modified by Mapping

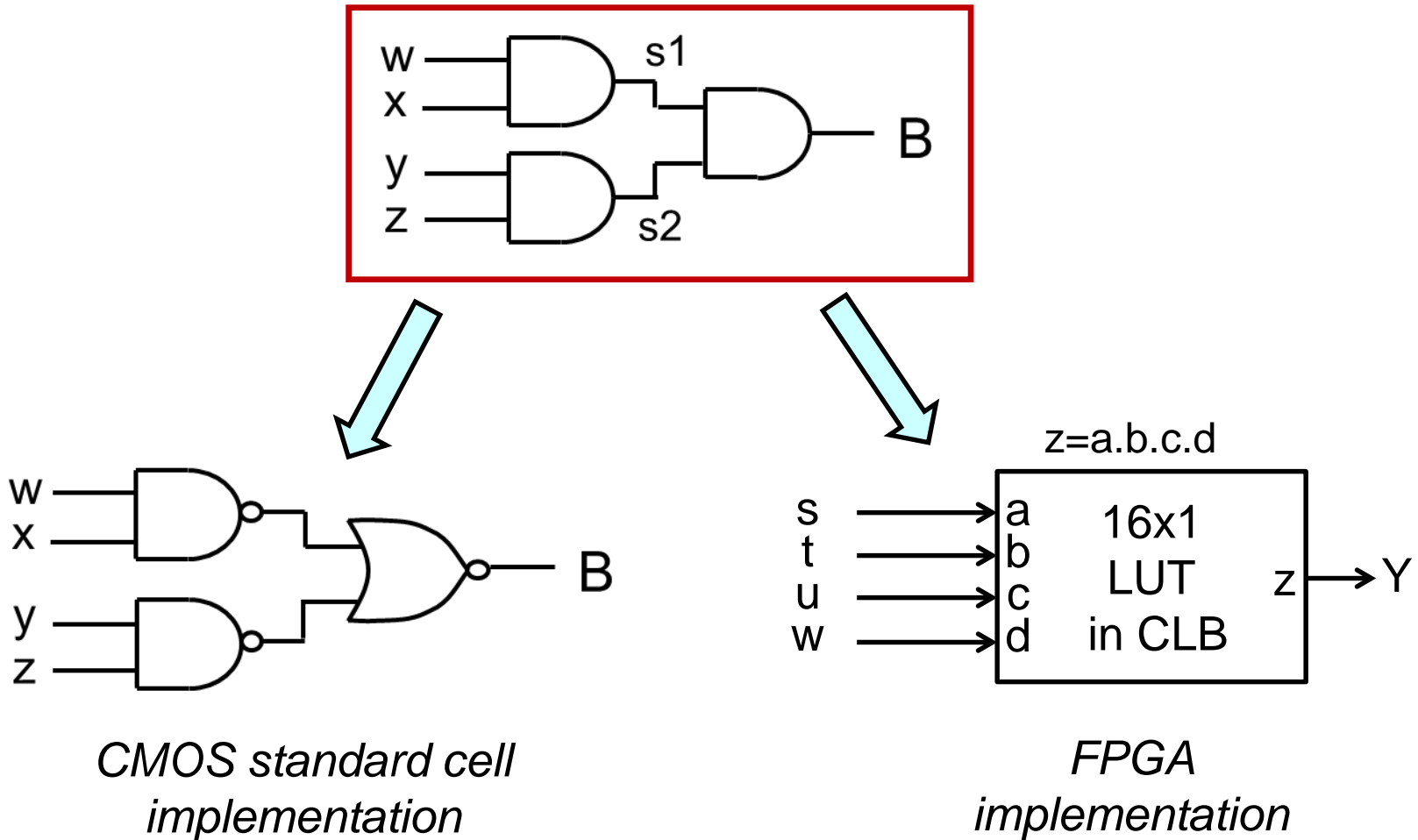- RTL structure may be considerably modified by technology mapping and optimization:




Inference from Conditional Signal Assignment
 
```
architecture cond_sa of mux is
begin
    z <= a and b when sel='0' else
        a or b;
end cond_sa;
```



gate-level implementation

 


FPGA implementation

Incomplete Assignment Implies Latch

- What happens if there are combinations of inputs that do not result in an assignment?
 
```
architecture cond_sa of mux is
begin
    z <= a and b when sel='1';
end cond_sa;
```




- A latch is inferred to cover the case $sel \neq '0'$
 - This is now a sequential circuit – is that what we intended?
- We may not care what the result is when $sel \neq '0'$
- Result is unnecessary, hazardous hardware
 - If we really wanted sequential operation, better to use flip-flop
- If combinational circuit is intention, make sure output is always assigned a value by using a final *else* clause

Conditional Maintains Priority Order

- This is great for priority encoder, but what about multiplexer where all conditions are mutually exclusive?

 architecture behave of mux4 is
begin
 z <= in0 when sel="00" else
 in1 when sel="01" else
 in2 when sel="10" else
 in3 when sel="11" else
 '0';
end behave;



- Only **red** gates are needed to implement multiplexer
- Blue** gates are inferred to maintain priority coding
- Not needed because the clauses are mutually exclusive

Selected Signal Assignment


- SSA is better construct for building a multiplexer
 - No longer implied priority order
 - Clauses are required to be mutually exclusive
 - No redundant gates

architecture SSA of mux4 is
begin

 with sel select

 z <= in0 when "00",
 in1 when "01",
 in2 when "10",
 in3 when "11"
 'X' when others;

end SSA;

 


Inferring Logic from Processes and Variables

- Simple variable assignment statements generate combinational logic
- Sensitivity list is often ignored by synthesis compiler

```
entity syn_y is  
port ( x,y,z: in std_logic;  
       res: out std_logic);  
end entity syn_v;
```

 
```
architecture behav of syn_v is  
begin  
pr1: process (x,y)  
    variable v1,v2: std_logic;  
    begin  
        v1 := x and y;  
        v2 := v1 xor z;  
        res <= v1 nand v2;  
    end process;  
end behav;
```



If-then-else Statements

- Like conditional assignment statements, if-then-else statements will generate latches *unless every “output signal” of the statement is assigned a value each time the process executes*
 - (a) One branch of the if-then-else clause must always be taken AND
 - (b) All output signals are assigned values in each branch

 
```
architecture behav of syn_if is
begin
  pr1: process (x,y,z,sel)
    variable v1: std_logic;
    begin
      if sel='1' then
        v1 := x xor y;
        w <= v1 and z;
      end if;
    end process;
end behav;
```



Avoiding latches by “initialization”

- Can ensure that a signal is always assigned in an if-then-else clause by including a final else clause that assigns a default value to all “output signals” of the statement
- Another alternative is to **set a signal to a default value** before the if-then-else statement:
 
```
architecture behav of syn_if is
begin
pr1: process (x,y,z,sel)
    variable v1: std_logic;
    begin
        w <= '0';
        if sel='1' then
            v1 := x xor y;
            w <= v1 and z;
        end if;
    end process;
end behav;
```




Case Statement

- Case statement is ideally suited for implementing multiplexers
 - all clauses must be mutually exclusive
 - no implied priority between clauses (unlike if-then-else)
 - no redundant logic
- Need to obey same rules to avoid latches
 - (a) One branch of the case statement must always be true AND
 - (b) If a signal is assigned a value in one branch of a case statement, it must be assigned a value in all branches

4 input multiplexer
 
```
architecture behav of syn_mux is
begin
  pr1: process (in0,in1,in2,in3,sel)
  begin
    case sel is
      when "00" => z <= in0;
      when "01" => z <= in1;
      when "10" => z <= in2;
      when "11" => z <= in3;
    end case;
  end process;
end behav2;
```




Sequential Circuits

- Any moderately complex digital system requires the use of sequential circuits, e.g. to
 - identify and modify current state of system
 - store and hold data
 - identify sequences of inputs
 - generate sequences of outputs
- If and case statements and conditional signal assignments can be used to infer latches
- Latches are not preferred means of generating sequential circuits.
 - A latch is transparent when LE is high – can lead to unintended asynchronous sequential behavior when a result is fed back to an input
 - Latches are prone to generate race conditions
 - Circuits with latches are difficult to verify timing
 - Circuits with latches are difficult to test


Synchronous (Single Clock) Digital Design

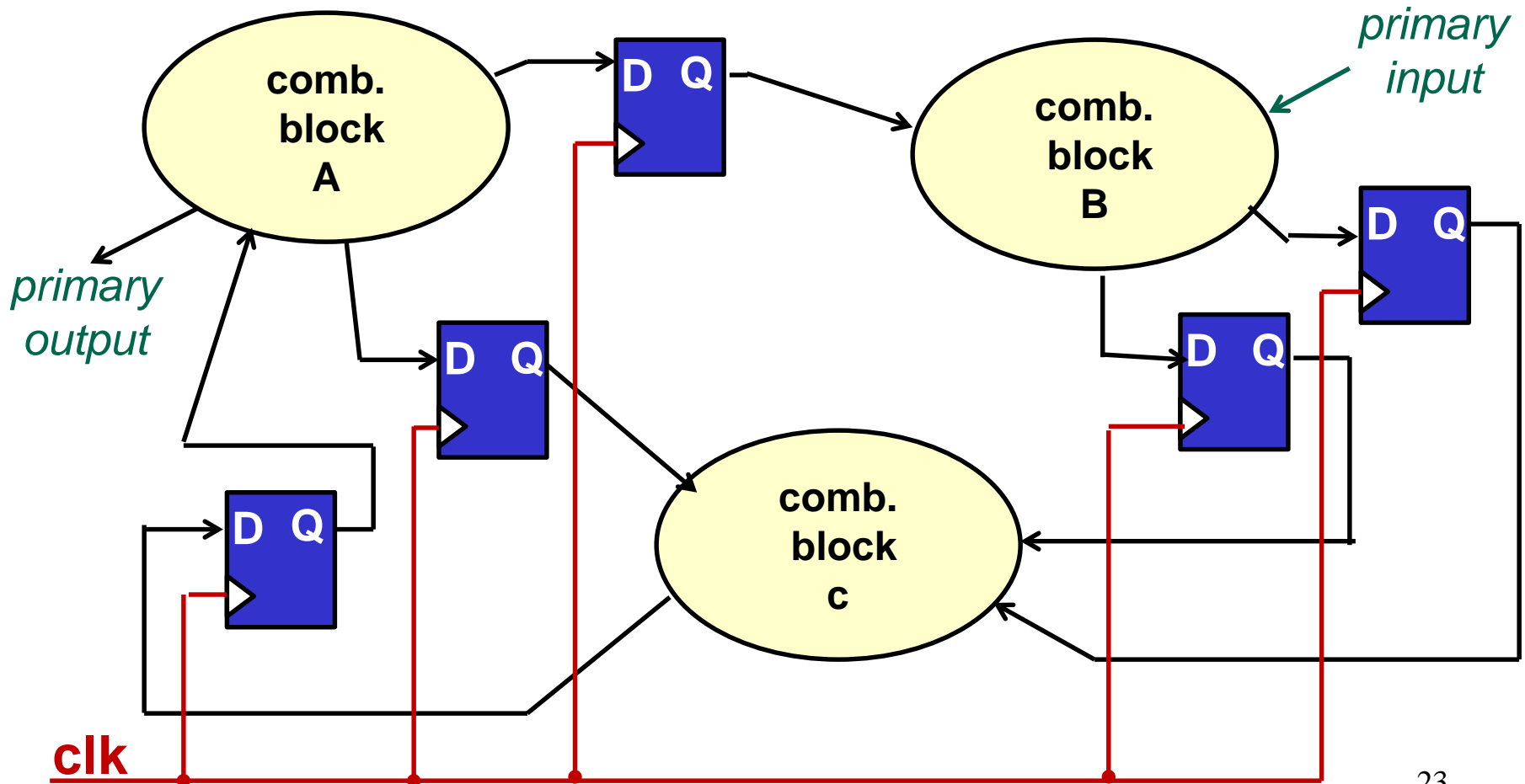- Preferred design style is combinational circuit modules connected via positive (negative) edge-triggered flip-flops that all use a common clock.




Finite State Machine

 - Single clock synchronous system can be modeled as a single combinational block and a multi-bit register



Advantages of single clock synchronous

- Edge triggered D flip-flops are never transparent
 - no unintended asynchronous sequential circuits
- Timing can be analyzed by:
 - determining all combinational delays
 - just add them up
 - checking flip-flop setup and hold times
- No race conditions
 - only time signal values matter is on clock edge
- Easy to test
- Most real systems cannot be designed using a single clock
 - different timing constraints on various I/O interfaces
 - clock delays across chip
 - goal is to make the single clock modules as large as possible²⁵

 


D Flip-flop

- Edge triggered D flip-flops are preferred sequential component
- Within a process, positive edge triggered operation is inferred using:

```
if rising_edge (clk) then  
  if clk'event and clk='1' then
```

- For example:
 
```
architecture RTL of FFS is  
begin  
  p0: process (clk)  
    begin  
      if rising_edge (clk) then  
        z <= a xor b;  
      end if;  
    end process;  
end RTL;
```



Inferring D Flip-flop with Asynchronous Reset

- Asynchronous reset takes precedence over clock
- Flip-flop can also include asynchronous set

architecture RTL of ARFF is

begin

p0: **process** (resn, clk)

begin

if resn='0' **then**

 z <= '0';


elsif rising_edge (clk) **then**

 z <= a xor b;

end if;

end process;


end RTL;

 

Inferring D Flip-flop with Synchronous Reset

- Synchronous reset waits for clock
- Flip-flop can also include synchronous set
 
```
architecture RTL of ARFF is
begin
p0: process (clk)
begin
    if rising_edge (clk) then
        if resn='0' then
            z <= '0';
        else
            z <= a xor b;
        end if;
    end if;
end process;
end RTL;
```




Example: 4-bit synchronous counter

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity count4 is
port( clk, reset: in std_logic;
      count: out std_logic_vector (3 downto 0));
end entity count4;

architecture RTL of count4 is
begin
p0: process (clk, reset)
variable vcount: std_logic_vector (3 downto 0);
begin
    if rising_edge (clk) then
        if reset='1' then
            vcount := "0000";
        else
            vcount := vcount+1;
        end if;
    end if;
    count <= vcount;
end process;
end RTL;
```

Example: 4-bit synchronous counter


 


Wait Statement

- Only one wait statement permitted per process
- Must be the first statement in the process
- Must be of the **wait until** form
 - cannot use **wait for** or **wait on** constructs
- Both of these will trigger execution on rising clock edge:
wait until clk'event **and** clk='1';
wait until rising_edge(clk); -- only with std_logic type
- A D flip-flop will be inferred for all signals assigned in the process
 - all signals are synchronously assigned in process

Wait Statement - Example
  
```
architecture RTL of ARFF is
begin
  p0: process
  begin
    wait until clock;
    if resn='0' then
      z <= '0';
    else
      z <= a xor b;
    end if;
  end process;
end RTL;
```



Loop Statements

- For loop is most commonly supported by synthesis compilers
- Iteration range should be known at compile time
- While statements are usually not supported because iteration range depends on a variable that may be data dependent.
- Compiler will unroll the loop, e.g.:

```
for k in 1 to 3 loop  
    shift_reg(n) <= shift_reg(n-1);  
end loop;
```

will be replaced by:


```
shift_reg(1) <= shift_reg(0);  
shift_reg(2) <= shift_reg(1);  
shift_reg(3) <= shift_reg(2);
```

Functions


- Since:
 - functions are executed in zero time and
 - functions do not remember local variable values between calls
- Functions will typically infer combinational logic
- Function call is essentially replaced by in-line code

```
function parity (data: std_logic_vector)
  return std_logic is
  variable par: std_logic := '0';
begin
    for i in data'range loop
      par := par xor data(i);
    end loop;
    return (par);
end function parity;
```
 
```
signal a: std_logic_vector (3 downto 0);
begin
  z <= parity (a);
```



↓ *optimized*

 


Procedures

- Like functions, procedures do not remember local variable values between calls
- Procedures, however, do not necessarily execute in zero time
- And procedures may assign new events to signals in parameter list
- Like function, think of procedure calls as substituting the procedure as inline code in the calling process or architecture
- Can include a **wait** statement, but then cannot be called from a process
 - Generally avoid wait statements in a procedure
 - Synchronous behavior can be inferred using if-then-else
- If procedure is called from a process with **wait** statement, flip-flops will be inferred for all signals assigned in procedure

Tri-state Gates

 - A tri-state gate is inferred if the output value is conditionally set to **high impedance Z**



din	en	dout
0	1	0
1	1	1
X	0	Z

Examples of Tri-state Gates

architecture RTL of STATE3 is

begin

seq0 : process (Din, EN)

begin

if (EN = '1') then

Dout(0) <= Din(0) xor Din(1);

else DOUT(0) <= 'Z';

end if;

end process;

seq1 : process (EN, Din)

begin

case EN is

when '1' => Dout(1) <= Din(2) nor Din(3);

when others => Dout(1) <= 'Z';

end case;

end process;


Dout(2) <= Din(1) nand Din(2) when EN = '1' else 'Z';

with EN select

Dout(3) <= Din (3) when '1',


'Z' when others;

end RTL;

 

Finite State Machines

Structure of Typical Digital System

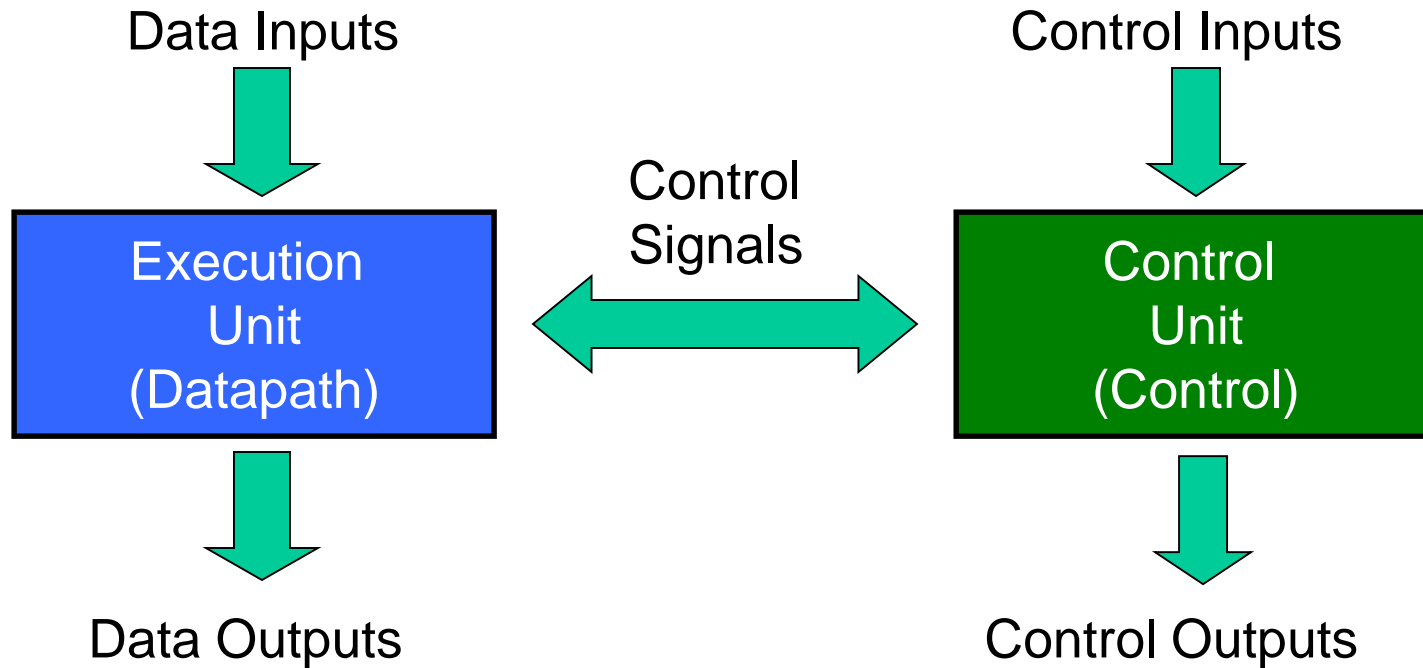

Provides necessary resources & interconnect to perform specified task e.g.:


Adders, Multipliers, Shifters, Registers, Memories, etc.

Controls data movement and operation of execution unit. Usually follows some “program” or “sequence”.

Often implemented as one or more Finite State Machine(s)


Finite State Machine

 - Single clock synchronous system can be modeled as a single combinational block and a multi-bit register




- Values stored in registers are **state** of the system
- Number of **states** is finite ($\leq 2^n$)
- State** may change as a function of inputs
- Outputs are function of **state** and inputs

General Architecture of FSM

 


- **Next state** (nx_state) is a function of **present state** (pr_state) and inputs
- Output is a function of pr_state. May also be a function of inputs
- Reset allows system to be set to a known state

Mealy Machine

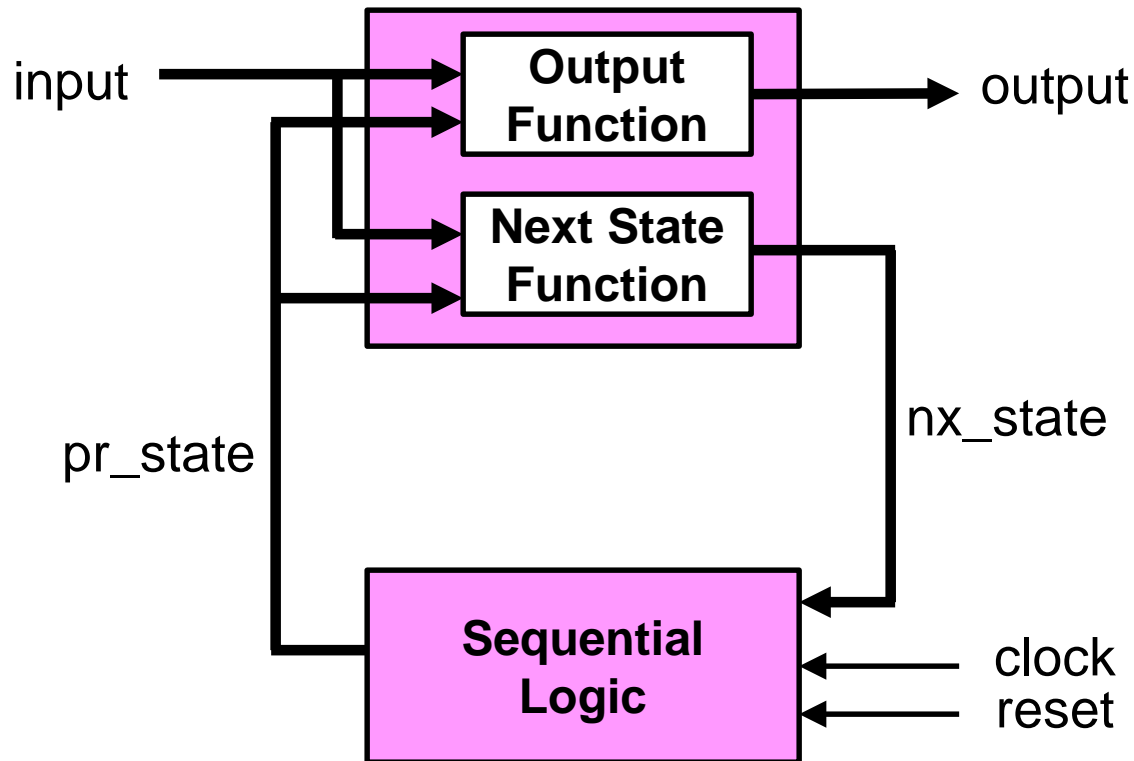

- Output is a function of **pr_state** *and* inputs
- Fast response (input -> output) – no FF's in way
- Leads to a fewer number of states
- Propagates asynchronous behavior (e.g. glitches) from input to output


Moore Machine

 

- Output is a function of *pr_state only*
- Slower response: (input -> output) requires clock transition
- Usually requires more states
- Operation is fully synchronous

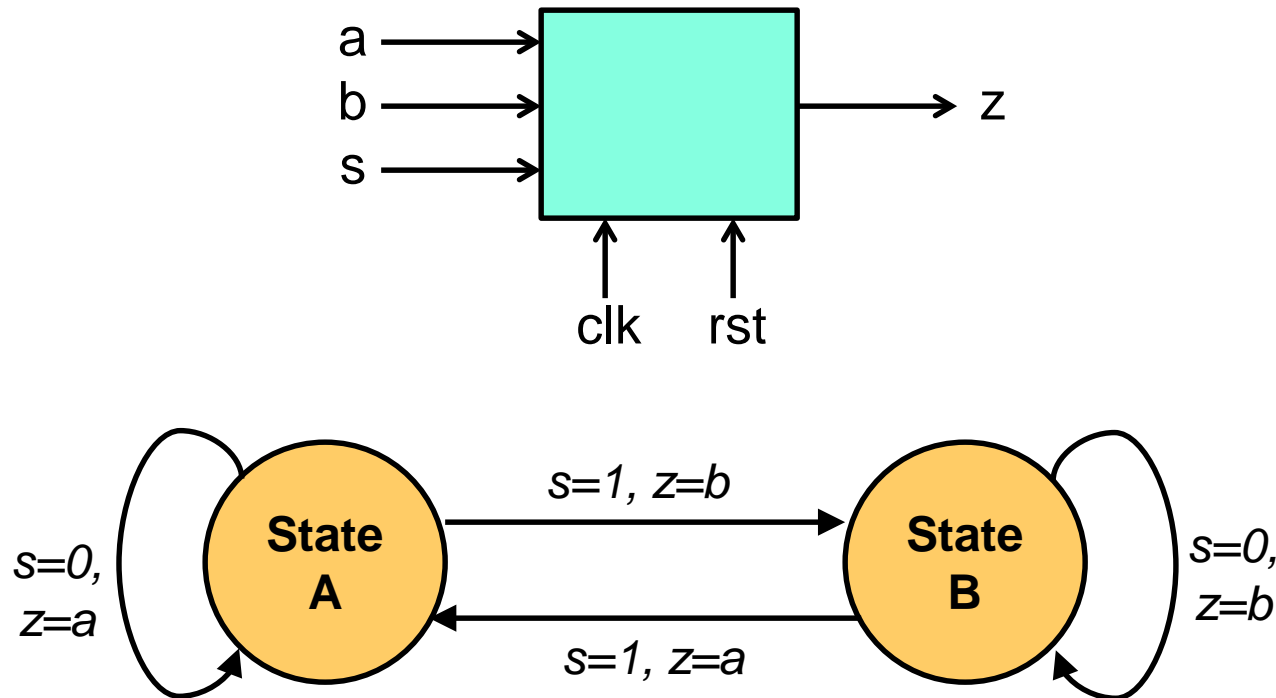
Example: Toggle Multiplexer

- Design a synchronous multiplexer that selects between two 1-bit inputs a and b . The multiplexer switches from one input to the other whenever a third input s is set to '1'



- This is a Mealy machine

Example: As a Moore Machine

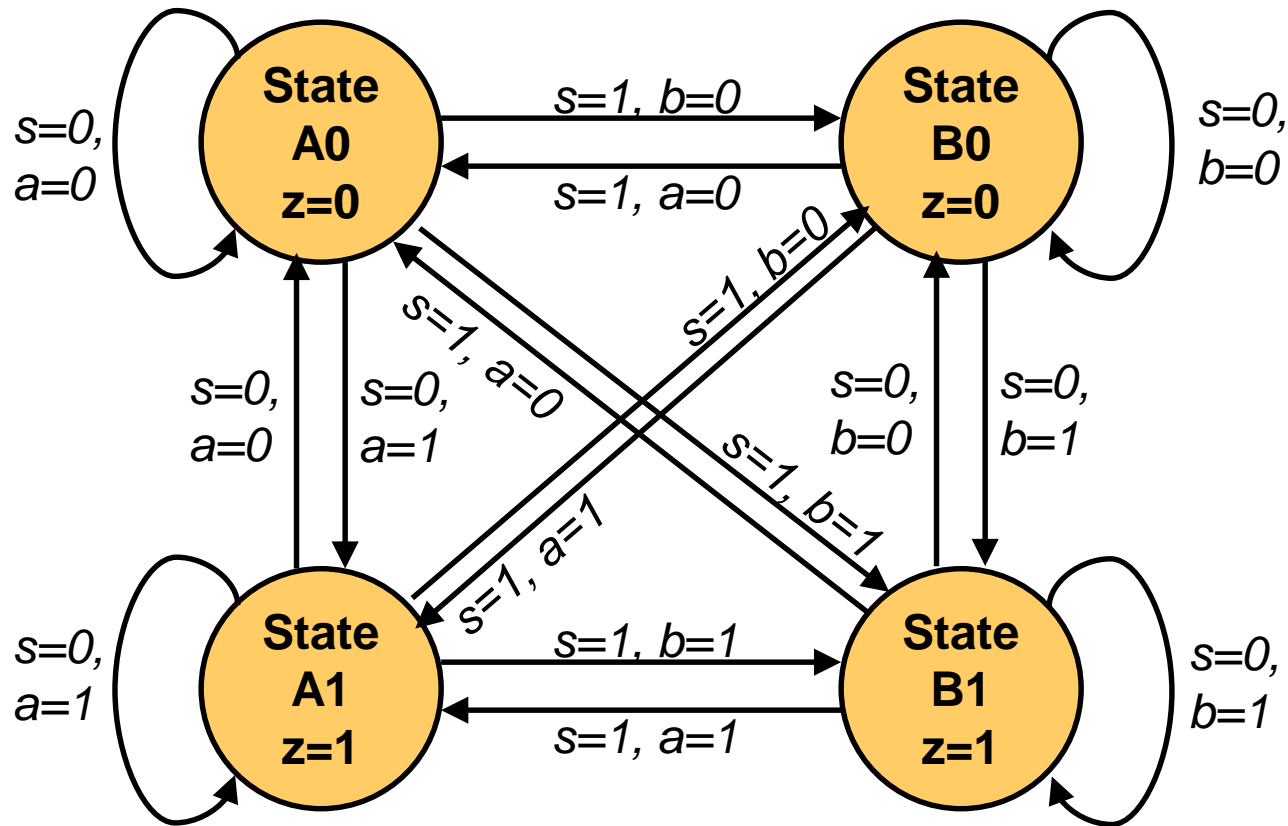


- This is a Moore machine

Toggle Multiplexer as Mealy Machine

- General approach is to model FSM as two communicating concurrent processes

 
- Combinational process
- Edge triggered clock process



```
library ieee;  
use ieee.std_logic_1164.all;
```



```
entity tmpx is  
  port(a,b,s,clk,rst: in std_logic;  
        z: out std_logic);  
end entity tmpx;
```
 
```
architecture mealy of tmpx is  
  type state is (stateA, stateB);  
  signal pr_state, nx_state : state;  
begin
```





Clock Process
 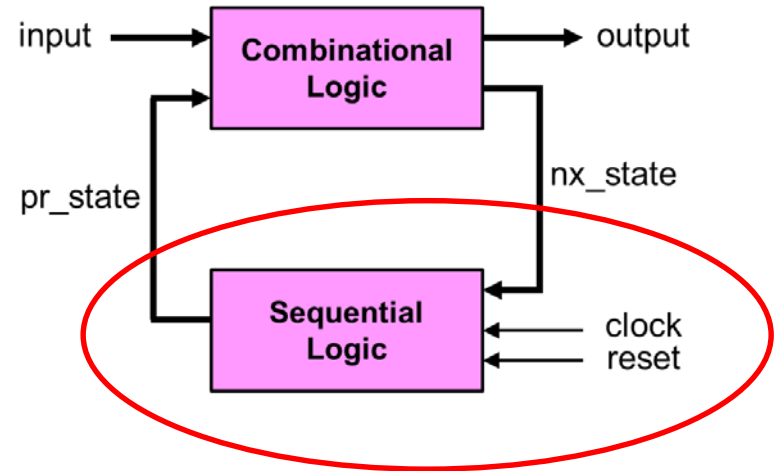
```
p_clk: process (rst, clk)
begin
  if (rst = '1') then
    pr_state <= stateA;
  elsif (clk'event and clk = '1') then
    pr_state <= nx_state;
  end if;
end process;
```



Combinational Process uses Case Statement
  
```
p_comb: process (a, b, s, pr_state)
begin
  case pr_state is
    when stateA =>
      z <= a;
      if (s = '1') then nx_state <= stateB;
        else nx_state <= stateA;
      end if;
    when stateB =>
      z <= b;
      if (s = '1') then nx_state <= stateA;
        else nx_state <= stateB;
      end if;
    end case;
  end process;
end architecture mealy;
```



- Make sure all signals are assigned in all branches of case statement to avoid inferring latches

Moore Machine Implementation

architecture moore of tmpx is
type state is (A0, A1, B0, B1);
signal pr_state, nx_state: state;

begin

p0: **process** (rst, clk)

if (rst = '1') **then**



 pr_state := A0;

elsif (clk'event **and** clk = '1') **then**

 pr_state <= nx_state;

end if;

end process;

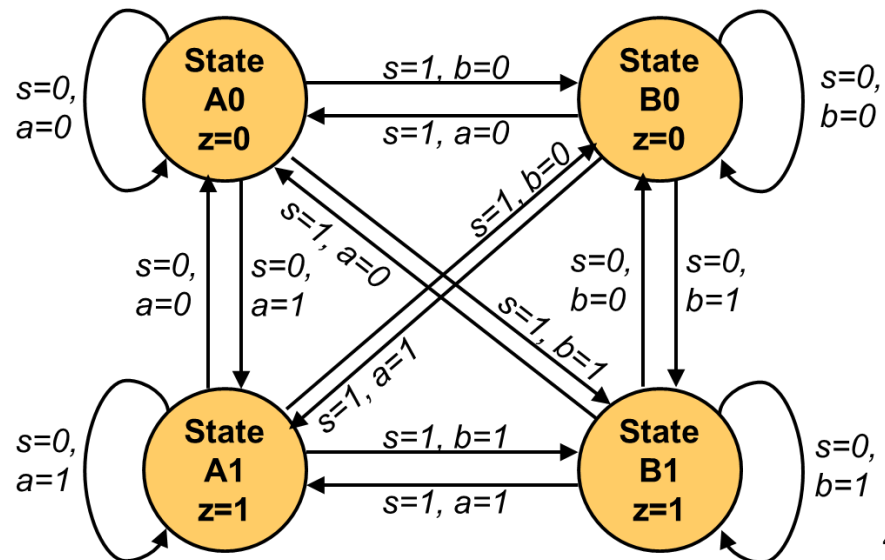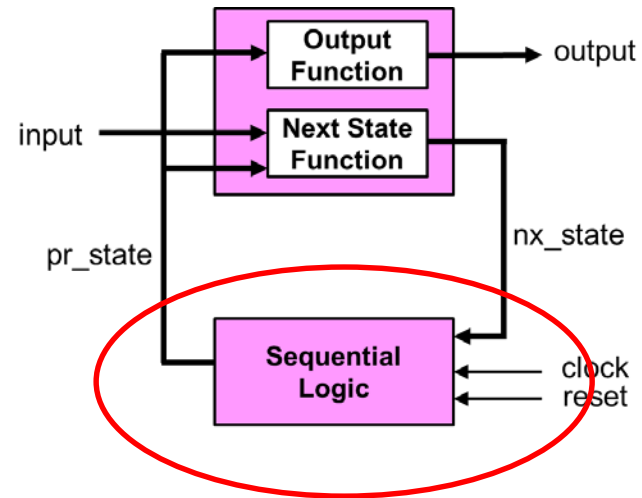

Moore Machine Implementation (2)

p_comb: **process** (a, b, s, pr_state)

begin

case pr_state **is**

when A0 =>

z<='0';

if s='0' **and** a='1' **then** nx_state<=A1;

elsif s='1' **and** b='0' **then** nx_state<= B0;

elsif s='1' **and** b='1' **then** nx_state<= B1;

else nx_state<=A0;

end if;

when A1 =>

z<='1';



if s='0' **and** a='0' **then** nx_state<=A0;

elsif s='1' **and** b='0' **then** nx_state<= B0;

elsif s='1' **and** b='1' **then** nx_state<= B1;

else nx_state<=A1;



end if;

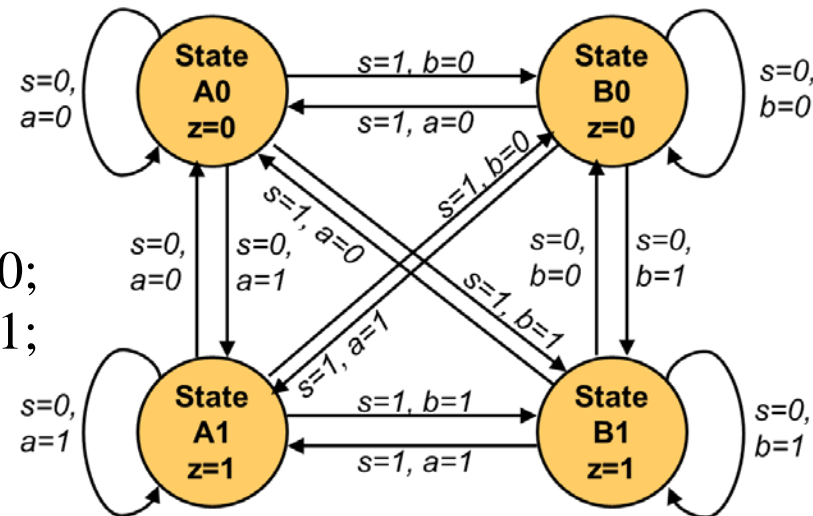 

Moore Machine Implementation (3)


```

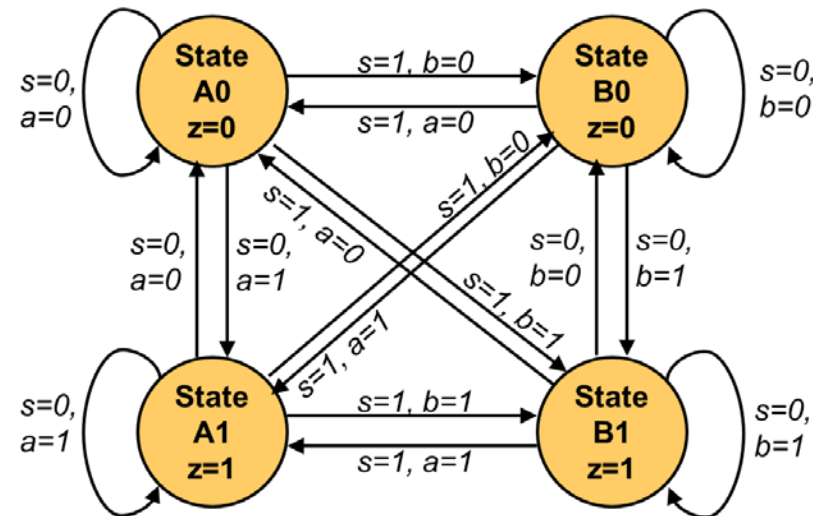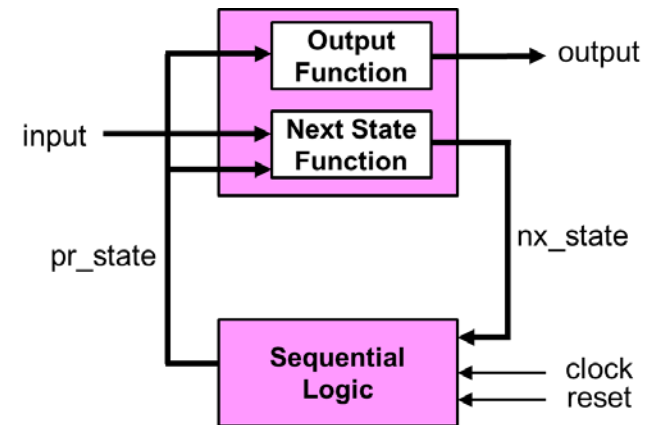when B0 =>
  z<='0';
  if s='0' and b='1' then nx_state<=B1;
  elsif s='1' and a='0' then nx_state<=A0;
  elsif s='1' and a='1' then nx_state<=A1;
  else nx_state<=B0;
  end if;
when B1 =>
  z<='1';
  if s='0' and b='0' then nx_state<=B0;
  elsif s='1' and a='0' then nx_state<=A0;
  elsif s='1' and a='1' then nx_state<=A1;
  else nx_state<=B1;
  end if;
end case;
end process;
end moore;
  
```



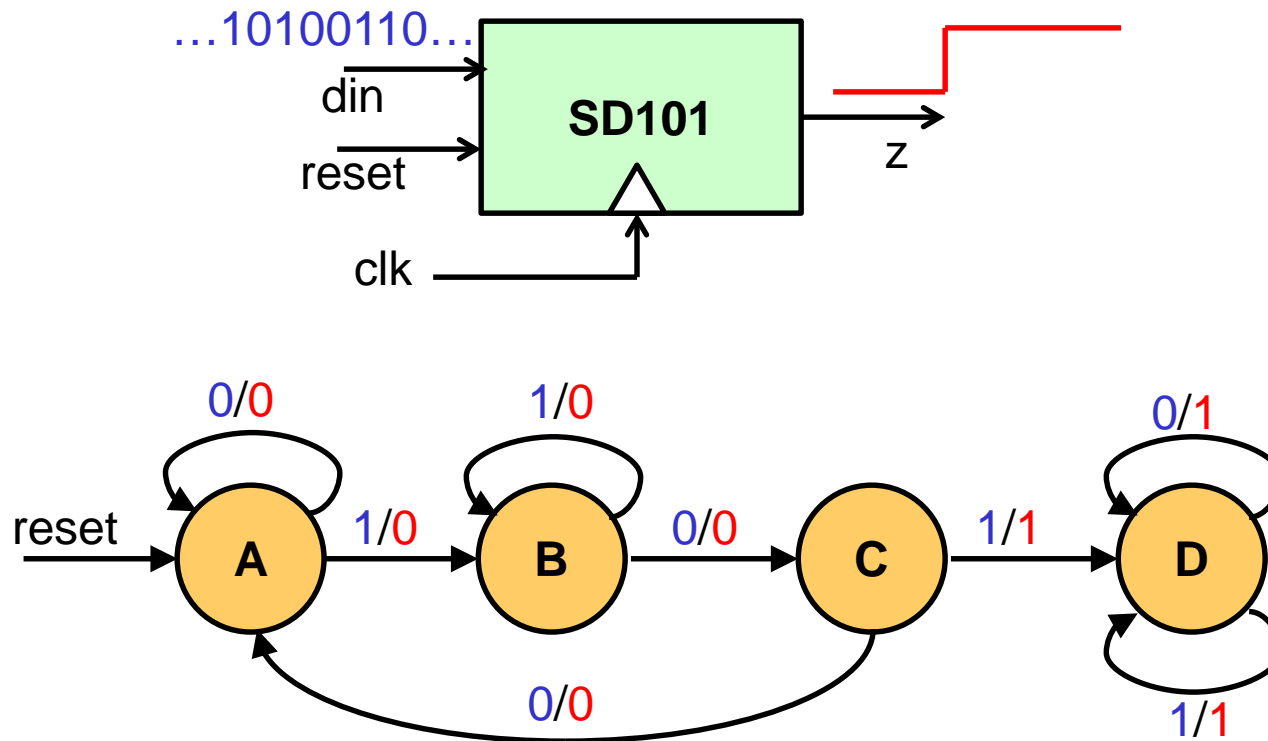Example: Sequence Detection

Build a Mealy FSM that has looks for sequence “101” in a serial input stream. When it detects the sequence, it outputs a 1 and holds that value until the machine is reset.




Sequence Detection: Clock Process

```
library ieee;
use ieee.std_logic_1164.all;

entity SD101 is
    port(din, reset, clk: in std_logic;
          z: out std_logic);
end entity SD101;

 architecture mealy of SD101 is
    type state is (stateA, stateB, stateC, stateD);
    signal pr_state, nx_state : state;
begin
    p_clk: process (rst, clk)
    begin
        if (reset = '1') then
            pr_state <= stateA;
        elsif (clk'event and clk = '1') then
            pr_state <= nx_state;
        end if;
    end process;
end architecture;
```



Sequence Detection: Combinational Process

```
p_comb: process (din, pr_state)
```

```
begin
```

```
  case pr_state is
```

```
    when stateA =>
```

```
      z <= '0';
```

```
      if (din = '1') then nx_state <= stateB;
```

```
      else nx_state <= stateA;
```

```
      end if;
```

```
    when stateB =>
```

```
      z <= '0';
```

```
      if (din = '1') then nx_state <= stateB;
```

```
      else nx_state <= stateC;
```

```
      end if;
```

```
    when stateC =>
```

```
      if (din = '1') then z <= '1';
```

```
      nx_state <= stateD;
```

```
      else z <= '0';
```

```
      nx_state <= stateA;
```

```
      end if;
```


```
    when stateD =>
```

```
      z <= '1';
```

```
      nx_state <= stateD;
```


```
  end case;
```

```
end process;
```

 

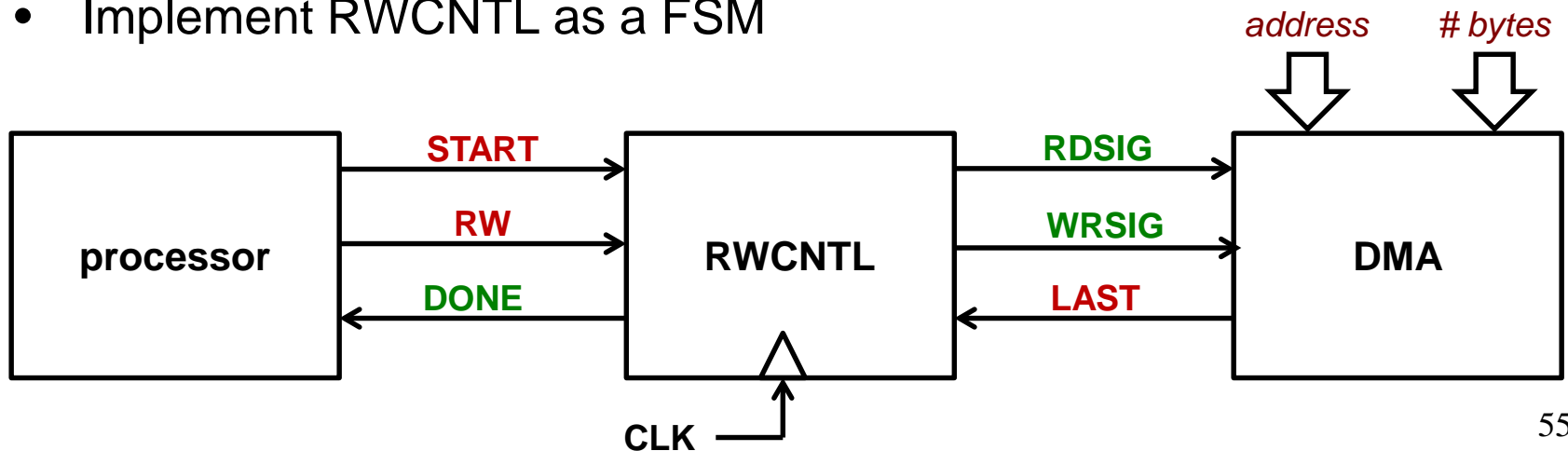Example: Read-Write Controller



- Suppose we have a read-write controller RWCNTL that acts as an interface between a processor and a DMA unit.
 - The DMA unit is used to transfer blocks of data between the processors memory and an external storage device like a hard disk.
 - Assume the processor has already communicated the memory address and byte count information to the DMA unit (this is part of the “data path”)
- Operation:
 - Processor raises start signal with $RW=1$ for reading, $RW=0$ for writing
 - RWCNTL sets (and holds) RDSIG or WRSIG to enable data transfer
 - When transfer is complete, DMA raises signal LAST
 - RWCNTL then resets RDSIG/WRSIG and raises DONE flag
- Implement RWCNTL as a FSM



 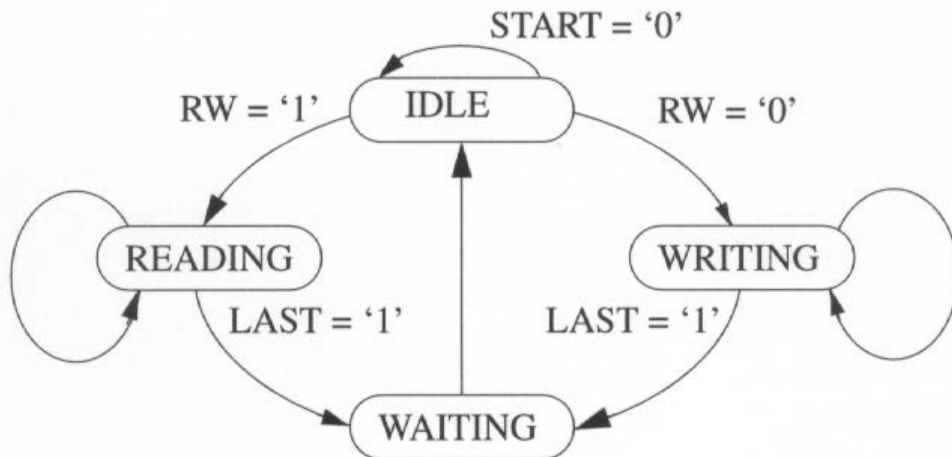Example: Read-Write Controller

Specifications: RWCNTL starts at state **IDLE**, waiting for input signal **START** to go to '1' and then changes to either state **READING** or state **WRITING** depending on the value of **RW** input. States **READING** and **WRITING** persist until input signal **LAST** goes to '1' which changes state to **WAITING**. After one clock cycle, state **WAITING** always goes to state **IDLE**.

The FSM has three outputs **RDSIG**, **WRSIG**, and **DONE**. They are '1' when they are in state **READING**, **WRITING**, and **WAITING**, respectively, otherwise they are '0'.



RWCNTL: Clock Process

entity RWCNTL is

port(

CLK : **in** std_logic;

START : **in** std_logic;

RW : **in** std_logic;

LAST : **in** std_logic;

RDSIG : **out** std_logic;

WRSIG : **out** std_logic;

DONE : **out** std_logic);

end entity RWCNTL;

architecture RTL of RWCNTL is

type STATE is (IDLE, READING,
WRITING, WAITING);

signal PR_STATE, NX_STATE: STATE;

begin

seq : **process**


begin

wait until CLK'event and CLOCK = '1';

PR_STATE <= NX_STATE;

end process;

end RTL;

 

RWCNTL: Combinational Process

comb : process (PR_STATE, START, RW, LAST)

begin

DONE <= '0'; RDSIG <= '0'; WRSIG <= '0';

case PR_STATE is

when IDLE =>

if START = '0' then

NX_STATE <= IDLE;

elsif RW = '1' then

NX_STATE <= READING;

else

NX_STATE <= WRITING;

end if;

when READING =>

RDSIG <= '1';


if LAST = '0' then

NX_STATE <= READING;


else

NX_STATE <= WAITING;

end if;

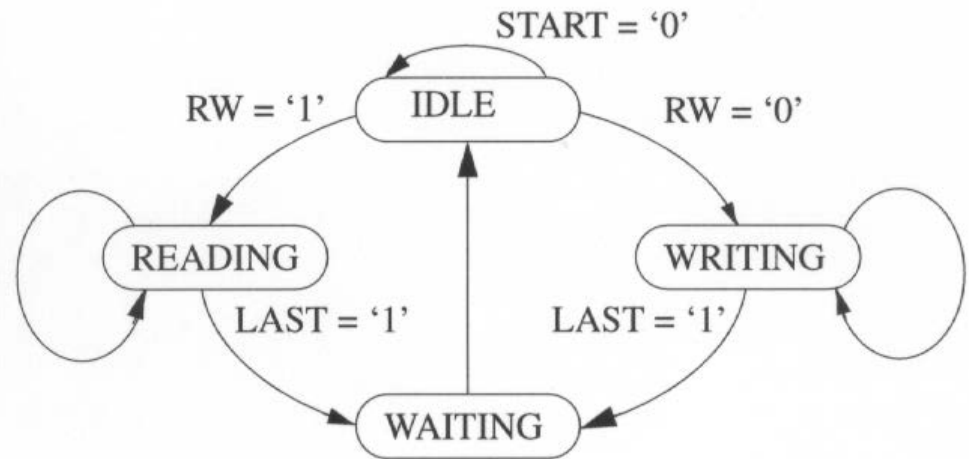


RWCNTL: Combinational Process (2)

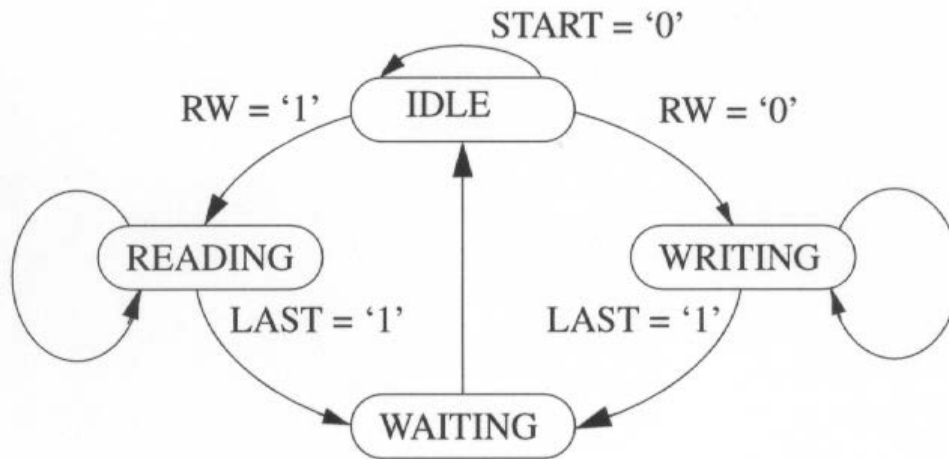


```
when WRITING =>
  WRSIG <= '1';
  if LAST = '0' then
    NX_STATE <= WRITING;
  else
    NX_STATE <= WAITING;
  end if;
when WAITING =>
  DONE <= '1';
  NX_STATE <= IDLE;
end case;
end process;
```

Simulation Waveforms

 


Synthesized RWCNTL

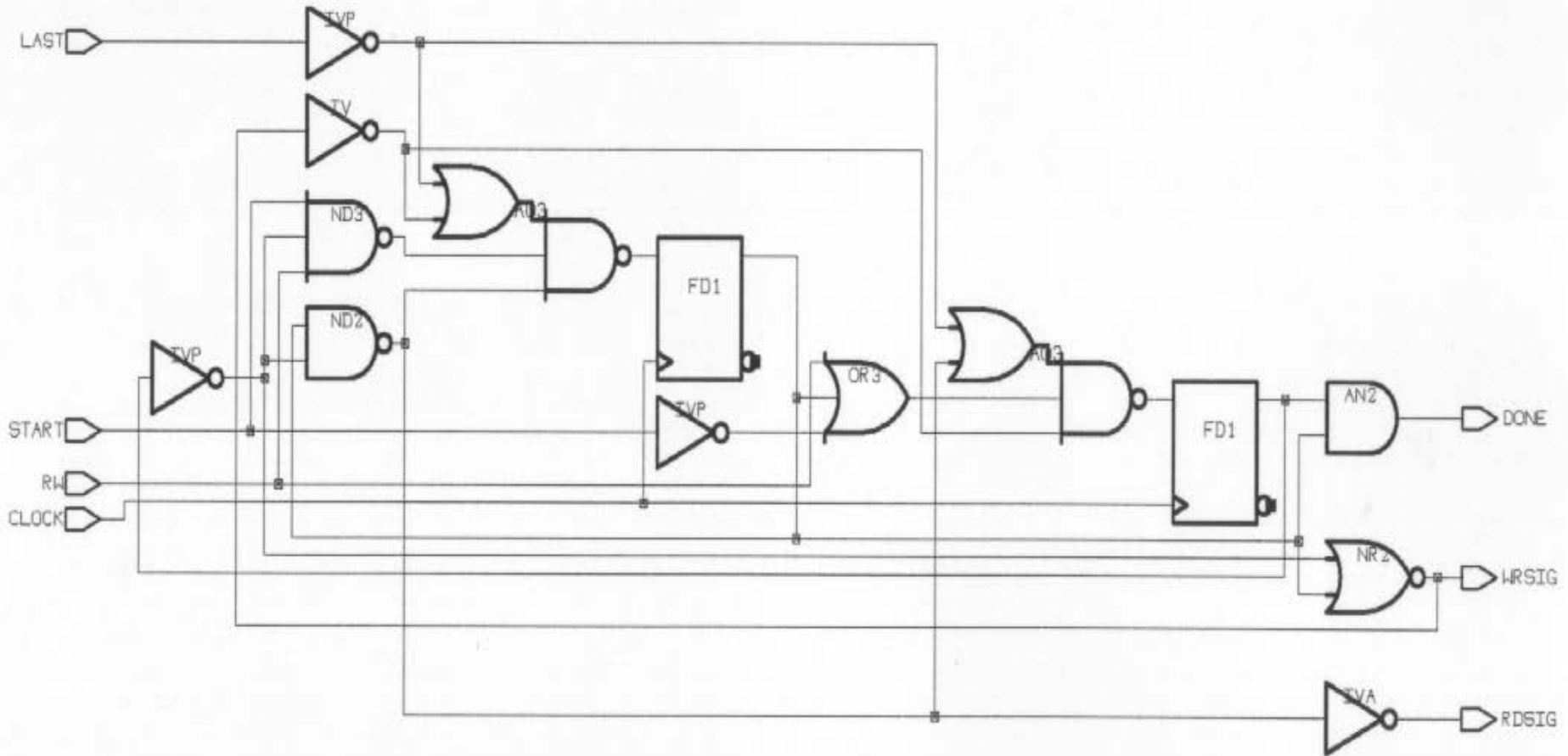


RWCNTL: Add Asynchronous Reset
 
```
seq : process
begin
  if (RESETn = '0') then
    PR_STATE <= IDLE;
  elsif (CLOCK'event and CLOCK = '1') then
    PR_STATE <= NX_STATE;
  end if;
end process;
end RTL;
```





Synthesized RWCNTL with Asynch. Reset

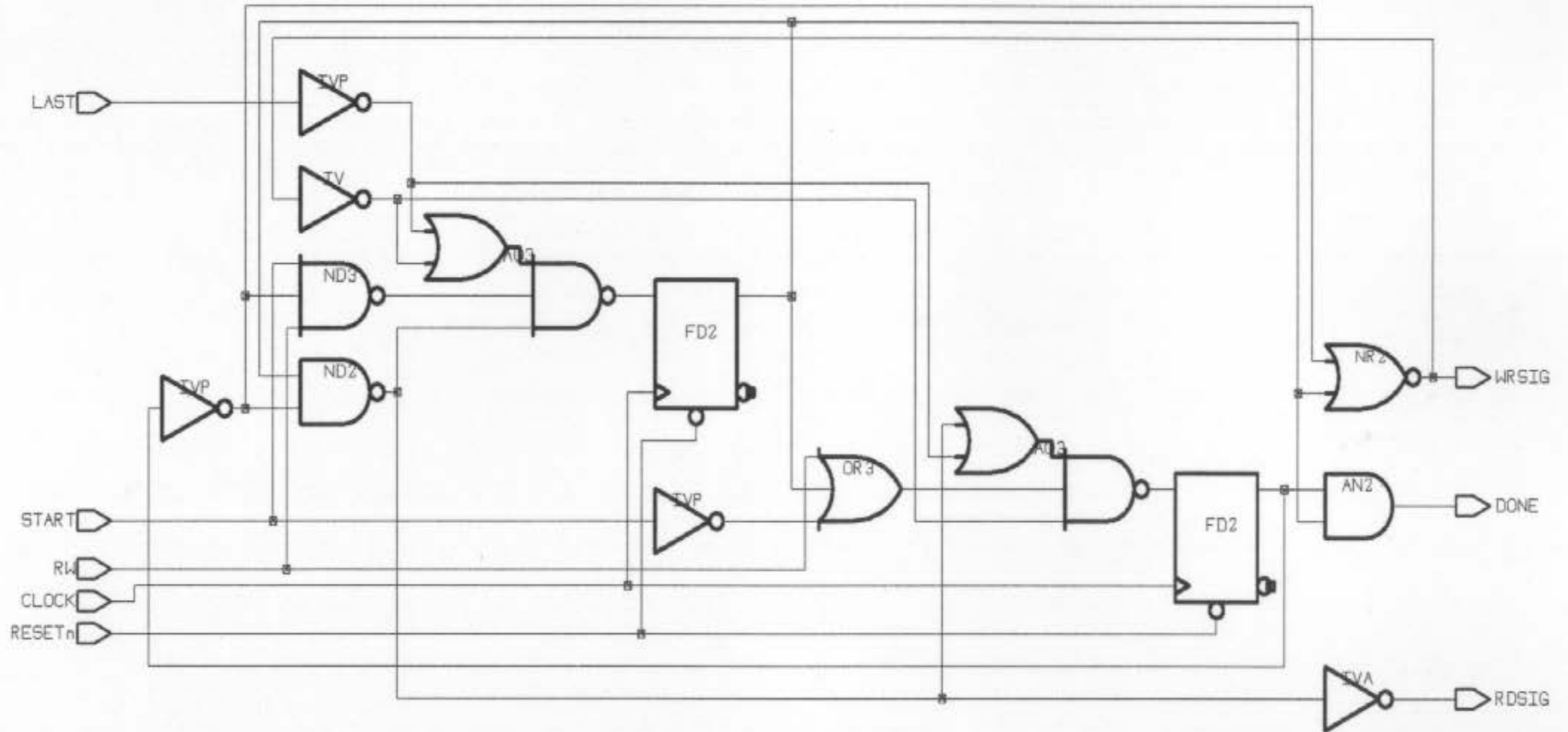


Test Bench Design

Testing Digital Circuits

  - In our class examples, circuits were limited to a few input & outputs
 - Easy to set up test bench with processes to explicitly drive the inputs
 - Look at output waveforms to check correct operation



But how do we
test this one?

 

*Processor for
SONY PlayStation 3*

Test Vectors

- For large complex designs, designers will set up a suite of test vectors
 - One or more files that contain a sequence of inputs and expected outputs

<i>inputs</i>	<i>expected outputs</i>
0010011100000110	11xx010110
1101001101100101	11x0111010
0100011010011010	1101101110
1110011111010100	0110001110

- Input vectors are typically applied to circuit under test at some regular clock rate. Outputs are read at same rate and compared to expected outputs
- It can take many millions of vectors to adequately test a complex chip e.g., a microprocessor

Design Verification vs. Product Testing

- During the design process, we develop **functional test vectors**
 - Apply vectors similar to what might be expected in normal operation of chip
 - Look for correct functionality across broad range of expected inputs
 - Purpose of these **functional vectors** is to **debug the design**
 - Each time design is refined, we reapply the functional vectors to check that no mistake has been made in moving from behavioral modeling to implementation
- Once design has been synthesized into gates, and checked once more using the functional vectors, we develop a new set of **manufacturing test vectors**
 - Now checking for **manufacturing defects**

Testing for Manufacturing Defects


- Popular approach is to assume that all manufacturing faults can be modeled as a single node being **stuck-at** either a '0' or a '1'
- Ideally, develop a set of test vectors that would show an error if any node is stuck-at '0' or '1'
 - Not practical as it would take too many vectors to exhaustively test for all stuck at faults – tradeoff between test time and cost of sending bad chips into the field
 - Ratio of tested faults to all possible stuck-at faults is known as **fault coverage** – 90% is considered good for a large, complex chip

Production chip tester.



Developing a Test Bench

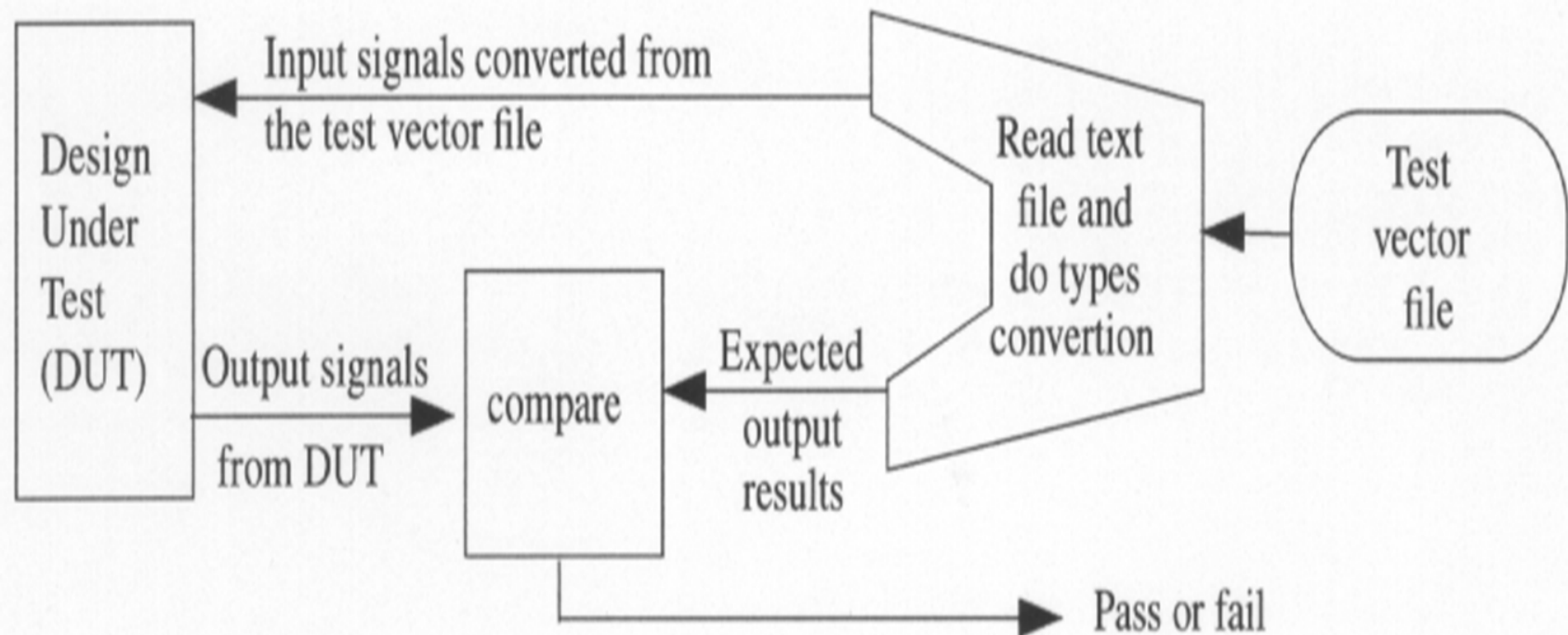- Develop a set of test benches using simple example: full adder
- Move towards fully automated model:




Device Under Test: Full-Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fadder is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          cin : in  STD_LOGIC;
          sum : out STD_LOGIC;
          cout : out STD_LOGIC);
end fadder;

architecture gates of fadder is
    signal S1,S2,S3: std_logic;
begin
    S1 <= A xor B after 5 ns;
    S2 <= cin and S1 after 3 ns;
    S3 <= A and B after 3 ns;
    sum <= S1 xor cin after 5ns;
    cout <= S2 or S3 after 3 ns;
end gates;
```

 

TB1: A Simple Test Bench

```
ENTITY fadd_tb1 IS
END fadd_tb1;

ARCHITECTURE behavior OF fadd_tb1 IS
    -- Component Declaration for UUT
    COMPONENT fadder
    PORT (
        A : IN  std_logic;
        B : IN  std_logic;
        cin : IN  std_logic;
        sum : OUT std_logic;
        cout : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic := '0';
    signal B : std_logic := '0';
    signal cin : std_logic := '0';

    --Outputs
    signal sum : std_logic;
    signal cout : std_logic;

BEGIN
    -- Instantiate the UUT
    uut: fadder PORT MAP (
        A => A,
        B => B,
        cin => cin,
        sum => sum,
        cout => cout
    );
```

```
TB: process
    constant PERIOD: time:= 20ns;
    BEGIN

        A<='0'; B<='0'; cin<='0';
        wait for PERIOD;

        A<='0'; B<='1'; cin<='0';
        wait for PERIOD;

        A<='1'; B<='0'; cin<='0';
        wait for PERIOD;

        A<='1'; B<='1'; cin<='0';
        wait for PERIOD;

        A<='0'; B<='0'; cin<='1';
        wait for PERIOD;


        A<='0'; B<='1'; cin<='1';
        wait for PERIOD;

        A<='1'; B<='0'; cin<='1';
        wait for PERIOD;

        A<='1'; B<='1'; cin<='1';
        wait for PERIOD;

        wait; -- will wait forever
    END process;
END;
```

TB1: Visually Check Simulation Result

 

This is a Lite version of ISim.

Time resolution is 1 ps

Simulator is doing circuit initialization process.

Finished circuit initialization process.

ISim>

Assert Statement (revisited)

assert *boolean-expression*

[**report** *string-expression*]

[**severity** *expression*];

- The *boolean-expression* is evaluated and if the expression is false, the *string-expression* specified in report statement is displayed in the simulator window
- The severity statement then indicates to the simulator what action should be taken in response to the assertion failure.
- Severity: NOTE, WARNING, ERROR, FAILURE.

TB2: Using Assert Statement

TB: process

constant PERIOD: time:= 20ns;

BEGIN

```
A<='0'; B<='0'; cin<='0';
wait for PERIOD;
assert(sum='0' and cout='0')
    report "Test FAILED" severity error;
```

```
A<='0'; B<='1'; cin<='0';
wait for PERIOD;
assert(sum='1' and cout='0')
    report "Test FAILED" severity error;
```

```
A<='1'; B<='0'; cin<='0';
wait for PERIOD;
assert(sum='1' and cout='0')|
    report "Test FAILED" severity error;
```

```
A<='1'; B<='1'; cin<='0';
wait for PERIOD;
assert(sum='0' and cout='1')
    report "Test FAILED" severity error;
```

```
A<='1'; B<='1'; cin<='0';
wait for PERIOD;
assert(sum='0' and cout='1')
    report "Test FAILED" severity error;
```

```
A<='0'; B<='0'; cin<='1';
wait for PERIOD;
assert(sum='1' and cout='0')
    report "Test FAILED" severity error;
```

```
A<='0'; B<='1'; cin<='1';
wait for PERIOD;
assert(sum='0' and cout='1')
    report "Test FAILED" severity error;
```

```
A<='1'; B<='0'; cin<='1';
wait for PERIOD;
assert(sum='0' and cout='1')
    report "Test FAILED" severity error;
```


```
A<='1'; B<='1'; cin<='1';
wait for PERIOD;
assert(sum='1' and cout='1')
    report "Test FAILED" severity error;
```

wait; -- will wait forever

END process;

END;

TB2: Using Assert – no errors

 

This is a Lite version of ISim.

Time resolution is 1 ps

Simulator is doing circuit initialization process.


Finished circuit initialization process.

ISim>

TB2: Using Assert – Introduce error

```
architecture gates of fadder is
  signal S1,S2,S3: std_logic;
begin
  S1 <= A xor B after 5 ns;
  S2 <= cin and S1 after 3 ns;
  S3 <= A and B after 3 ns;
  sum <= S1 or cin after 5ns;
  cout <= S2 or S3 after 3 ns;
end gates;
```

*Use **or** instead of **xor***

 

This is a Lite version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.

at 120 ns: Error: Test FAILED
at 140 ns: Error: Test FAILED

ISim> |

TB3: Using Test Vector Array


```
ARCHITECTURE behavior OF fadd_tb3 IS
    -- Component Declaration for UUT
    COMPONENT fadder
    PORT (
        A,B,cin : IN  std_logic;
        sum,cout : OUT std_logic
    );
    END COMPONENT;
--Inputs
signal A : std_logic := '0';
signal B : std_logic := '0';
signal cin : std_logic := '0';
--Outputs
signal sum : std_logic;
signal cout : std_logic;
```

```
type test_array is array(integer range<>)
    of std_logic_vector(0 to 4);
constant test_vector: test_array(0 to 7):=(
    ('0', '0', '0', '0', '0'),
    ('0', '0', '1', '1', '0'),
    ('0', '1', '0', '1', '0'),
    ('0', '1', '1', '0', '1'),
    ('1', '0', '0', '1', '0'),
    ('1', '0', '1', '0', '1'),
    ('1', '1', '0', '0', '1'),
    ('1', '1', '1', '1', '1')
);
```

```
BEGIN
    -- Instantiate the UUT
    uut: fadder PORT MAP (
        A => A,
        B => B,
        cin => cin,
        sum => sum,
        cout => cout
    );
TB: process
    constant PERIOD: time:= 20ns;
    variable testv: std_logic_vector(0 to 4);
    BEGIN
        for i in test_vector'range loop
            testv := test_vector(i);
            A <= testv(0);
            B <= testv(1);
            cin <= testv(2);
            wait for PERIOD;
            assert (sum=testv(3) and cout=testv(4))
                report "Test FAILED" severity error;
            end loop;

            wait; -- will wait forever
        END process;
    END;
```

TB3: Using Test Vector Array – no errors

 

run 1000 ns
Simulator is doing circuit initialization process.
Finished circuit initialization process.
ISim>

Reading and Writing Files – TEXTIO Package

- A **file** is a class of object in VHDL (like signal, variable & constant). Each file has a **type**.
- The standard VHDL library contains the **TEXTIO** package which provides a set of file types, data types and I/O procedures for simple text I/O to and from **files**
- To make the package visible:

```
use std.textio.all;
```
- TEXTIO read and write procedures are available for predefined types **bit**, **bit_vector**, **character** and **string**
- The **ieee.std_logic_textio** package overloads these procedures to support **std_logic** and **std_logic_vector**

Declaring and Opening Files

- New Types:

text -- a file of character strings

line – a string (to or from a text file)

- Example Declarations

file testfile: text; -- testfile is “file handle”

variable L: line; -- L is a single line buffer

- Procedure to open a file:

`file_open(file_handle, filename, open_kind);`

- where *open_kind* is one of (`read_mode`, `write_mode` or `append_mode`), for example:

`file_open (testfile, “my_file.txt”, read_mode);`

Reading Files

- `readline (file_handle, line_buffer);`
 - Read one line from "text" file *file_handle* into *line_buffer*
- `read(line_buffer, value);`
 - Read one item from *line_buffer* into variable *value*.
 - Variable *value* can be bit, bit_vector, character or string
 - Variable can also be std_logic or std_logic vector if IEEE `std_logic_textio` package is used.
- `endfile(file_handle);` --returns boolean (TRUE if at EOF)
- For example:

```
variable buf_in: line;  
variable bit0: std_logic;  
begin  
    readline(my_file, buf_in);  
    read(buf_in, bit0);
```


Writing Files

- `writeline (file_handle, line_buffer);`
 - Write one line to "text" file *file_handle* from *line_buffer*
- `write(line_buffer, value);`
 - Write variable value into *line_buffer*
 - Variable *value* can be bit, bit_vector, character or string
 - Variable can also be std_logic or std_logic vector if IEEE `std_logic_textio` package is used.
- For example:

```
variable buf_out: line;  
variable abc : bit_vector (3 downto 0);  
begin  
    write(buf_out, "abc is");  
    write(buf_out, abc);  
    writeline(my_file, buf_in);
```

TB4: Reading Vectors from File
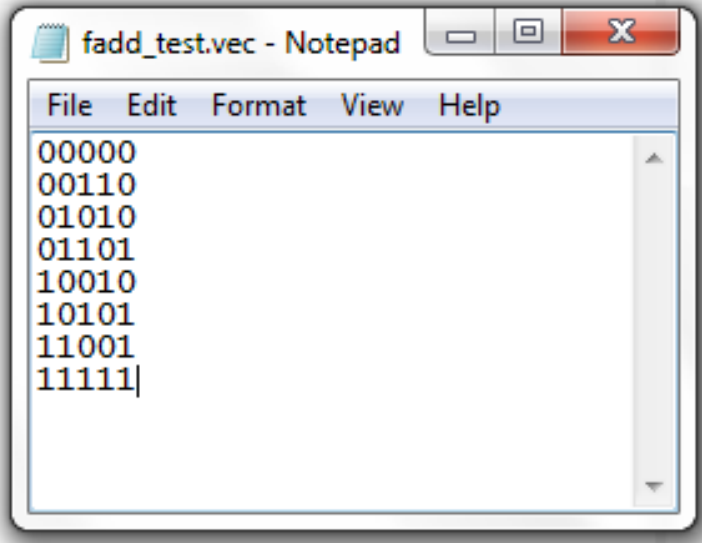
```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE std.textio.all;  
USE ieee.std_logic_textio.ALL;
```



```
TB: process  
    constant PERIOD: time:= 20ns;  
    file vec_file: text;  
    variable buf_in: line;  
    variable testv: std_logic_vector(0 to 4);  
    BEGIN  
  
        file_open(vec_file,"fadd_test.vec", read_mode);  
        while not endfile(vec_file) loop  
            readline(vec_file, buf_in);  
            read(buf_in, testv);  
  
            --apply the stimulus from the vector  
            A <= testv(0);  
            B <= testv(1);  
            cin <= testv(2);  
            wait for PERIOD;  
            assert (sum=testv(3) and cout=testv(4))  
                report "Test FAILED" severity error;  
        end loop;  
  
        wait; -- will wait forever  
    END process;  
END;
```

TB5: Writing Results to File

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE std.textio.all;
USE ieee.std_logic_textio.ALL;

ENTITY fadd_tb5 IS
END fadd_tb5;

ARCHITECTURE behavior OF fadd_tb5 IS
    -- Component Declaration for UUT
    COMPONENT fadder
    PORT (
        A,B,cin : IN  std_logic;
        sum,cout : OUT std_logic
    );
END COMPONENT;
```

```
--Inputs
signal A : std_logic := '0';
signal B : std_logic := '0';
signal cin : std_logic := '0';
--Outputs
signal sum : std_logic;
signal cout : std_logic;


BEGIN

    -- Instantiate the UUT
    uut: fadder PORT MAP (
        A => A,
        B => B,
        cin => cin,
        sum => sum,
        cout => cout
    );
```

TB5: Writing Results to File (2)

```
TB: process
    constant PERIOD: time:= 20ns;
    file vec_file, result_file: text;
    variable buf_in, buf_out: line;
    variable testv: std_logic_vector(0 to 4);
    BEGIN
        file_open(vec_file,"fadd_test.vec", read_mode);
        file_open(result_file,"fadd_test.out", write_mode);
        while not endfile(vec_file) loop
            readline(vec_file, buf_in);
            read(buf_in, testv);
            --apply the stimulus from the vector
            A <= testv(0);
            B <= testv(1);
            cin <= testv(2);
            wait for PERIOD;
            assert (sum=testv(3) and cout=testv(4))
                report "Test FAILED" severity error;
            write(buf_out, "Time="); write(buf_out, now);
            write(buf_out, ":A="); write(buf_out, testv(0));
            write(buf_out, ",B="); write(buf_out, testv(1));
            write(buf_out, ",cin="); write(buf_out, testv(2));
            write(buf_out, " ---> sum="); write(buf_out, sum);
            write(buf_out, ",cout="); write(buf_out, cout);
            writeline(result_file, buf_out);
        end loop;
        wait; -- will wait forever
    END process;
END;
```

TB5: Writing Results to File (2)

 

This is a Lite version of ISim.

Time resolution is 1 ps

Simulator is doing circuit initialization process.


Finished circuit initialization process.

ISim>

```
fadd_test.out - Notepad

File Edit Format View Help
Time=20 ns:A=0,B=0,cin=0 ---> sum=0,cout=0
Time=40 ns:A=0,B=0,cin=1 ---> sum=1,cout=0
Time=60 ns:A=0,B=1,cin=0 ---> sum=1,cout=0
Time=80 ns:A=0,B=1,cin=1 ---> sum=0,cout=1
Time=100 ns:A=1,B=0,cin=0 ---> sum=1,cout=0
Time=120 ns:A=1,B=0,cin=1 ---> sum=0,cout=1
Time=140 ns:A=1,B=1,cin=0 ---> sum=0,cout=1
Time=160 ns:A=1,B=1,cin=1 ---> sum=1,cout=1
```

TB5: Writing Results with OR/XOR error

 

```
architecture gates of fadder is
signal S1,S2,S3: std_logic;
begin
    S1 <= A xor B after 5 ns;
    S2 <= cin and S1 after 3 ns;
    S3 <= A and B after 3 ns;
    sum <= S1 or cin after 5ns;
    cout <= S2 or S3 after 3 ns;
end gates;
```

This is a Lite version of ISim.

Time resolution is 1 ps

Simulator is doing circuit initialization process.

Finished circuit initialization process.

at 80 ns: Error: Test FAILED

at 120 ns: Error: Test FAILED

ISim>

