

# CpE 690: Introduction to VLSI Design

## Lecture 12

### Low Power Design


Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology

Hoboken, NJ 07030

 Adapted from Digital Integrated Circuits: A Design Perspective, Rabaey *et. al.*, 2003  
and Lecture Notes, David Mahoney Harris CMOS VLSI Design




# CMOS – a Low Power Technology

- CMOS developed in 1970's as a low power technology
  - (almost) no DC current when gate is not switching
  - no static power dissipation
- CMOS replaces NMOS in 1980's as dominant digital technology
  - NMOS designs dissipated about  $200\mu\text{W}/\text{gate}$
  - Power dissipation no longer an issue!
- CMOS process technology evolves to provide:
  - more transistors per chip (Moore's Law)
  - faster switching speed (few MHz  $\Rightarrow$  hundreds of MHz)
- 1992 DEC announces Alpha 64-bit microprocessor
  - triumph of high speed CMOS digital design
  - first 200MHz processor, 1.7M transistors
  - **30W power dissipation !!**
  - Power dissipation is once again an issue!
 
# Why Power Matters: Package & System Cooling


- Need to remove heat from high performance chips
  - max. operating temperature silicon transistors: 150 – 200 °C
  - above these temperatures, dopants diffuse
- Chip on PC board can dissipate 2-3 watts
- With suitable heatsink, maybe 10 watts
- With forced-air cooling (fans), up to 150W



- With sophisticated liquid cooling, maybe 1000W
 
# Why Power Matters: Battery Size & Weight

- Today, we see more hand-held battery operated devices
- Unlike CMOS technology, battery technology has seen only modest improvements over last few decades



“Mobile Computing Environment”,  
Paradiso et. al. Pervasive  
Computing, IEEE 2005

- Expected battery lifetime increase over the next 5 years:  
30 to 40%

# Why Power Matters: Power Distribution

- Power Supply and Ground design
  - If  $V_{DD}=1.0V$ , a 100W chip draws 100 amps!
  - Many package pins required
  - Virtex-6 1924-pin package:
    - 220 power and 484 GND pins
  - On-chip wiring distribute this current
  - Electro-migration issues
- On-chip noise and system reliability
  - Large currents switched through package and PCB inductance
- Environmental Concerns
  - Computers and consumer electronics account for 15% of residential energy consumption



# Back to Basics: Power & Energy

- Power is drawn from a voltage source attached to the  $V_{DD}$  and GND pins of a chip.
- Instantaneous Power:  $P(t) = I(t)V(t)$  (watts)

- Energy: 
$$E = \int_0^T P(t)dt \quad (\text{joules})$$

- Average Power: 
$$P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t)dt$$


# Back to Basics: Power in Circuit Elements

- Power Supply:



$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$

- Resistor

 


$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$

- Capacitor



Capacitors don't  
dissipate power!

– but they do store energy:

 

$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t)dt = \int_0^{\infty} C \frac{dV}{dt} V(t)dt \\ &= C \int_0^{V_C} V(t)dV = \frac{1}{2} CV_C^2 \end{aligned}$$

# Power Dissipation in CMOS

- $P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$
- Dynamic power:  $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$ 
  - Switching load capacitances
  - Short-circuit current
- Static power:  $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$ 
  - Subthreshold leakage
  - Gate leakage
  - Junction leakage
  - Contention current



# Dynamic Power: Charging a Capacitor

- When the gate output rises from GND to  $V_{DD}$ :

- Energy stored in capacitor is

$$E_C = \frac{1}{2} C_L V_{DD}^2$$

- But energy drawn from the supply is


$$E_{VDD} = \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt$$

$$= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2 \quad \text{independent of size of transistors!}$$

- Half the energy from  $V_{DD}$  is dissipated in the pMOS transistor as heat, other half stored in capacitor


- When the gate output falls from  $V_{DD}$  to GND

 - Stored energy in capacitor is dumped to GND
- Dissipated as heat in the nMOS transistor



# Switching Waveforms

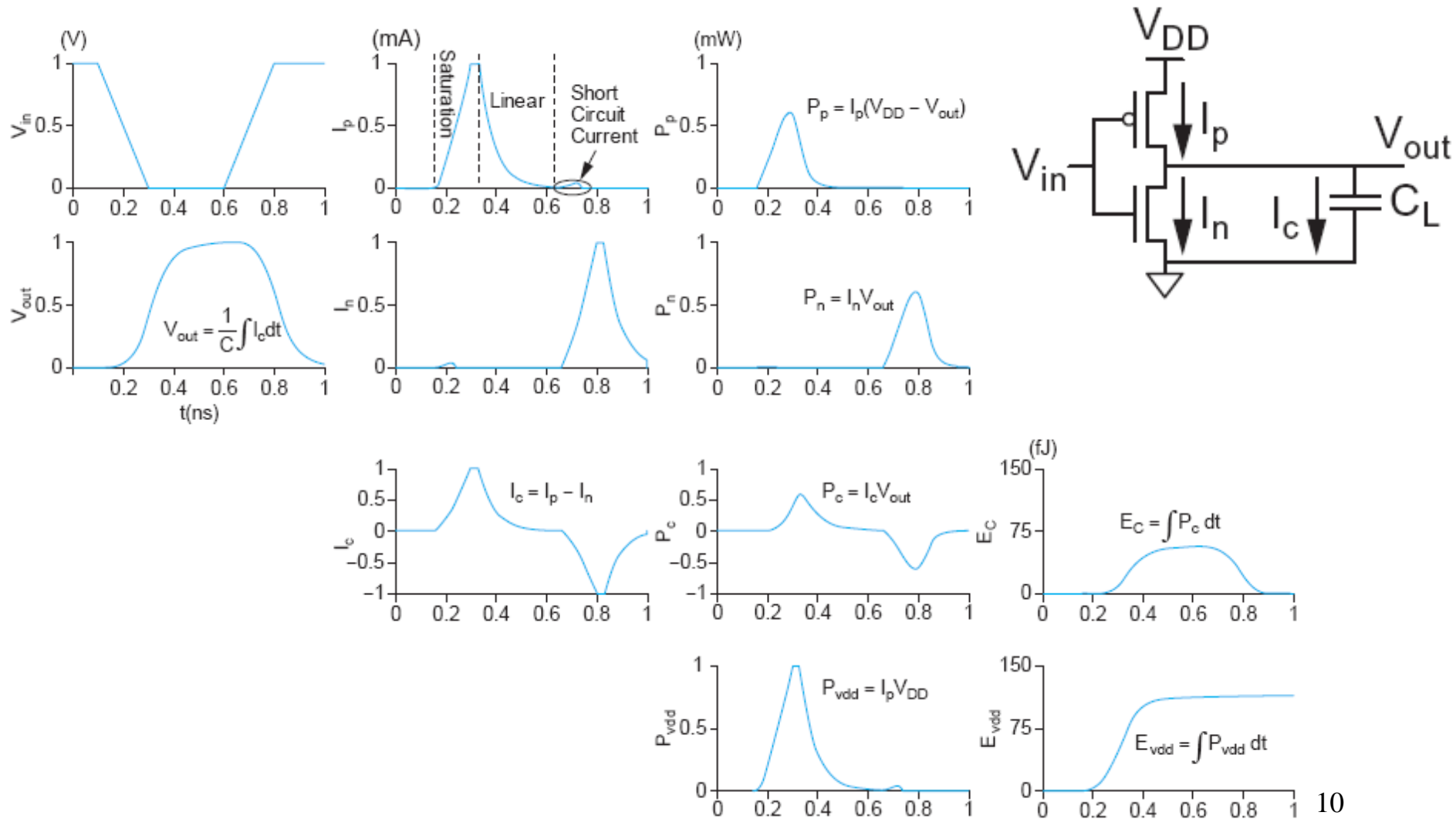- Example:  $V_{DD} = 1.0 \text{ V}$ ,  $C_L = 150 \text{ fF}$ ,  $f = 1 \text{ GHz}$



# Switching Waveforms


$$P_{switching} = \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt$$

$$= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt$$

$$= \frac{V_{DD}}{T} \times \left[ \begin{array}{l} \text{total charge drawn} \\ \text{from power supply} \\ \text{in time } T \end{array} \right]$$

$$= \frac{V_{DD}}{T} \times [T f_{sw} C V_{DD}]$$
 
$$P_{switching} = C \cdot V_{DD}^2 \cdot f_{sw}$$



*Note:  $P_{switching}$  is independent of drive strength of the nMOS and pMOS transistors*

# Activity Factor

- Suppose the system clock frequency =  $f$
- Most gates do not switch every clock cycle
- Let  $f_{sw} = \alpha f$ , where  $\alpha$  = activity factor
  - $\alpha = P_{0 \rightarrow 1}$  : probability that a signal switches from 0 to 1 in any clock cycle
  - If the signal is the system clock,  $\alpha = 1$
  - If the signal switches once per cycle,  $\alpha = 0.5$
  - If the signal is random (clocked) data,  $\alpha = 0.25$
  - Static CMOS logic has (empirically)  $\alpha \approx 0.1$
- Switching power of each node  $i$  is  $P_i = \alpha_i \cdot C_i \cdot V_{DD}^2 \cdot f$

$$P_{switching} = \sum_i P_i = V_{DD}^2 \cdot f \cdot \sum_i \alpha_i \cdot C_i$$

# Dynamic Power Example

- 1 billion transistor chip
  - 50M logic transistors
    - Average width:  $12 \lambda$
    - Activity factor = 0.1
  - 950M memory transistors
    - Average width:  $4 \lambda$
    - Activity factor = 0.02
  - 65 nm, 1.0V process ( $\lambda = 25\text{nm}$ )
  - $C = 1 \text{ fF}/\mu\text{m}$  (gate) +  $0.8 \text{ fF}/\mu\text{m}$  (diffusion)
- Estimate dynamic power consumption @ 1 GHz.  
Neglect wire capacitance and short-circuit current.

## Solution

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = [0.1C_{\text{logic}} + 0.02C_{\text{mem}}](1.0)^2 (1.0 \text{ GHz}) = 6.1 \text{ W}$$


# Reducing Switching Power

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

- So try to minimize:
  - Activity factor
  - Capacitance
  - Supply voltage
  - Frequency
 
# Activity Factor Estimation


- Let  $P_i$  = probability (node  $i = 1$ )  
and  $\bar{P}_i = (1 - P_i)$  = probability (node  $i = 0$ )
- $\alpha_i$  = prob. that node  $i$  makes a transition from 0 to 1, so
- $\alpha_i = \bar{P}_i \cdot P_i = (1 - P_i) \cdot P_i$





 
# Activity Factor Estimation

- For random data,  $\alpha = 0.5 \cdot 0.5 = 0.25$



- Data is often not completely random
  - e.g. upper bits of 64-bit words representing bank account balances are usually 0
- Data propagating through ANDs and ORs has lower activity factor

# Example: Switching Probability of NOR2

 

- For NOR2,  $P_Y = \overline{P}_A \cdot \overline{P}_B$
- $\overline{P}_Y = (1 - P_Y) = (1 - \overline{P}_A \cdot \overline{P}_B)$
- $\alpha_Y = P_Y \cdot \overline{P}_Y$   
 $= (\overline{P}_A \cdot \overline{P}_B) \cdot (1 - \overline{P}_A \cdot \overline{P}_B)$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

- If  $P_A = P_B = 0.5$ ,  $P_Y = 0.25$ ,  $\alpha_Y = 3/16 \approx 0.19$




# Switching Probabilities (Static Gates)

Gate	$P_Y$
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

- Remember  $\alpha_Y = \bar{P}_Y \cdot P_Y$

# Example: 4-input AND gate

- Assume all inputs have  $P=0.5$

   


- Which has the lowest power?
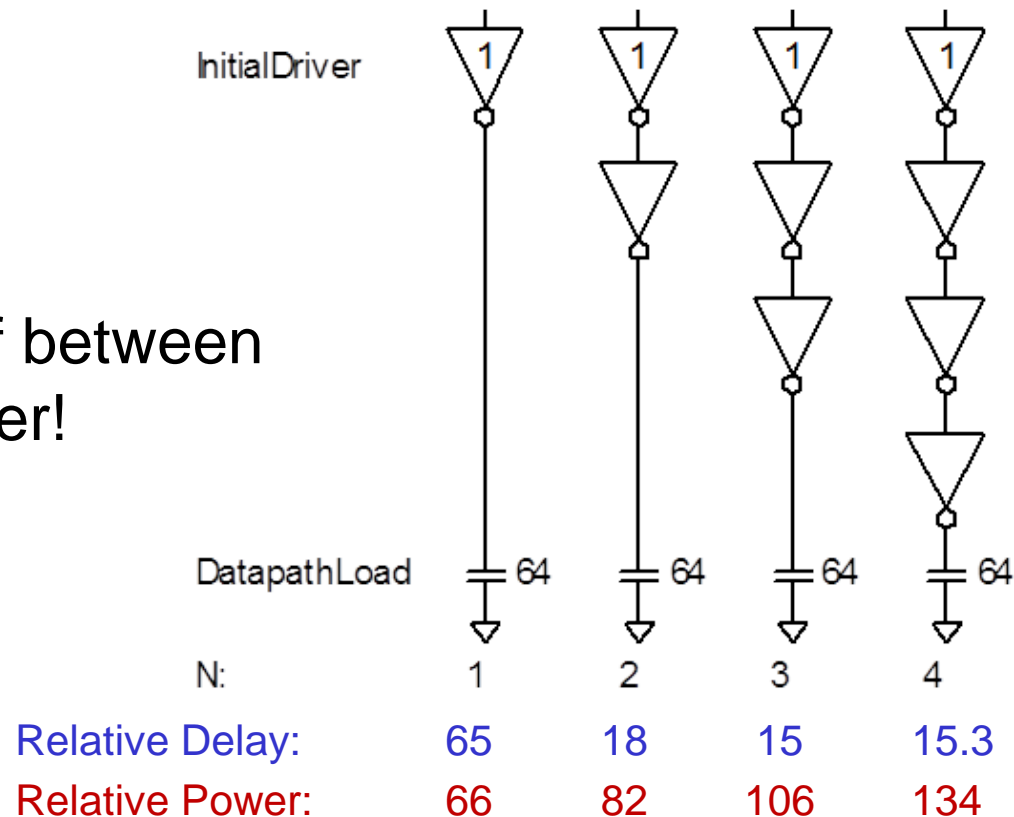
# Number of Stages vs. Power



- Power depends on activity and capacitance at each node
  - Generally fewer stages usually mean less power
- Compare this to delay
  - frequently add stages to improve delay (stage effort  $\approx 4$ )

- Usually tradeoff between speed and power!


 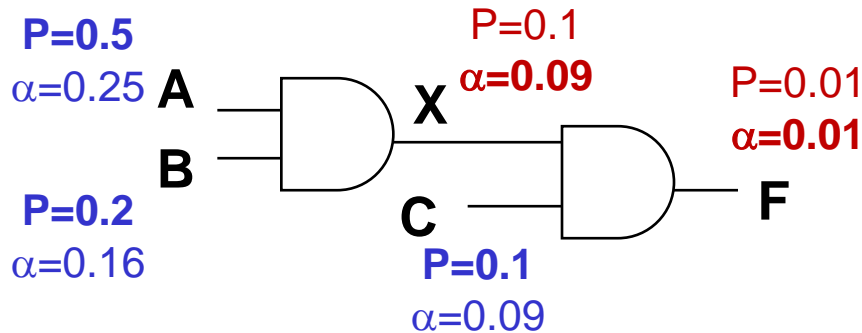
# Input Ordering



- What if inputs have different activity levels?



- Beneficial to postpone the introduction of signals with a **high** activity
  - i.e. signals with signal probability close to 0.5
  
# Beware of Glitches!

- Extra transitions caused by finite propagation delay




*Suppose input changes  
from  $ABCD = "1101"$  to  $"0111"$  ?*

*Glitching occurs whenever a node  
makes more transitions than  
necessary to reach its final value*

*Glitching can raise the activity  
factor of a gate to greater than 1!*

# Activity of Dynamic Circuits

 
*Exercise: What is activity factor of node Y (output of a dynamic NOR2) if  $P_A=P_B=0.5$  ?*





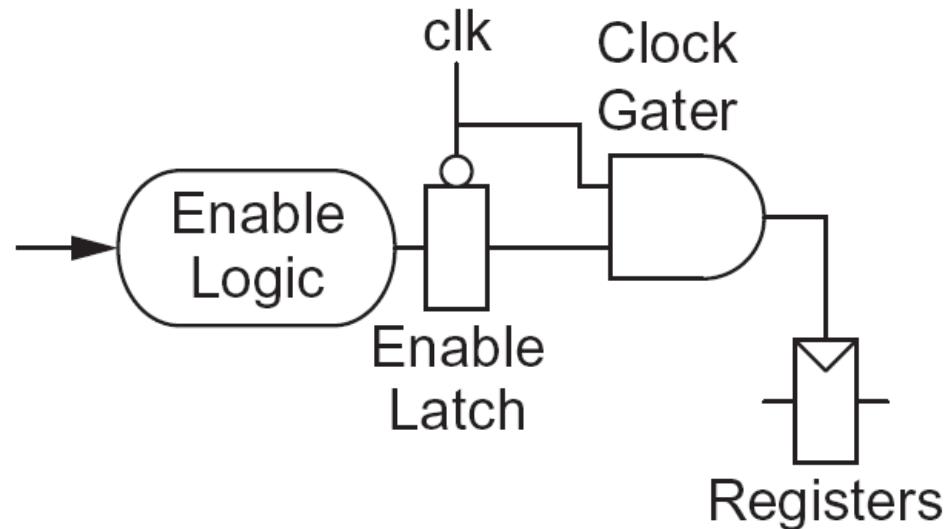
# Clock Gating

- Another way to reduce the activity is to turn off the clock to registers in unused blocks
  - Saves clock activity ( $\alpha = 1$ )
  - Eliminates all switching activity in the block
  - Requires determining if block will be used


 
# Capacitance

- Extra capacitance slows response and increases power
  - Always try to reduce parasitic and wiring capacitance
  - Good floorplanning to keep high activity communicating gates close to each other
  - Drive long wires with inverters or buffers rather than complex gates
- Gate sizing and number of stages
  - Designing network for minimum delay will usually result in a high-power network.
  - Small increase in delay (by reducing the # of stages or increasing the logical effort per stage) can give large reduction in power
  - There are no closed form solutions to determine gate sizes that minimize power under a delay constraint.
  - Can be solved numerically



# Voltage


- Power dissipated in gate is  $P_{av} = \alpha \cdot f \cdot C_L \cdot V_{DD}^2$
- Energy per switching event\* is  $E_s = P_{av} / (2 \cdot \alpha \cdot f) = (C_L \cdot V_{DD}^2) / 2$ 
  - Power & Energy can be significantly reduced by decreasing  $V_{DD}$
- *But* delay of gate is  $D = (C_L \cdot \Delta V) / I$ 
$$\approx (C_L \cdot V_{DD}) / [(\beta/2) \cdot (V_{DD} - V_t)^2]$$
  - Decreasing  $V_{DD}$  increases delay
- Circuit can be made (almost) arbitrarily low power at the expense of performance – not very useful

\* *switching event is defined as a transition from 0→1 or 1→0*
 
# Energy-Delay Product

- Introduce metric **energy-delay product** (EDP)

$$EDP = E_s \cdot D = \frac{k \cdot C_L^2 \cdot V_{DD}^3}{(V_{DD} - V_t)^2}$$



- Minimum EDP at  $V_{DD} = 3 \cdot V_t$  (for long channel process)


# Frequency

- Suppose we can do a task in  $T$  sec. on one processor
- Can we do it in  $T/2$  sec. on two processors
  - if application has sufficient intrinsic parallelism
- How about doing it in  $T$  sec. on two processors running at half clock frequency?

$$\begin{array}{|c|} \hline \text{Proc. at} \\ V \text{ volts, } f \text{ Hz} \\ = P \text{ watts} \\ \hline \end{array} \quad \equiv \quad \begin{array}{|c|} \hline \text{Proc. at} \\ V \text{ volts, } f/2 \text{ Hz} \\ = P/2 \text{ watts} \\ \hline \end{array} + \begin{array}{|c|} \hline \text{Proc. at} \\ V \text{ volts, } f/2 \text{ Hz} \\ = P/2 \text{ watts} \\ \hline \end{array}$$

- This gives no net power savings.
- But  $speed \propto (V_{DD} - V_T)^2 / V_{DD}$ , so if we reduce clock frequency, we can also reduce  $V_{DD}$ :

# Reduced Frequency & Voltage

 

*In this example,  
reducing speed by  
factor of 50%  
allows voltage  
reduction of ~35%*

Proc. at  
 $V$  volts,  $f$  Hz  
 $= P$  watts

$\equiv$


Proc. at  $0.65V$   
volts,  $f/2$  Hz  
 $\approx 0.2 P$  watts

+

Proc. at  $0.65V$   
volts,  $f/2$  Hz  
 $\approx 0.2 P$  watts

- Parallelism with reduced  $f$  and  $V_{DD}$  leads to lower power
  - diminishing returns as  $V_{DD}$  approaches  $V_T$


# Dynamic Power Dissipation Example

 

- A NAND2 gate of size (input capacitance) 12C is driving an inverter of size 36C which in turn drives a load of 120C units of capacitance. Assume the inputs A, B are independent and uniformly distributed. What is the power dissipation of this circuit if the gate capacitance C of a unit sized transistor is 0.1fF,  $V_{DD}$  is 1.0V and the operating frequency is 1GHz?
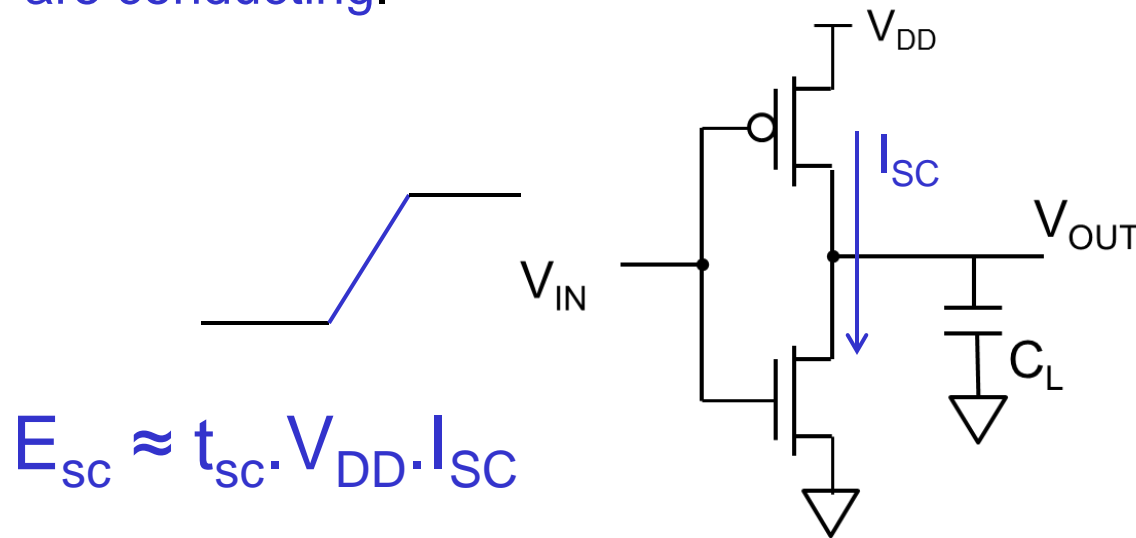
# Short-Circuit Power

- Finite slope of the input signal
  - sets up a direct current path between  $V_{DD}$  and GND for a short period during switching when both the NMOS and PMOS devices are conducting.




- Depends on duration and slope of the input signal,  $t_{sc}$
- $I_{SC}$  which is determined by
  - saturation current of the P and N transistors
    - depends on sizes, process technology, temperature, etc.
  - ratio between input and output slopes (a function of  $C_L$ )




# Slope Engineering

## Small Capacitive Load

 


- Output fall time significantly shorter than input rise time
- Output “tracks” input as per DC transfer function
- Large  $I_{SC}$  when  $V_{IN} = V_{SW} \approx V_{DD}/2$

## Large Capacitive Load

 

- Output fall time significantly longer than input rise time
- Output transition lags input
- When  $V_{IN} = V_{SW}$ ,  $V_{dsp}$  is still very small, so small  $I_{SC}$

# Impact of $C_L$ on $I_{SC}$

 


- When  $C_L$  is small,  $I_{SC}$  is large!
  - Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - [slope engineering](#).
- Typically less than 10% of dynamic power if rise/fall times are comparable for input and output

# Static Power Dissipation

- Static power is consumed even when chip is quiescent
  - i.e. powered up but not running
- Ratio'ed circuits (e.g. pseudo-NMOS) burn power in fight between ON transistors
  - known as contention current
- Leakage consumes power from current passing through normally off devices
  - sub-threshold current
  - gate leakage current
  - diode junction leakage current

# Leakage Sources

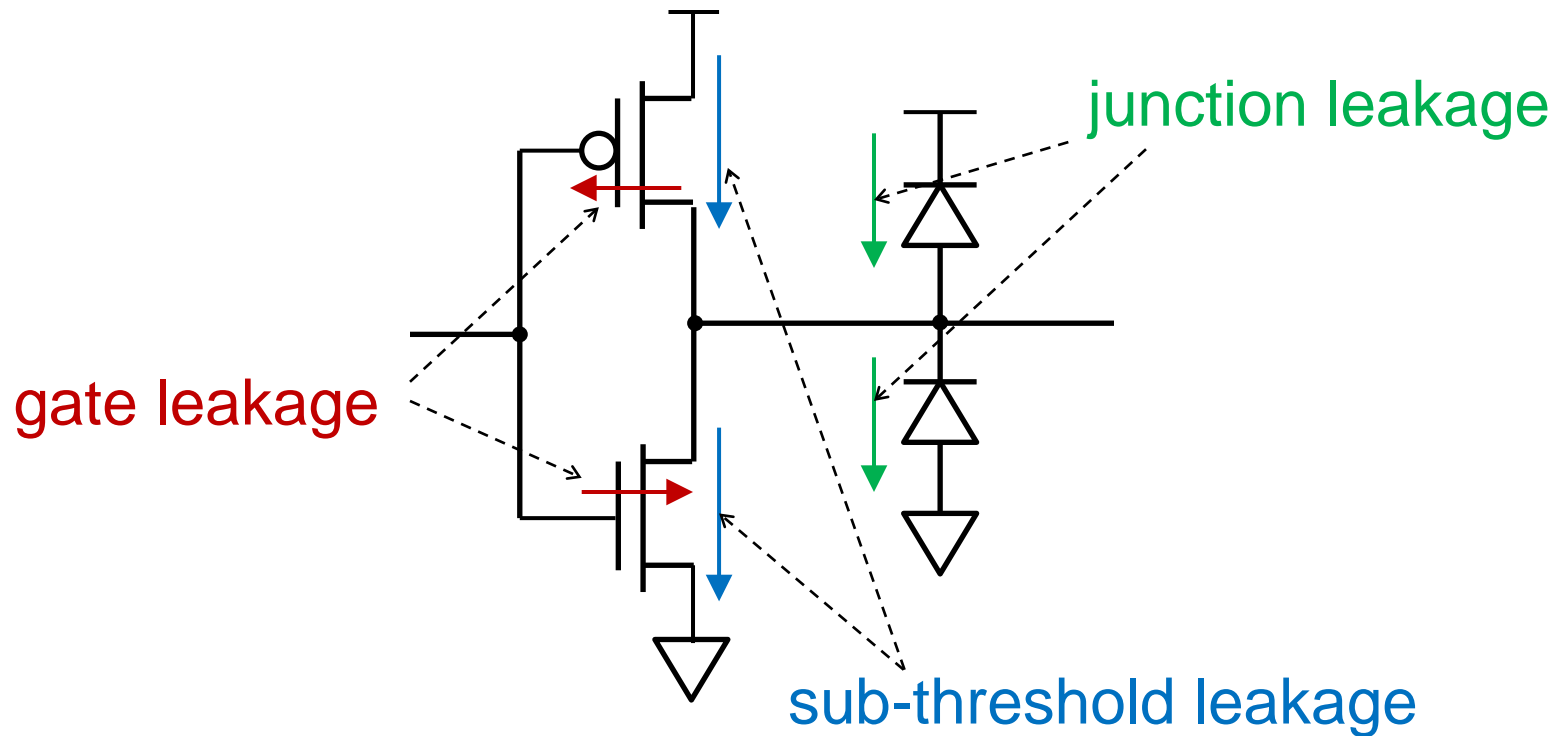


- Leakage currents are very small (per transistor basis)
  - prior to 130 nm, not usually an issue (except in sleep mode of battery operated devices)
  - but when multiplied by hundreds of millions of nanometer devices, can account for as much as 1/3 of active power
- All increase exponentially with temperature

# Sub-threshold Leakage

- Shockley model assumes  $I_d = 0$  when  $V_{gs} \leq V_t$
- But in real transistors,  $I_d \approx 100nA \times (W/L)$  when  $V_{gs} = V_t$
- For  $V_{gs} < V_t$ ,  $I_d$  decreases exponentially with  $V_{gs}$

$$I_d = I_0 10^{\frac{(V_{gs} - V_t)}{S}}$$

 where  $S$  is sub-threshold slope  $\approx 100\text{mV/decade}$



# Sub-threshold Leakage

- In sub-threshold:  $I_d = I_0 10^{\frac{(V_{gs}-V_t)}{S}}$
- In nanometer processes, as we reduce  $V_{DD}$ , we also reduce  $V_t$  to maintain good *on-current*
- But *off-current*  $I_{off} = I_0 10^{\frac{(-V_t)}{S}}$  increases with smaller  $V_t$

Typical values in 65 nm,  $V_{ds}=1.0V$ :


$$I_{off} = 100 \text{ nA}/\mu\text{m} @ V_t = 0.3 \text{ V}$$

$$I_{off} = 10 \text{ nA}/\mu\text{m} @ V_t = 0.4 \text{ V}$$

$$I_{off} = 1 \text{ nA}/\mu\text{m} @ V_t = 0.5 \text{ V}$$
 
# Stack Effect

- Series OFF transistors have less leakage
  - for N1 to have any leakage,  $V_x > 0$
  - so N2 has negative  $V_{gs}$
  - leakage through 2-stack reduces  $\sim 10\times$
  - leakage through 3-stack reduces further
- Leakage and delay trade off
  - Aim for low leakage in sleep and low delay in active mode
- To reduce leakage:
  - Increase  $V_t$ : *multiple*  $V_t$ 
    - Use low  $V_t$  only in speed critical circuits
  - Increase  $V_s$ : *stack effect*
    - *Input vector control* in sleep



# Gate & Junction Leakage


- **Gate leakage** extremely strong function of  $t_{\text{ox}}$  and  $V_{\text{gs}}$ 
  - Negligible for older processes
  - Approaches sub-threshold leakage at 65 nm
- An order of magnitude less for pMOS than nMOS
- Control gate leakage in the process using  $t_{\text{ox}} > 10 \text{ \AA}$ 
  - High-k gate dielectrics help
  - Some processes provide multiple  $t_{\text{ox}}$ 
    - e.g. thicker oxide for 3.3 V I/O transistors
- **Junction leakage** usually negligible
  - becoming little more significant in nanometer processes
- Control gate & junction leakage in circuits by limiting  $V_{\text{DD}}$


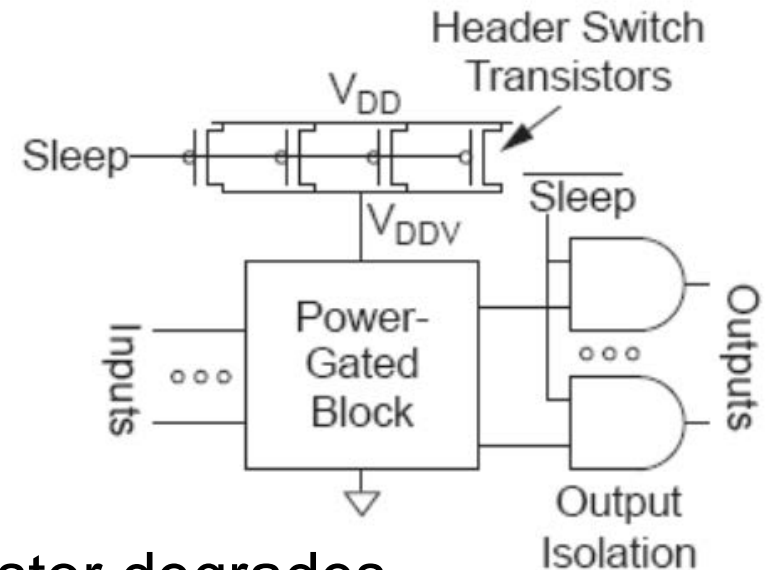
# Power Gating

- Turn OFF power to blocks when they are idle to save leakage

- Use virtual  $V_{DD}$  ( $V_{DDV}$ )
- Gate outputs to prevent invalid logic levels to next block



- Voltage drop across sleep transistor degrades performance during normal operation
  - Size the transistor wide enough to minimize impact
- Switching wide sleep transistor costs dynamic power
  - Only justified when circuit sleeps long enough

# Static Power Example

- Revisit power estimation for 1 billion transistor chip
- Estimate static power consumption
  - 65nm process,  $V_{DD}=1.0V$ ,  $\lambda = 25nm$
  - 50M logic transistors (average width  $12 \lambda$ )
  - 950M memory transistors (average width  $4 \lambda$ )
  - Subthreshold leakage
    - Normal  $V_t$ : 100 nA/ $\mu m$
    - High  $V_t$ : 10 nA/ $\mu m$
    - High  $V_t$  used in all memories and in 95% of logic gates
  - Gate leakage 5 nA/ $\mu m$
  - Junction leakage negligible

# Static Power Solution

$$W_{\text{normal-}V_t} = (50 \times 10^6)(12\lambda)(0.025\mu\text{m} / \lambda)(0.05) = 0.75 \times 10^6 \mu\text{m}$$

$$W_{\text{high-}V_t} = \left[ (50 \times 10^6)(12\lambda)(0.95) + (950 \times 10^6)(4\lambda) \right] (0.025\mu\text{m} / \lambda) = 109.25 \times 10^6 \mu\text{m}$$

$$I_{\text{sub}} = \left[ W_{\text{normal-}V_t} \times 100 \text{ nA}/\mu\text{m} + W_{\text{high-}V_t} \times 10 \text{ nA}/\mu\text{m} \right] / 2 = 584 \text{ mA}$$

$$I_{\text{gate}} = \left[ (W_{\text{normal-}V_t} + W_{\text{high-}V_t}) \times 5 \text{ nA}/\mu\text{m} \right] / 2 = 275 \text{ mA}$$

$$P_{\text{static}} = (584 \text{ mA} + 275 \text{ mA})(1.0 \text{ V}) = 859 \text{ mW}$$

# Voltage & Frequency Control

- Run each block at the lowest possible voltage and frequency that meets performance requirements
- Multiple Voltage Domains
  - Provide separate supplies to different blocks
  - Level converters required when crossing from low to high  $V_{DD}$  domains
- Dynamic Voltage Scaling
  - Adjust  $V_{DD}$  and  $f$  according to workload

