

## Lecture 13

### Design of Arithmetic Circuits


Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology


Hoboken, NJ 07030

 Adapted from Lecture Notes, David Mahoney Harris CMOS VLSI Design



 
# Generic Digital Processor

- **Arithmetic Unit**
  - bit-sliced datapath
  - adder, multiplier, shifter, comparator etc.
- **Memory**
  - RAM, ROM
  - registers, FIFO etc.
- **Control**
  - Finite state machine
  - PLA, random logic
- **Interconnect**
  - switches
  - arbiters
  - bus


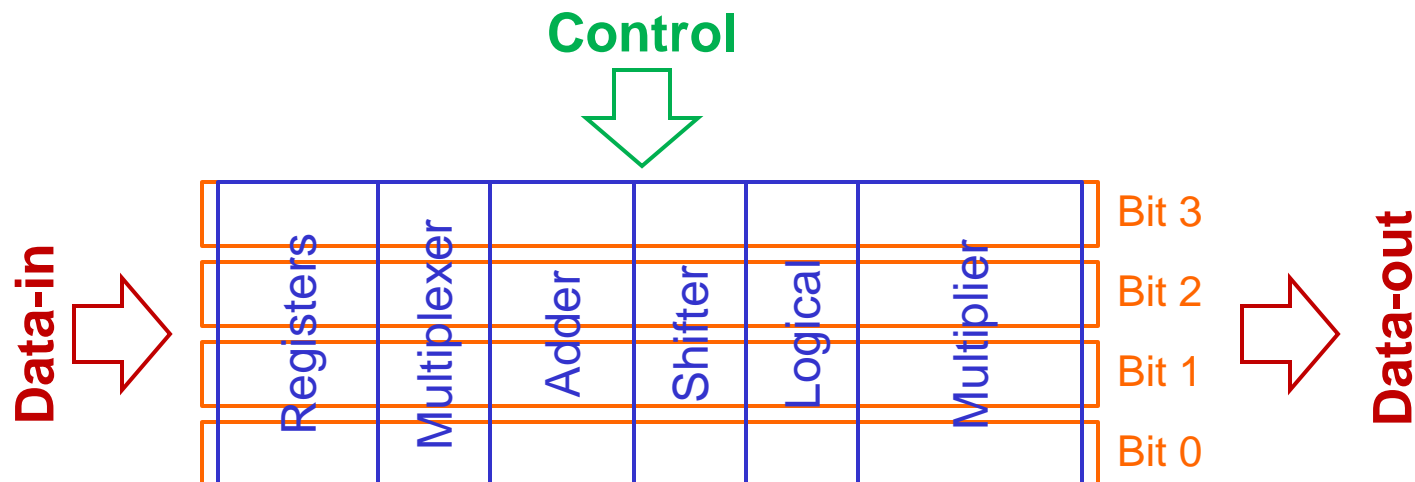
# Bit-Sliced Datapath


- Datapath (or ALU) may consist of number of arithmetic units components that operate on uniform width data words (e.g. 32-bit)
  - Arithmetic components often apply the same operation to each bit in the data word (e.g. add, and, left-shift)
- Bit-Sliced is an efficient physical layout style in which an  $n$ -bit datapath built by stacking together  $n$  1-bit data paths
  - Data buses run (mostly) in the horizontal direction
  - Control runs (mostly) in the vertical direction



# Single Bit Addition: Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 



A	B	C	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full Adder Design I


- Direct Implementation of Boolean Equations:

$$\text{SUM} = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

 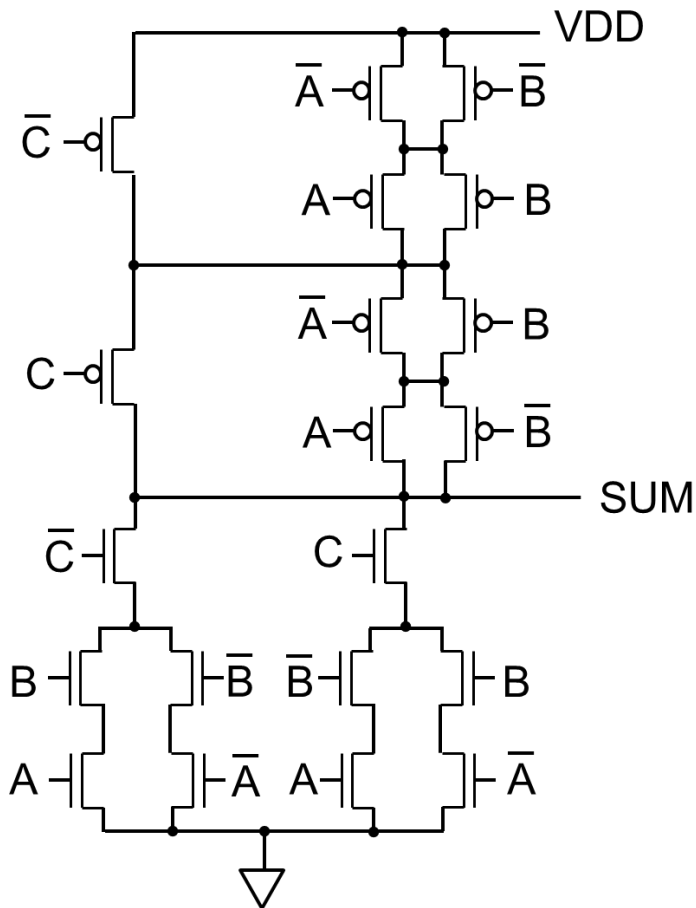


36 transistors

 

# Mult-bit Ripple Carry Adder

- Simplest design: cascade full adders

 

- Critical path goes from C<sub>in</sub> to C<sub>out</sub>
- Worst case delay is linear in number of bits


$$t_d (N\text{-bit adder}) = (N-1) \cdot t_{\text{carry}} + t_{\text{sum}}$$

- To make a fast adder, we need to minimize delay  
 $t_{\text{carry}}$  = (delay from C to C<sub>out</sub>) in each full adder
  - $t_{\text{sum}}$  (delay from A,B,C to S) is negligible for large N
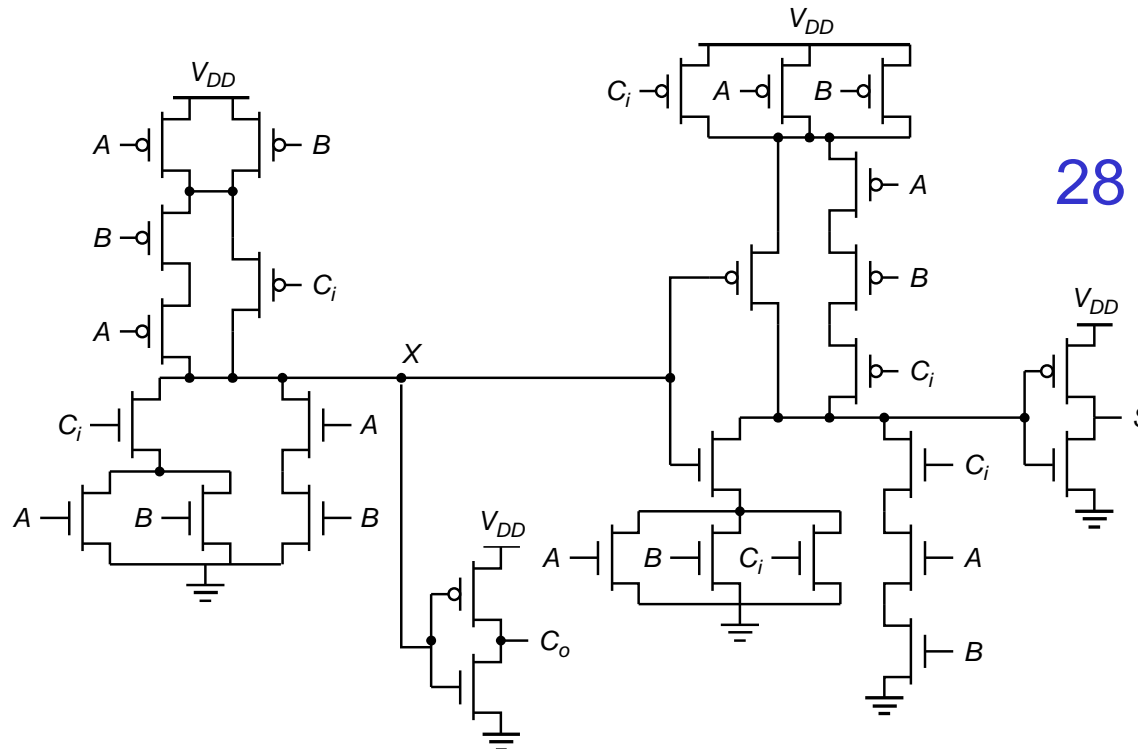
# Full Adder Design II

- A more compact design can be realized by generating S as a function of  $C_{out}$  :

$$S = ABC + (A + B + C) \cdot \overline{C}_{out}$$




28 transistors

- If we could eliminate output inverters
  - simplify design and reduce C to  $C_{out}$  delay
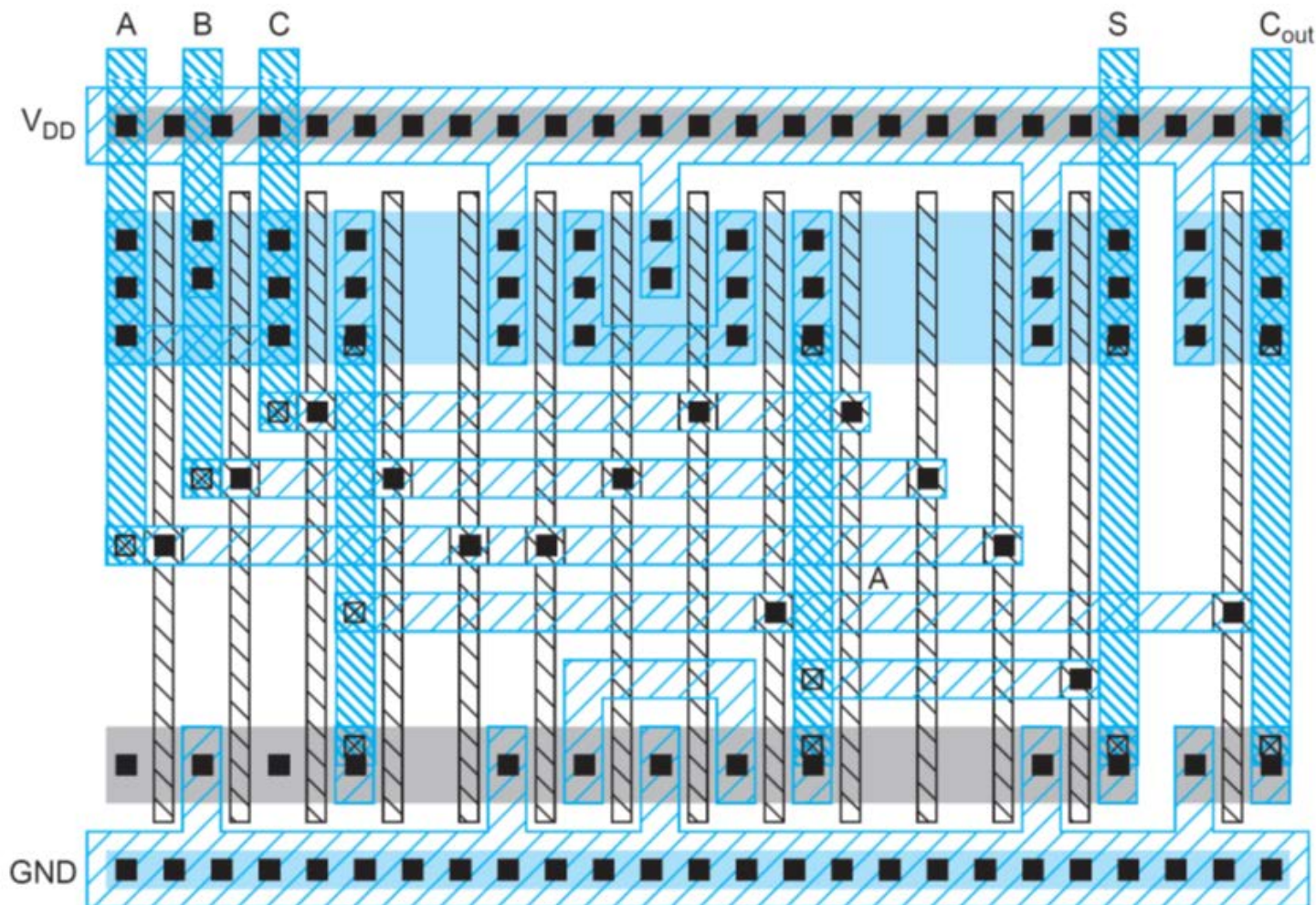
# Full Adder Design II - Layout


- Standard cell style (not bit-slice) layout:





 
# Full Adder Inversion


- Full adder is symmetric with respect to signal inversion:



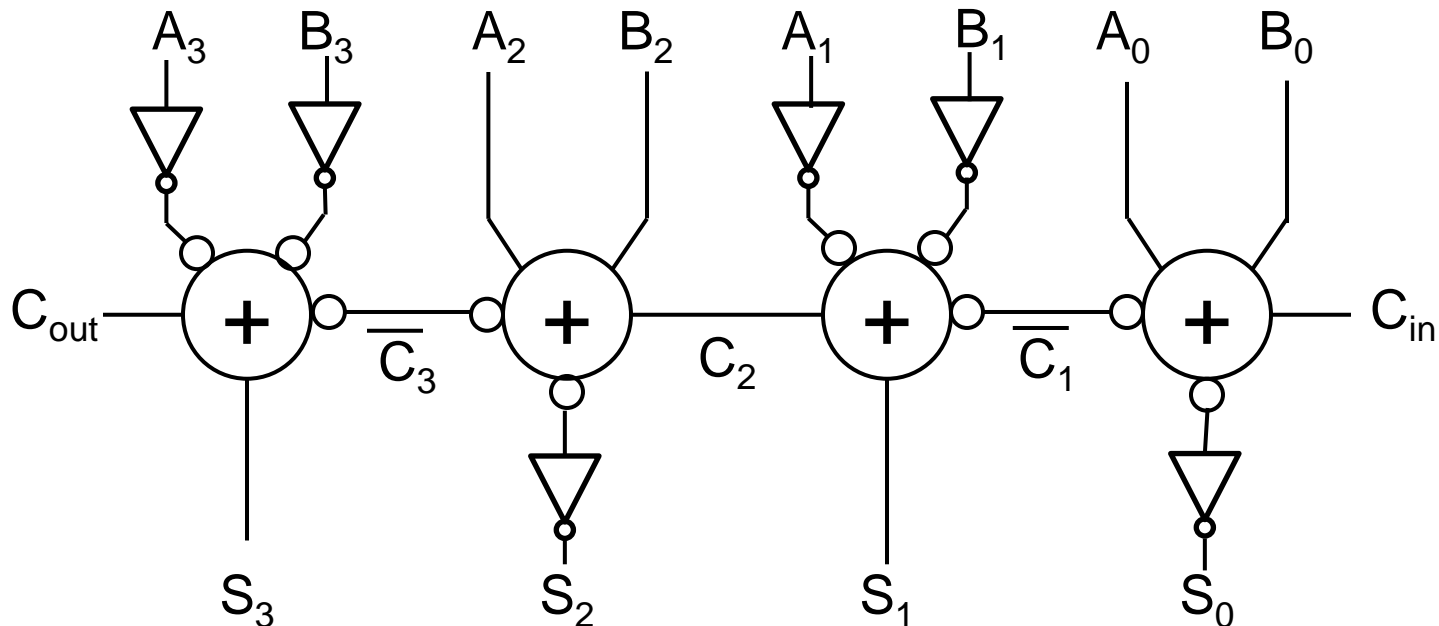- Eliminate inverters and use inverting full adder



# Full Adder: Design III (Mirror Adder)

 


24 transistors

- Output inverters removed
- pMOS and nMOS networks are “mirror” of each other
  - rather than complimentary – simplifies layout
  - enabled by symmetry of the add operation
- Transistors placed & sized to minimize carry propagation
  - at the expense of sum generation
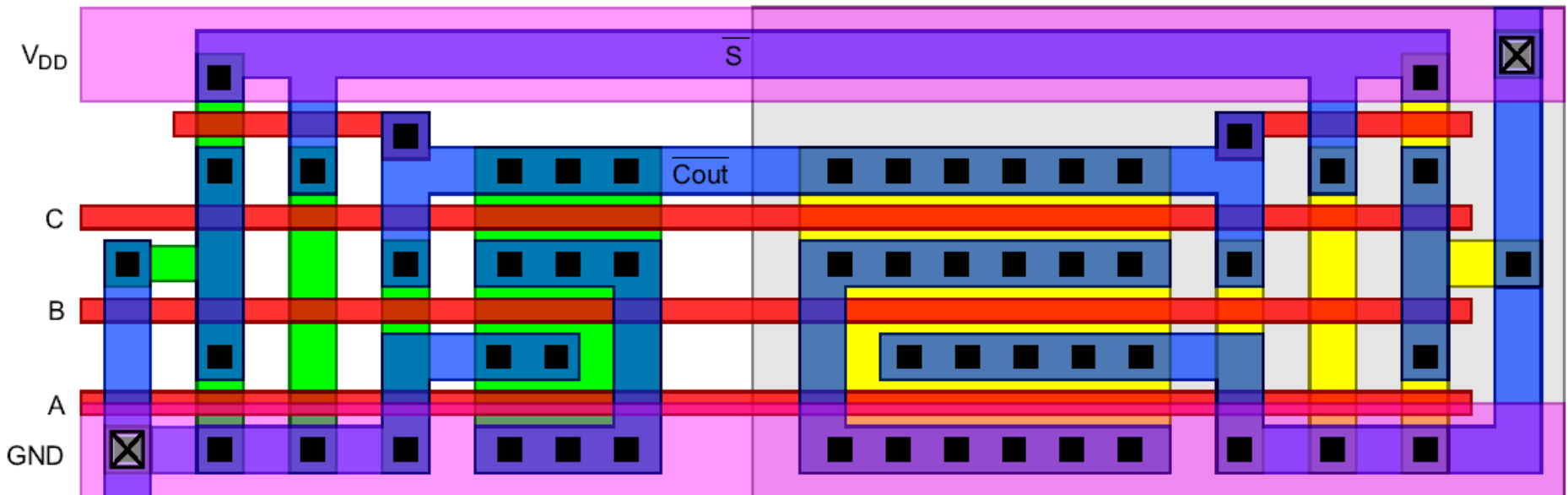
# Mirror Adder Layout

- Bit-slice cell style (not standard cell) layout:



- Transistors now run vertically with horizontal poly
- Data travels from left to right
  - carry propagates vertically from one bit to the next
- Can build wide transistors without affecting bit pitch

# GPK Representation


- Introduce new intermediate signals that describe full adder operation in terms of carry propagation

A	B	C	G	P	K	C <sub>out</sub>	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

- $G = A \cdot B$  (i.e. **generate** carry:  $C_{out} = 1$  independent of C)
- $K = \bar{A} \cdot \bar{B}$  (i.e. **kill** carry:  $C_{out} = 0$  independent of C)
- $P = A \oplus B$  (i.e. **propagate** carry:  $C_{out} = C$ )
- Note that G, P and K are:
  - mutually exclusive
  - only functions of A and B (don't need to wait for C)

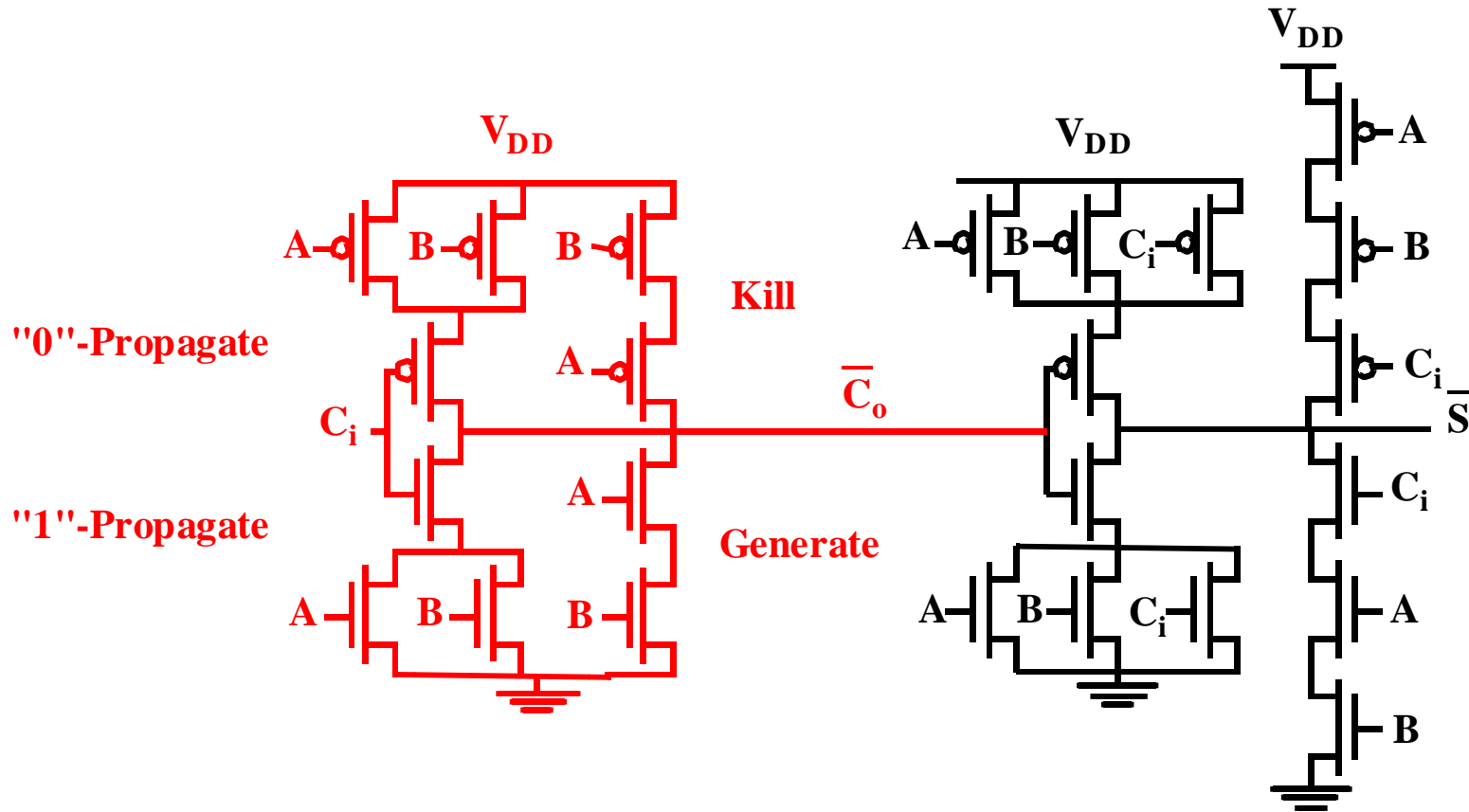
# GPK Representation

- Can see the action of generate, propagate and kill operators in mirror adder:


 
# Using GPK to Speed up Carry Propagation

- Divide the words to be added into bit groups or blocks
  - e.g. think about adding 4-bits at a time



- Addition of each block is a three-step process:


1. Compute bit-wise generate, propagate (& kill) signals

$$G_i = A_i \cdot B_i \qquad P_i = A_i \oplus B_i \qquad K_i = \overline{A_i} \cdot \overline{B_i}$$

2. Use PG(K) signals and  $C_{in}$  to determine  $C_i$  for each bit (and  $C_{out}$ ) *(this is the only speed-critical operation)*


3. Calculate sums using  $S_i = P_i \oplus C_i$

# Group Addition with PG Logic

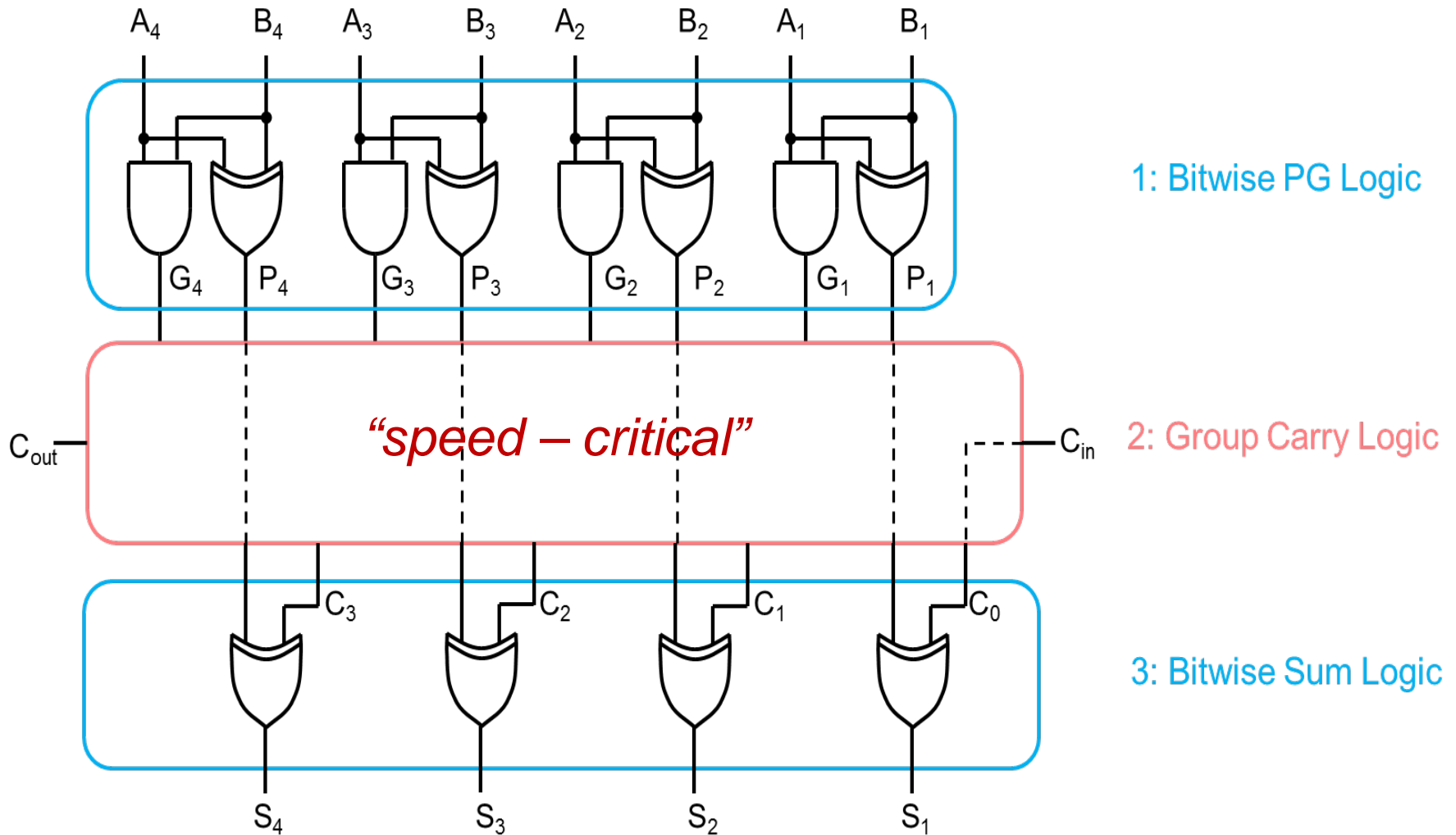

 
# Group Carry Logic: Manchester Carry

- Use transmission gates to provide carry propagation




static

 


dynamic



# 4-bit Manchester Carry Logic

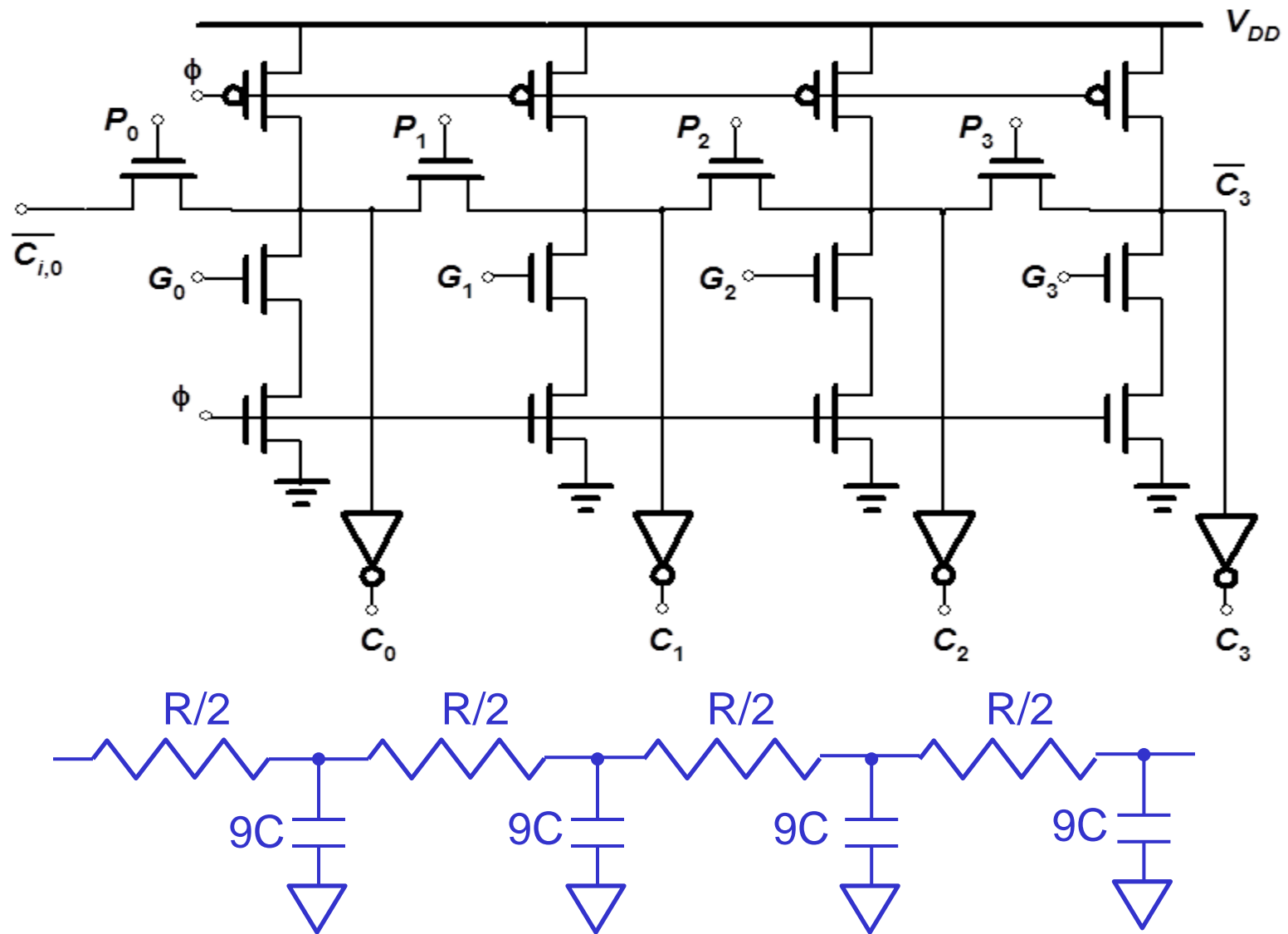

# Delays in Manchester Chain

 


- Using Elmore, delay (after  $n$  stages) =  $(9/4).n(n+1)RC$
- Delay increases quadratically with  $n$

<b>n</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>
total delay	4.5 RC	13.5 RC	27 RC	45 RC
delay of extra stage		9 RC	13.5 RC	18 RC

- Better to add a couple of inverters after 3-4 bits
  - makes overall delay linear in  $n$
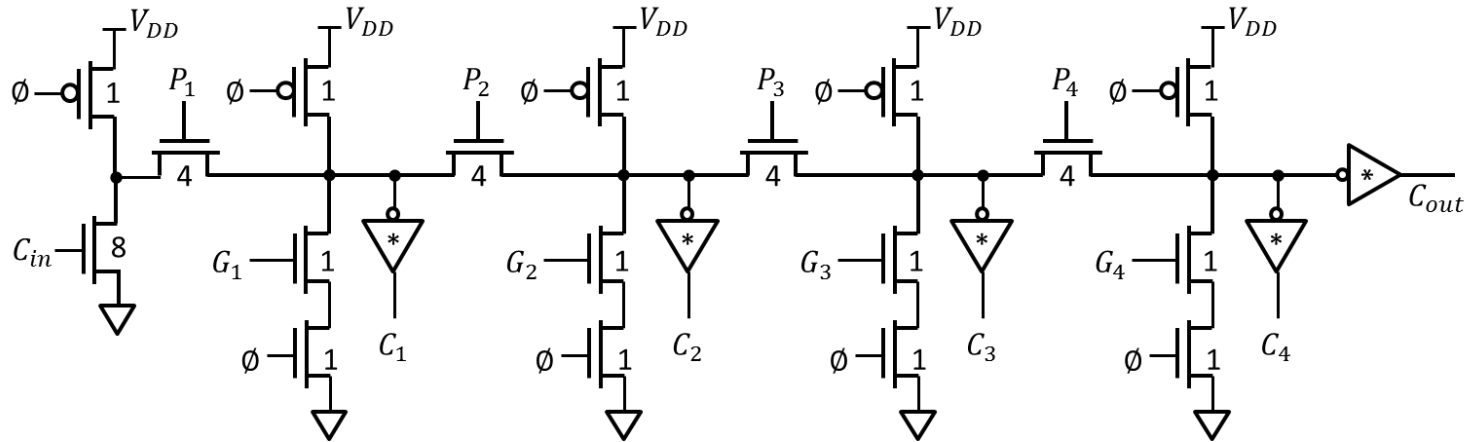
# Manchester Chain with pre and post-inverter




\* each inverter has  $P=1$ ,  $N=1$


number of bits	1	2	3	4	5	6	7	8
total delay (RC)	16.8	22.5	30.3	40	51.8	65.5	81.3	99.0
delay per bit ( $\tau$ )	5.6	3.8	3.4	3.3	3.5	3.6	3.9	4.1

- Compare to Mirror Adder Ripple Carry =  $5.5\tau$  per bit

# Manchester Carry Stick Layout

 


# Carry-Bypass Adder

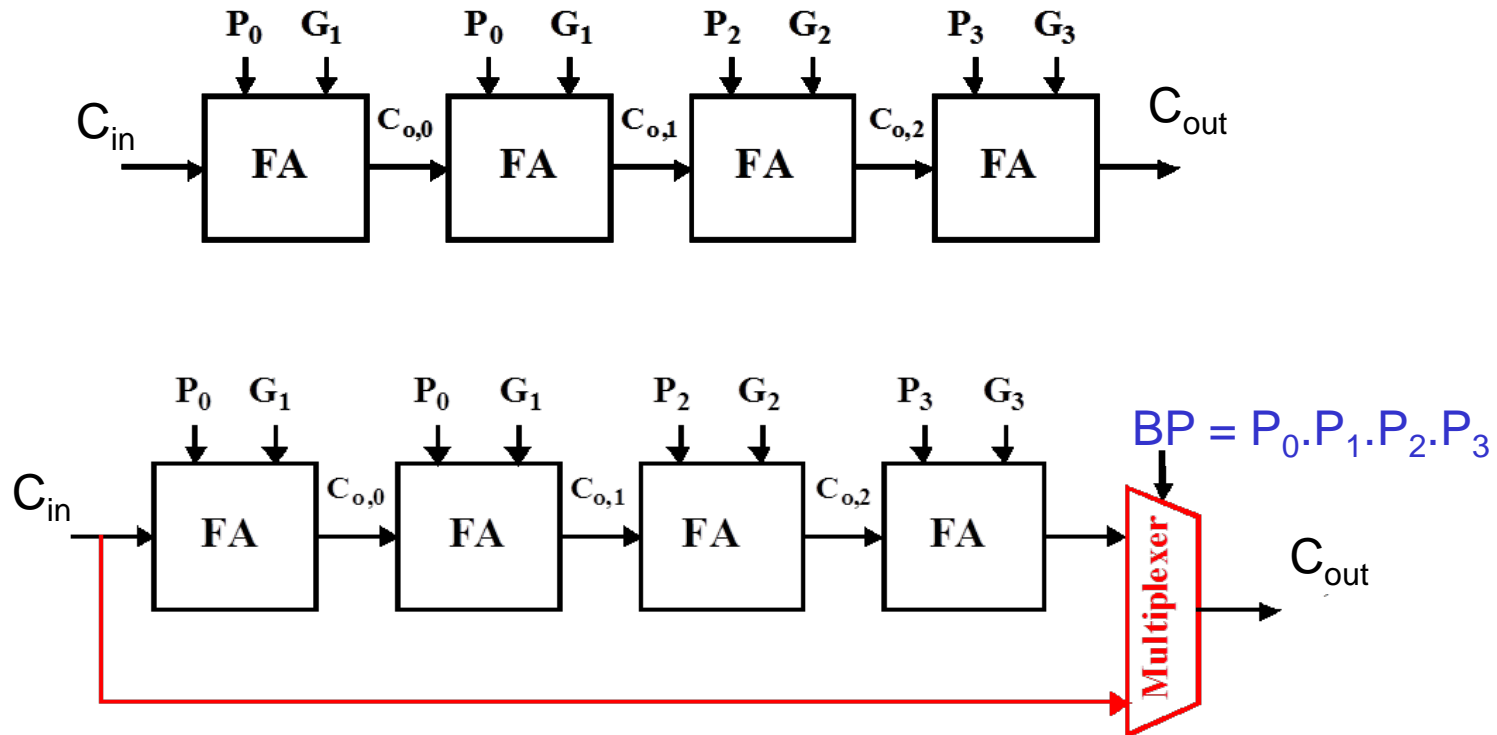


- If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3$ ) then  $C_{out} = C_{in}$
- Otherwise use PG within the block
- In an large adder with many blocks, BP is set up well before  $C_{in}$  arrives
- Also known as Carry-Skip Adder

# Carry-Bypass Manchester Block

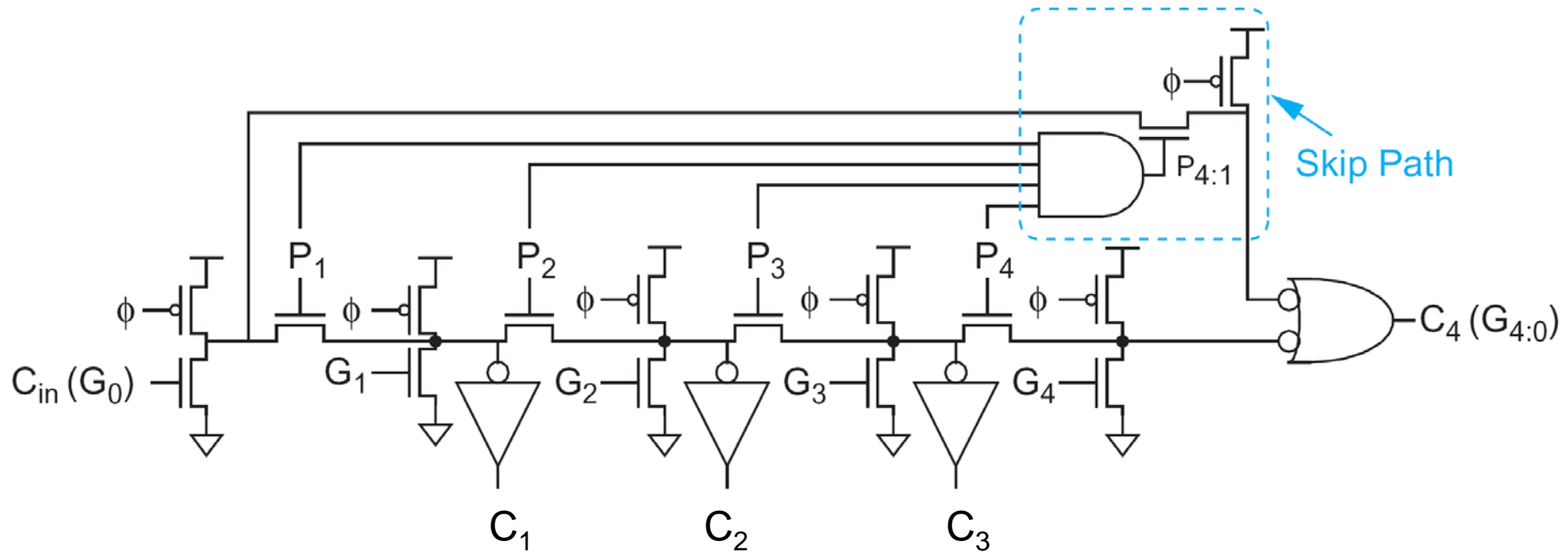


# Carry-Bypass Critical Path

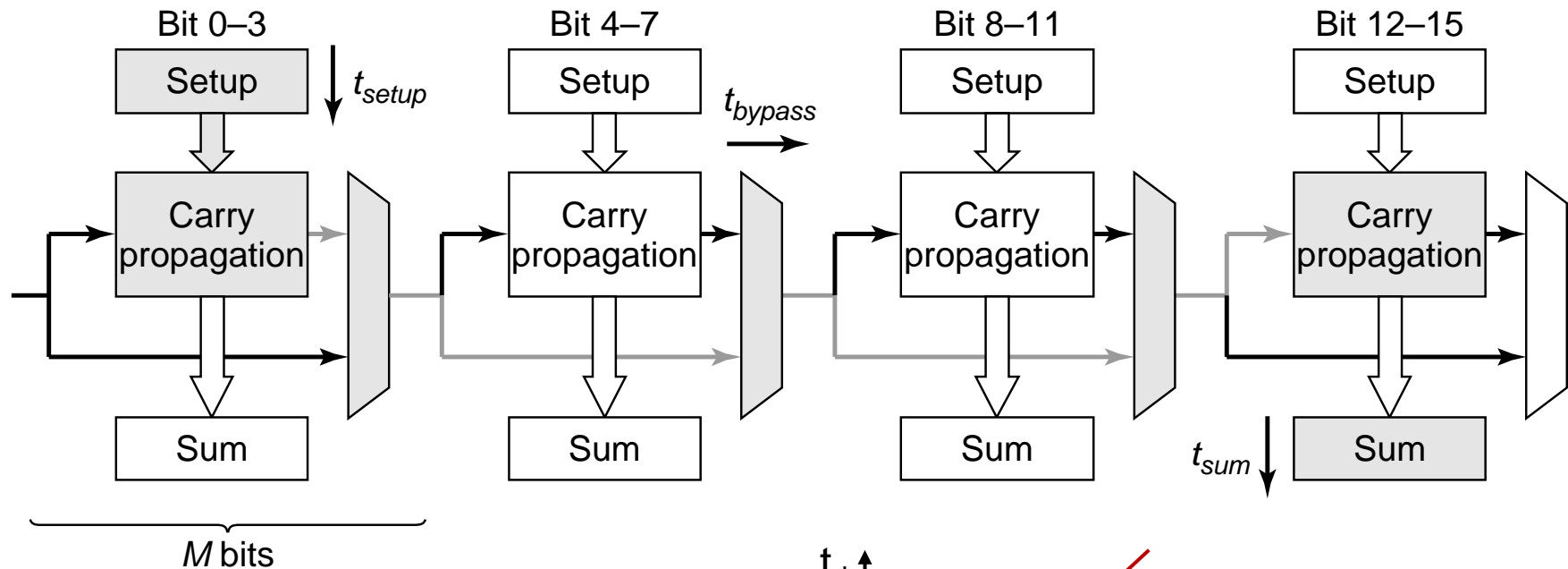

If we have  $N$  bits,  
 $M$  bits/block,  
 $N/M$  blocks,


worst case delay is
 
$$t_{adder} = t_{setup} + M \cdot t_{carry} + (N/M - 1) \cdot t_{bypass} + (M - 1) \cdot t_{carry} + t_{sum}$$



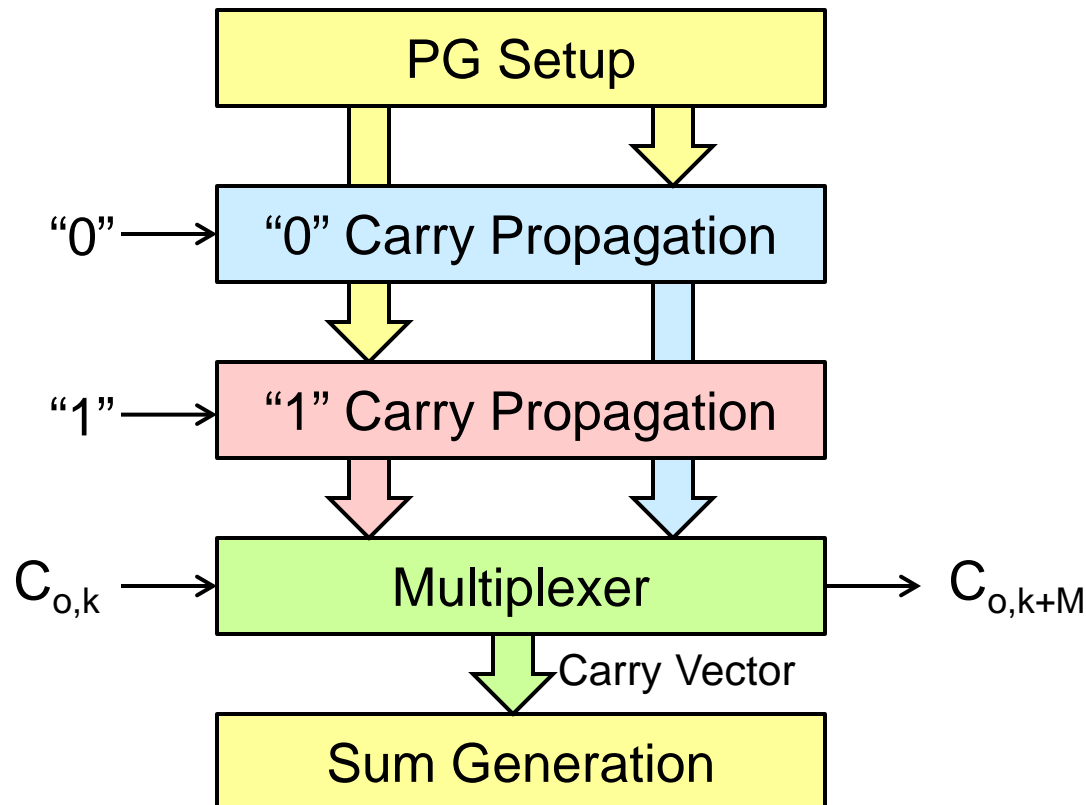
# Carry-Select Adder

- For each M-bit block:
- Calculate block carries for both  $C_{in}=0$  and  $C_{in}=1$
- Then when  $C_{in}$  finally arrives, use multiplexer to select correct result





# Carry-Select Adder – Critical Path

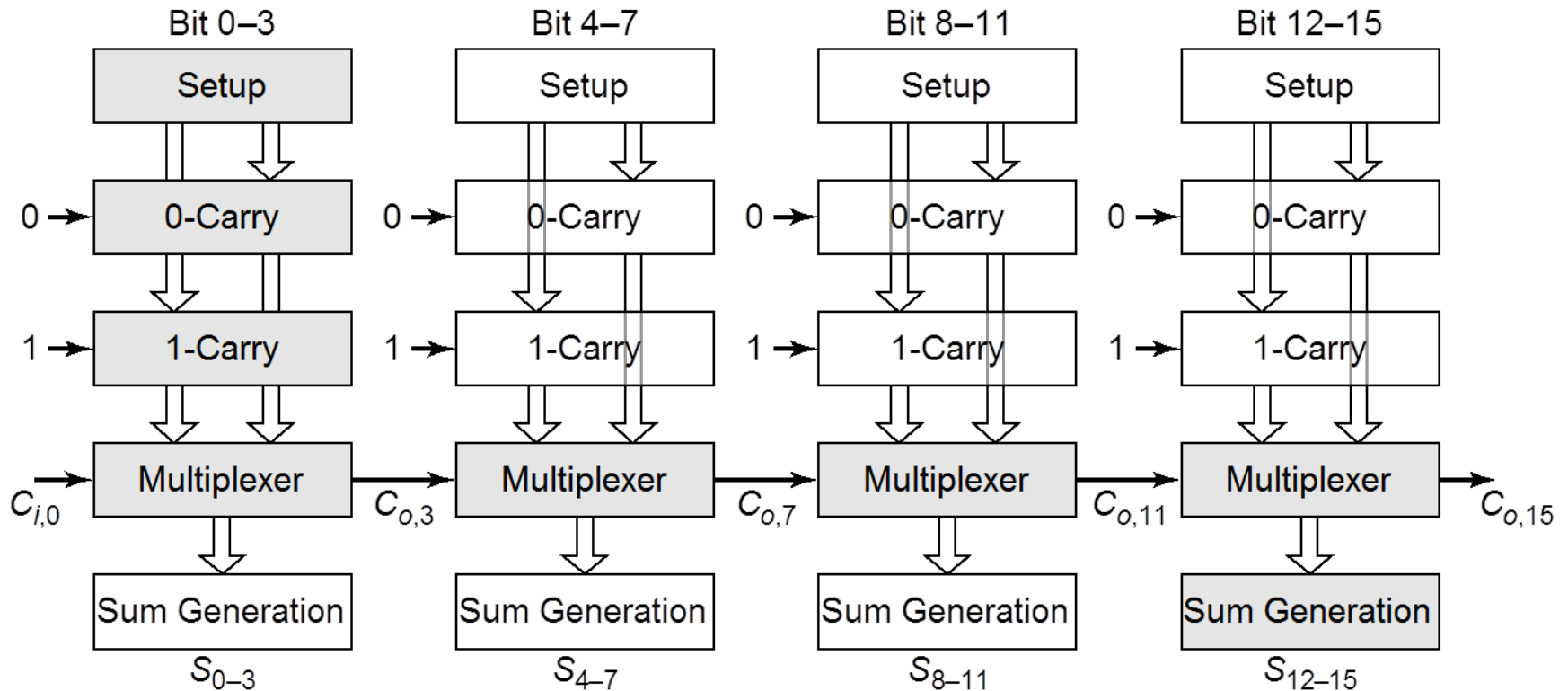


worst case delay is:

$$t_{adder} = t_{setup} + M \cdot t_{carry} + (N/M) \cdot t_{mux} + t_{sum}$$
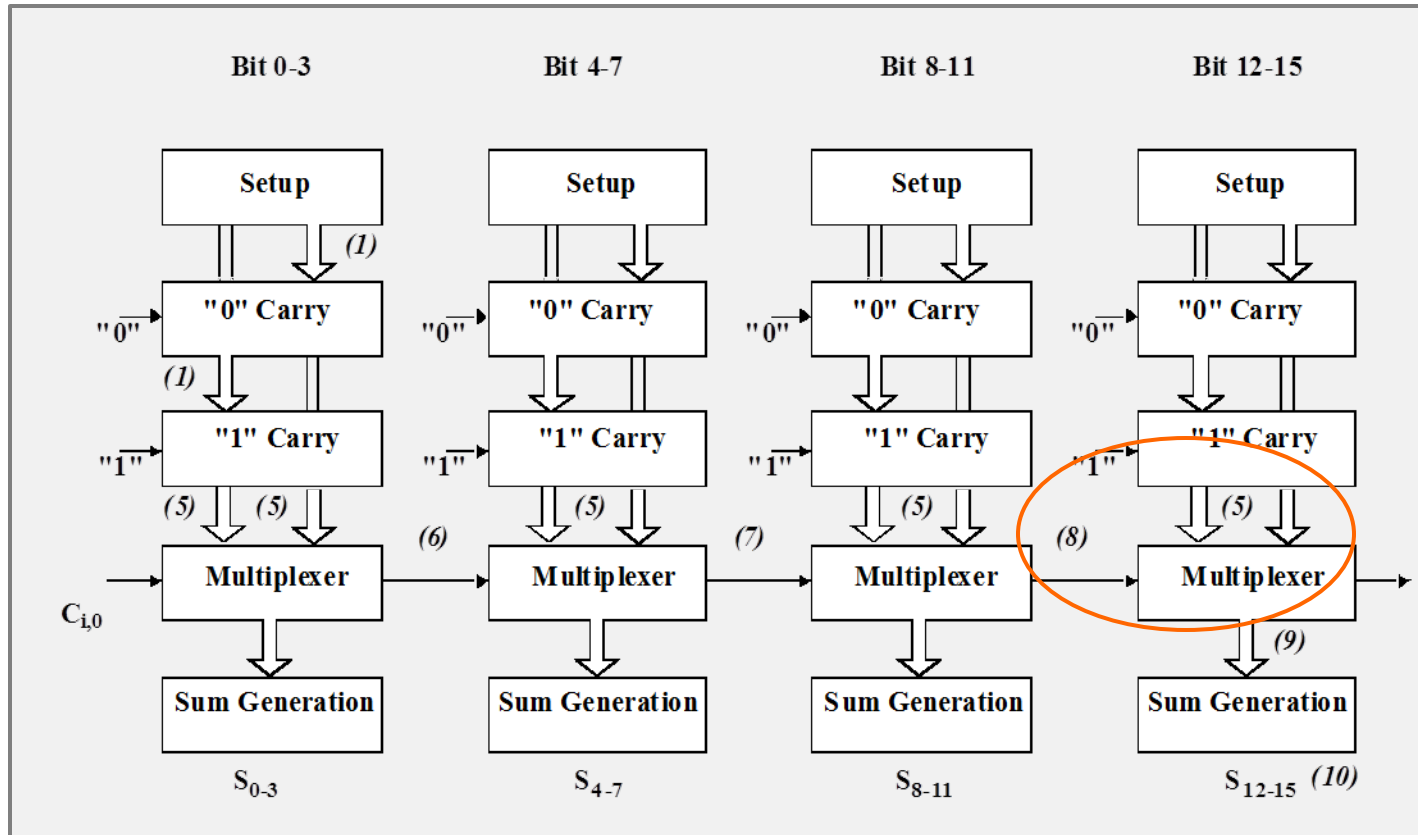
# Linear Carry-Select Adder


- Lets look at worst case delays in adder with  $N=16$ ,  $M=4$
- Assume  $t_{\text{full-adder}} = t_{\text{multiplexer}} = 1$



- For last block, output of "0" and "1" carry sections arrive well before multiplexer select signal from previous block
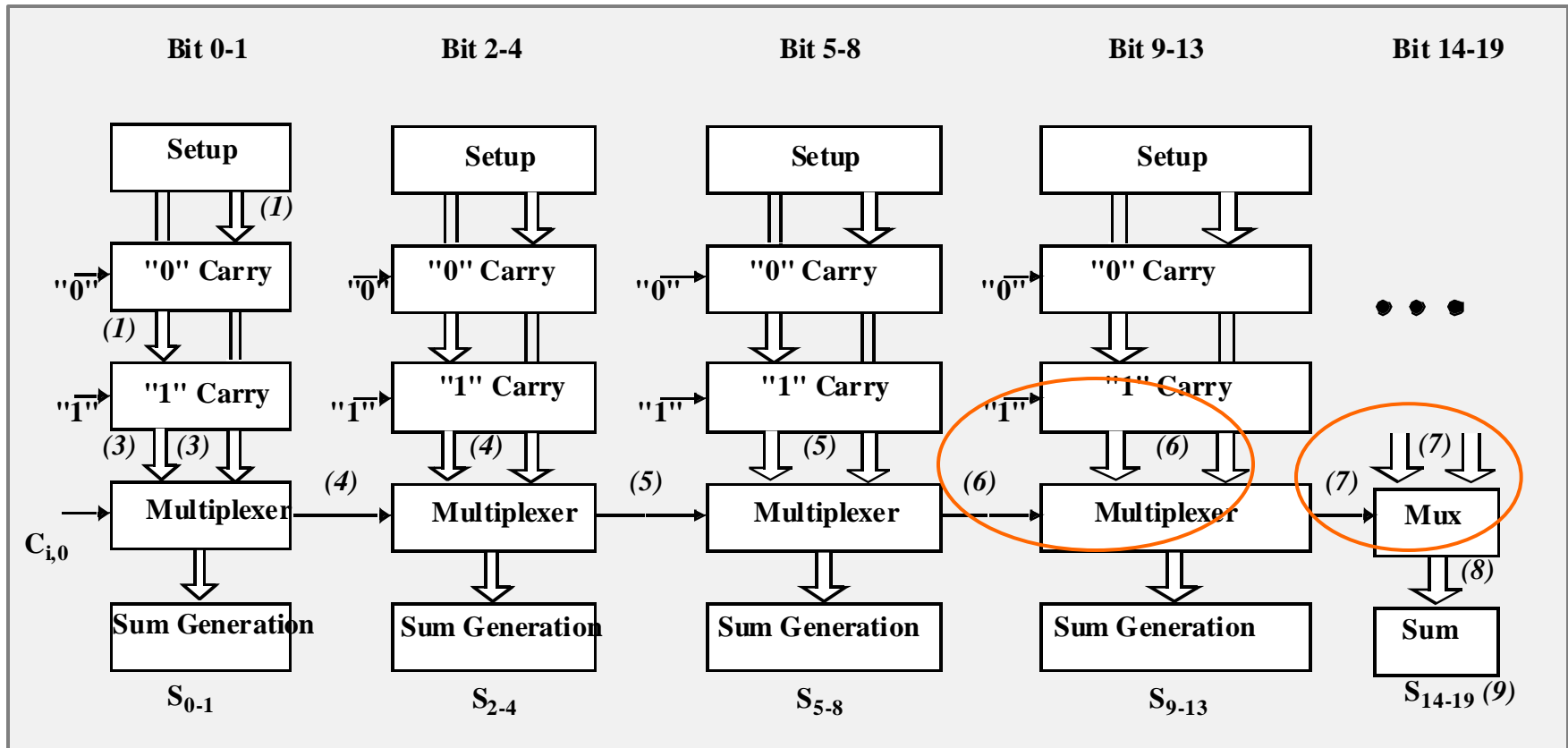
# Square Root Carry-Select Adder


- By making blocks of increasing length, we can perform more carry calculations while waiting for the multiplexer select signal



$$t_{adder} = t_{setup} + M.t_{carry} + (\sqrt{2N}).t_{mux} + t_{sum}$$
 
# Carry-Select Adder: Delay Comparisons


- Square root select particularly effective for large  $N$  (e.g. 64-bit)



# Tree Adders


- For wide adders ( $N > 32$  bits) delay of carry lookahead (bypass or select) adders is dominated by delay of passing carry through the lookahead stages (multiplexers).
- This delay can be reduced by recursively looking ahead across lookahead blocks, e.g.
  - lookahead across 2-bit blocks to generate  $C_{in}$  to 4-bit blocks
  - lookahead across 4-bit blocks to generate  $C_{in}$  to 8-bit blocks, etc.
- Delay can  $O(\log N)$  *(at expense of area and power!)*

e.g. Brent-Kung Adder

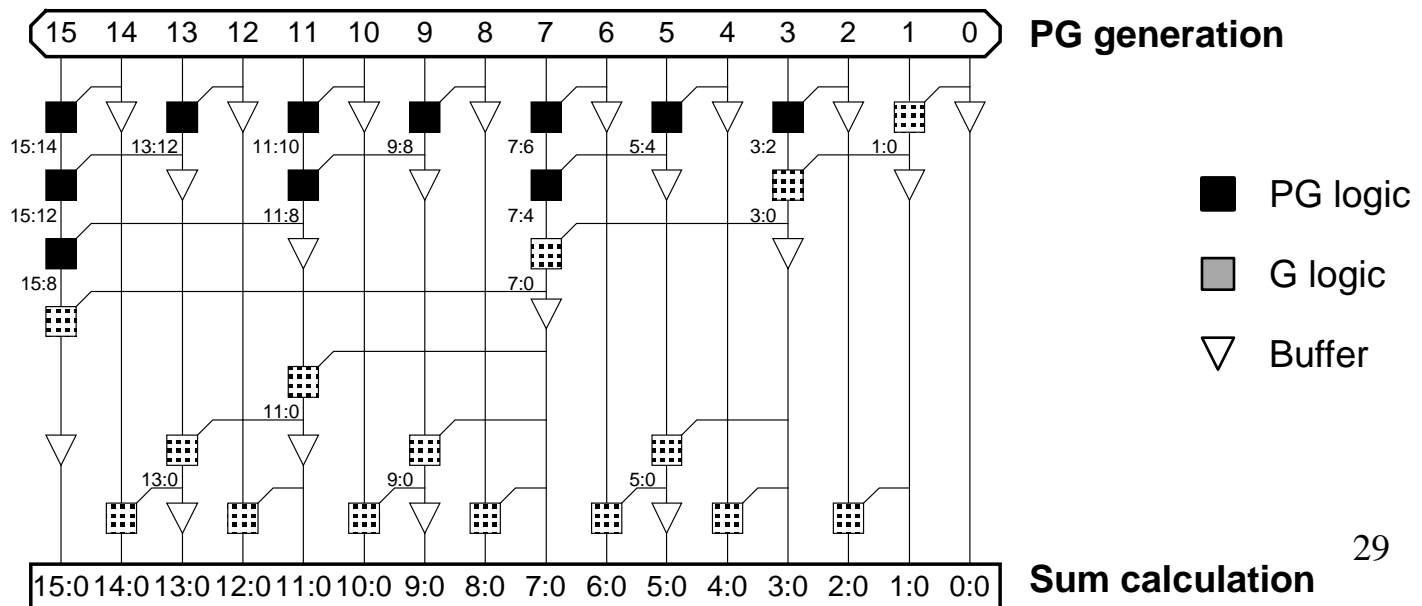
 
# Subtraction

- $A - B = A + (-B)$  (where  $-B$  is two's complement of  $B$ )
- $-B = \text{NOT}(B) + 1$





# Unsigned Multiplication

- Example:

1 1 0 0	:12 <sub>10</sub>	multiplicand
X 0 1 0 1	: 5 <sub>10</sub>	multiplier
<hr/>		
1 1 0 0		} partial products
0 0 0 0		
1 1 0 0		
0 0 0 0		
<hr/>		
0 0 1 1 1 1 0 0	:60 <sub>10</sub>	product


- M x N-bit multiplication
  - Produce N M-bit partial products
  - Sum these to produce (M+N)-bit product

# Array Multiplier

  





# Array Multiplier – Critical Path

 


$$t_{\text{mult}} = (M+N-3).t_{\text{carry}} + N.t_{\text{sum}} + t_{\text{AND}}$$

# Carry Save Multiplier

  

# Carry Save Multiplier – Critical Path

 


$$t_{\text{mult}} = (M+N-2).t_{\text{carry}} + 2.t_{\text{sum}} + t_{\text{AND}}$$

OR

$$t_{\text{mult}} = (N-1).t_{\text{carry}} + t_{\text{fast\_adder}} + t_{\text{sum}} + t_{\text{AND}}$$

# CSA Multiplier – Compact Layout

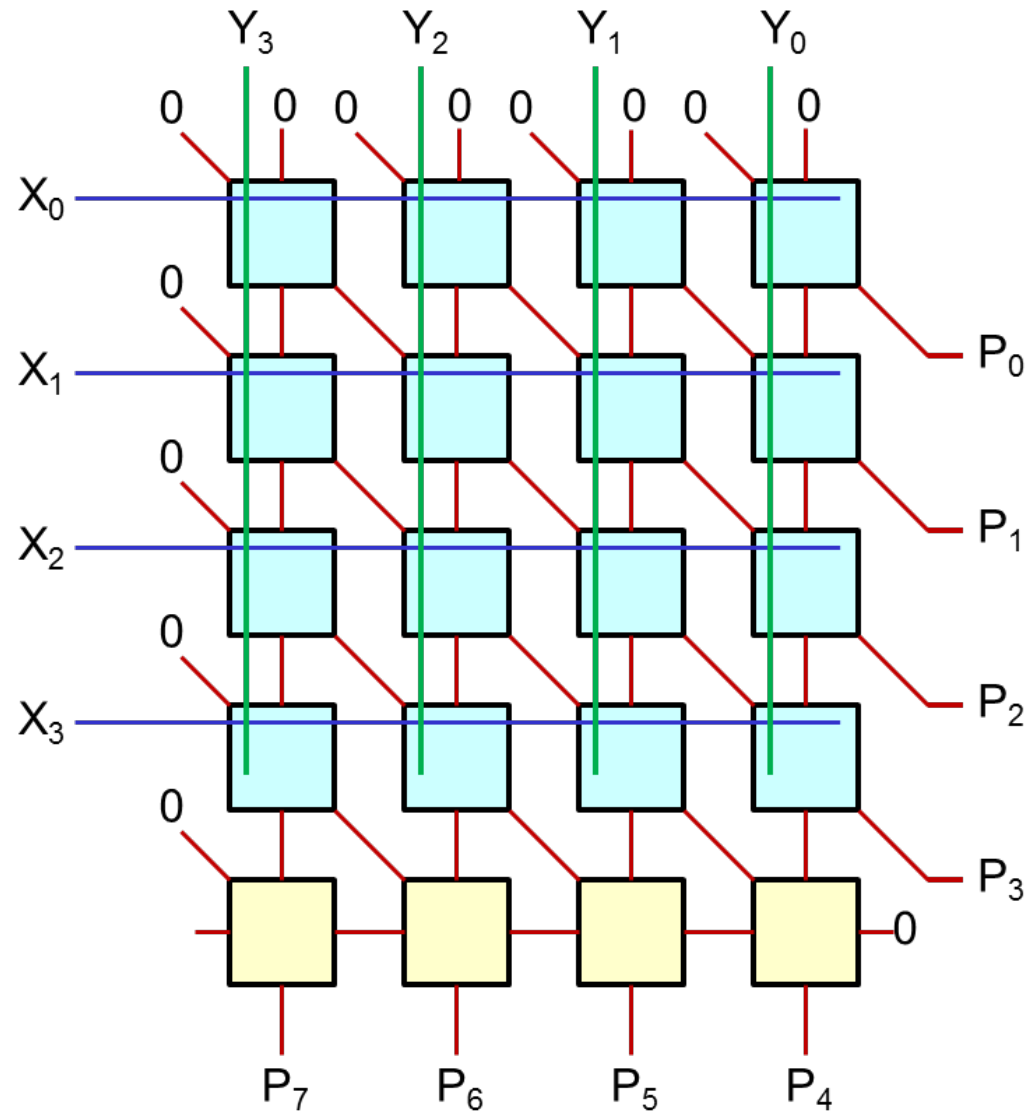

# Two's Complement (Signed) Multiplication

- In two's complement representation:  $X = -x_{N-1} \cdot 2^{N-1} + \sum_{i=0}^{N-2} x_i 2^i$

$$P = Y \cdot X = \left[ -y_{M-1} \cdot 2^{M-1} + \sum_{j=0}^{M-2} y_j 2^j \right] \cdot \left[ -x_{N-1} \cdot 2^{N-1} + \sum_{i=0}^{N-2} x_i 2^i \right]$$

$$= \sum_{i=0}^{N-2} \sum_{j=0}^{M-2} x_i \cdot y_j \cdot 2^{i+j}$$

unsigned (N-1)x(M-1) multiply

$$+ x_{N-1} \cdot y_{N-1} \cdot 2^{M+N-2}$$

product of MSB's

$$- \left[ \sum_{i=0}^{N-2} x_i \cdot y_{M-1} \cdot 2^{i+M-1} + \sum_{j=0}^{M-2} x_{N-1} \cdot y_j \cdot 2^{j+N-1} \right]$$

two terms to be subtracted

## Baugh-Wooley Partial Products

- Subtraction of these terms is accomplished by adding two's complement, i.e. by adding  $(\overline{term} + 1)$


[illegible]

# Baugh-Wooley Multiplication Array

								$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
								$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$
						1	$\overline{x_5 y_0}$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	
					$\overline{x_5 y_1}$		$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
				$\overline{x_5 y_2}$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$				
			$\overline{x_5 y_3}$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$					
		$\overline{x_5 y_4}$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$						
1	$x_5 y_5$	$\overline{x_4 y_5}$	$\overline{x_3 y_5}$	$\overline{x_2 y_5}$	$\overline{x_1 y_5}$	$\overline{x_0 y_5}$							
$p_{11}$	$p_{10}$	$p_9$	$p_8$	$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$			
 
# Modified Baugh-Wooley Multiplier

- Simply replace AND gate in these cells with NAND gate
  - and set two of the carry-in constants to '1'





# Faster Multipliers

- Multiplication is key element in many DSP applications
  - Digital Filters
  - Transforms
  - Modulation & Correlation
- Many architectures have been proposed to speed up multiplication
  - radix-4 Booth encoding
  - Wallace tree
  - Compressor trees
  - Pipelining
  - Various combinations of above
- Each starts by examining critical path and looking for ways to “short-circuit” computation
- Each provides improved speed at cost of area & power